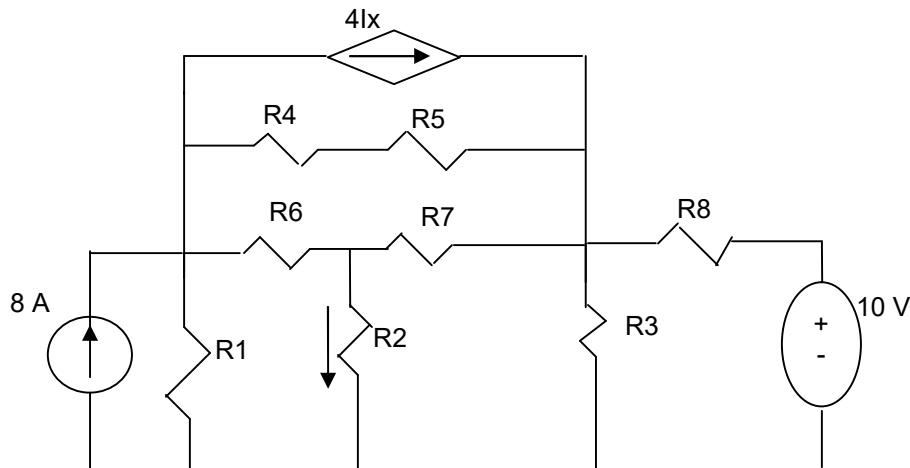


Fundamentals of Electrical Circuits - Chapter 4

1S. For the following circuit find:

- a) Number of Branches
- b) Number of Branches with unknown current
- c) Number of Essential Branches
- d) Number of Essential Branches with unknown current
- e) Number of Nodes
- f) Number of Essential Nodes
- g) Number of Meshes




Solution:

- a) Number of Branches = 11
- b) Number of Branches with unknown current = 9
- c) Number of Essential Branches = 9
- d) Number of Essential Branches with unknown current = 7
- e) Number of Nodes = 6
- f) Number of Essential Nodes = 4
- g) Number of Meshes = 6


1U. For the following circuit:

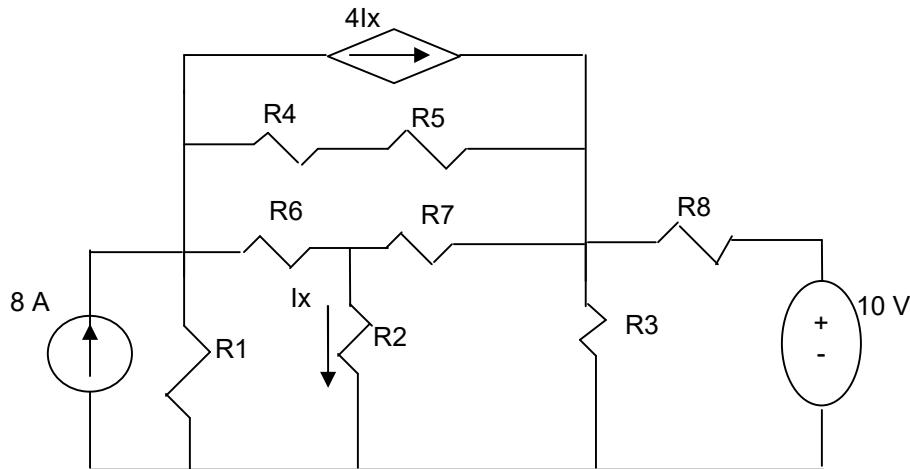- a) How many independent equations can be derived using Kirchhoff's Current Law (KCL)?
- b) How many independent equations can be derived using Kirchhoff's Voltage Law (KVL)?
- c) What two meshes should be avoided in applying Kirchhoff's Voltage Law (KVL)?



Solution:

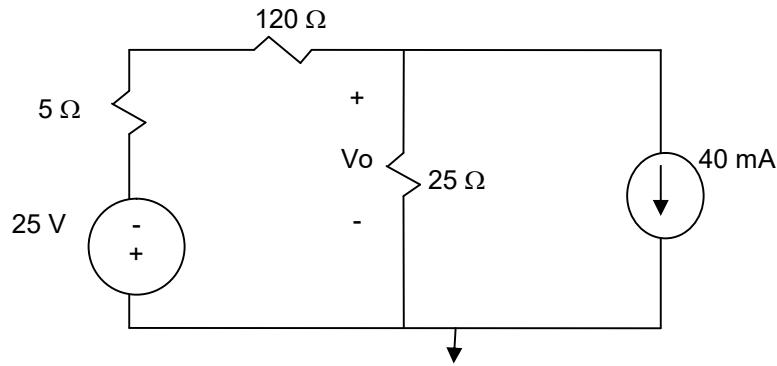-
- 2S. Use the node-voltage method to find V_o in the circuit shown below.




Solution:

$$\frac{V_o - (-25)}{125} + \frac{V_o}{25} + 40 * 10^{-3} = 0$$

$$6V_o = -30$$


$$V_o = -5$$

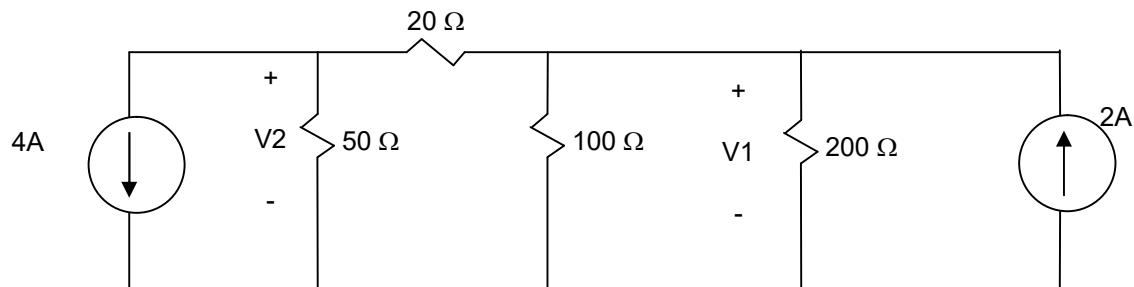-
- 2U. Use the node-Voltage method to find V_1 and V_2 in the following circuit.



Solution:

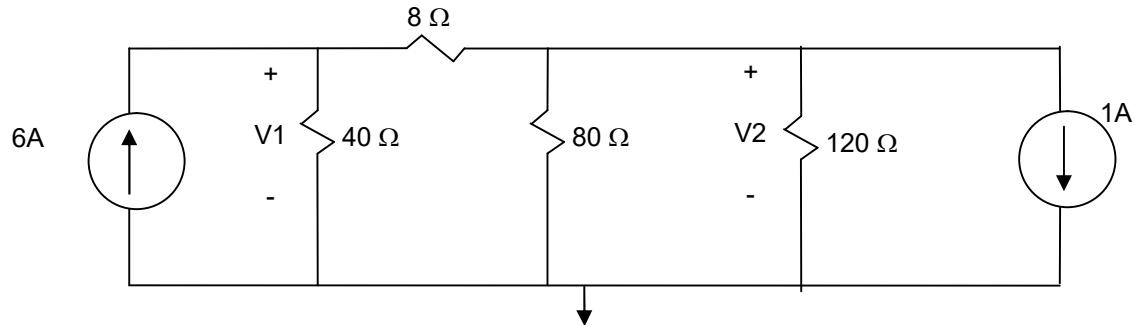2Sb. Use the node-Voltage method to find V₁ and V₂ in the following circuit.



Solution:

Three Nodes so we need to write two Node-Voltage equations:

$$\text{Node } V_1 \rightarrow -6 + V_1/40 + (V_1 - V_2)/8 = 0$$

$$\text{Node } V_2 \rightarrow 1 + V_2/120 + V_2/80 + (V_2 - V_1)/8 = 0$$

Solve two unknowns, two equations


$$6V_1 - 5V_2 = 240$$

$$-30V_1 + 35V_2 = -240$$


$$V_1 = 120 \text{ V} \quad \text{and} \quad V_2 = 96 \text{ V}$$

2Sc. a) Use the node-voltage method to find the branch currents ($i_a - i_e$) in the circuit shown below.

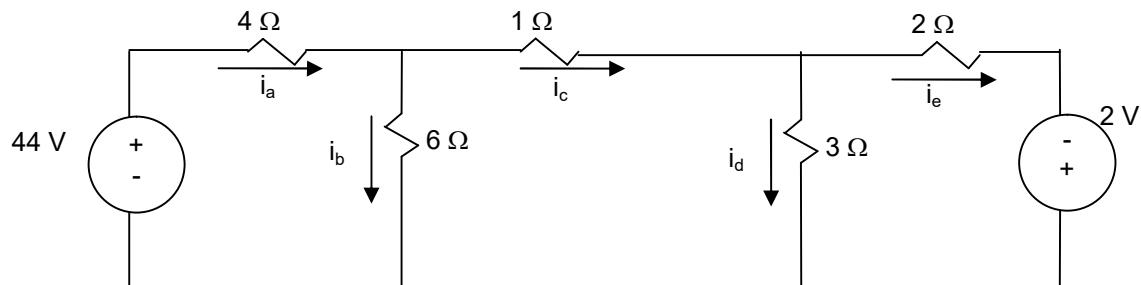b) Find the total power developed in the circuit.



Solution:

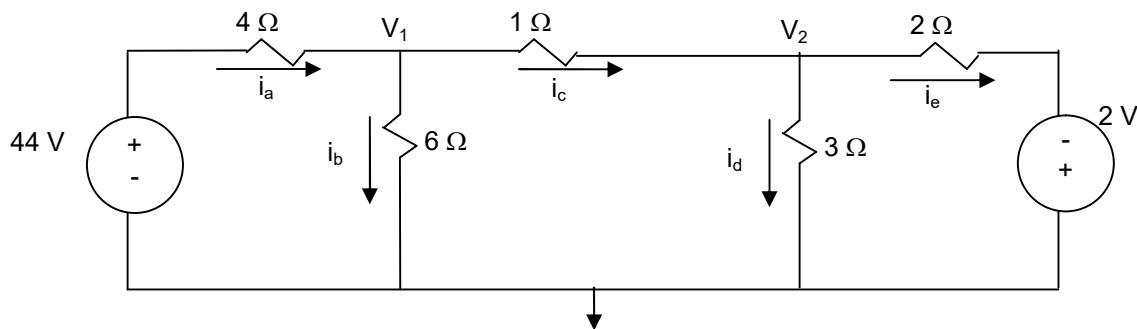

a) Three essential nodes so we can write 2 Node-Voltage Equations:

$$\frac{V_1 - 44}{4} + \frac{V_1}{6} + \frac{V_1 - V_2}{1} = 0$$

$$\frac{V_2 - (-2)}{2} + \frac{V_2}{3} + \frac{V_2 - V_1}{1} = 0$$

$$17V_1 - 12V_2 = 132$$

$$-6V_1 + 11V_2 = -6$$

$$V_1 = 12 \quad \text{and} \quad V_2 = 6$$

\therefore


$$i_a = 8A; \quad i_b = 2A; \quad i_c = 6A; \quad i_d = 2A; \quad i_e = 4A;$$

$$i_a - i_e = 8 - 4 = 4A$$

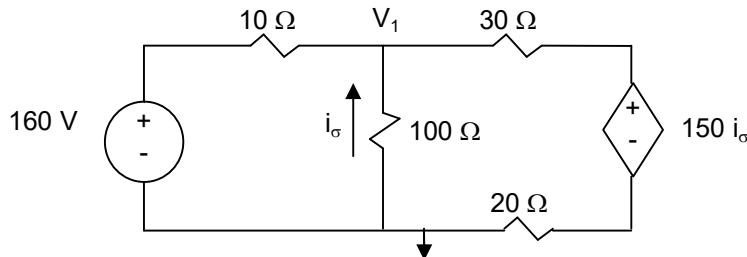b) $P_{\text{total developed}} = ?$

$$P_{\text{total developed}} = -4*(8)^2 - 6*(2)^2 - 1*(6)^2 - 3*(2)^2 - 2*(4)^2 = -360W$$

3S. Use the node-voltage method to calculate the power delivered by the dependent voltage source in the following circuit.



Solution:

There is only one node and one reference node \rightarrow one node-voltage equation

$$\frac{V_1 - 160}{10} + \frac{V_1}{100} + \frac{V_1 - 150i_\sigma}{50} = 0 \quad \text{and} \quad i_\sigma = -\frac{V_1}{100}$$


$$\text{Replace } i_\sigma \text{ in first equation} \Rightarrow \frac{V_1 - 160}{10} + \frac{V_1}{100} + \frac{V_1 + 1.5V_1}{50} = 0 \Rightarrow V_1 = 100V$$

$$\text{Dependent Voltage } V_d = 150i_\sigma = -\frac{150V_1}{100} = -150V$$

$$50\Omega \text{ Current } I_{50\Omega} = \frac{V_1 - V_d}{50} = \frac{100 - (-150)}{50} = 5$$


$$P_{\text{Dependent Source}} = V_d * I_{50\Omega} = (-150) * (5) = -750W \text{ delivered}$$

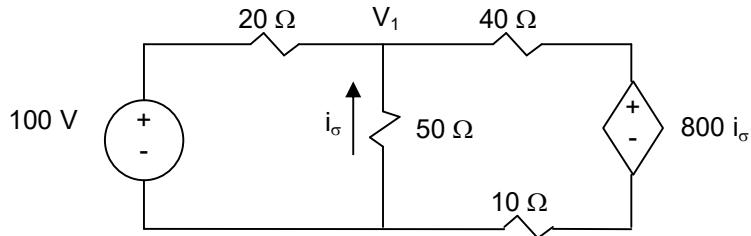3U. Use the node-voltage method to calculate the power delivered by the dependent voltage source in the following circuit.




Solution:

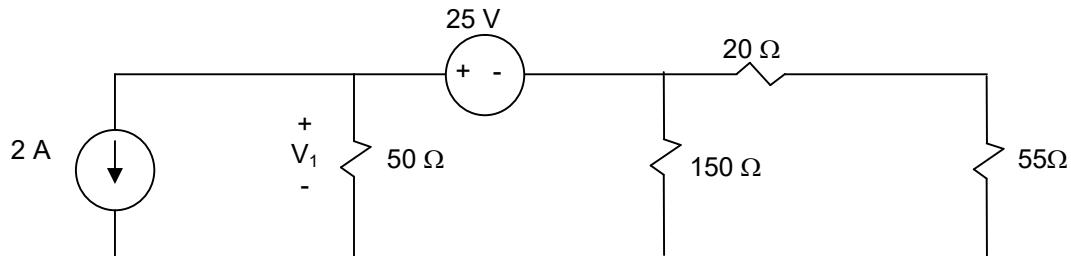4S. Use the node-voltage method to find V_1 and the power delivered by the 25 V voltage source in the following circuit,



Solution: $P_{25V} = ?$

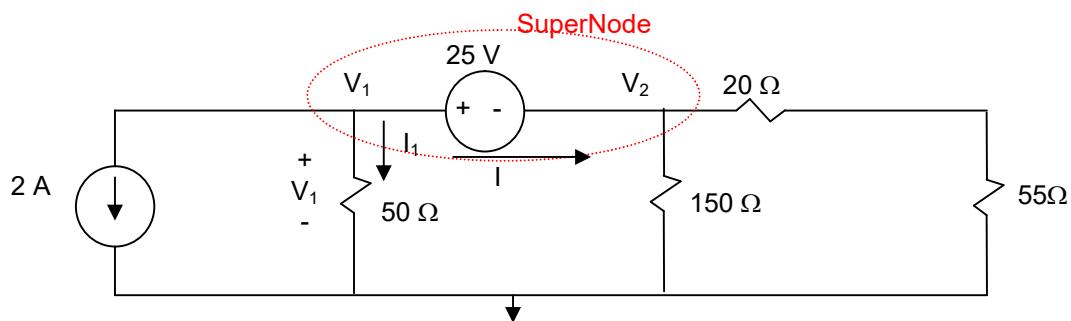

Use SuperNode technique (V_1 & V_2):

KCL for Super Node (all current out of supernode) $\rightarrow 2 + V_1/50 + V_2/150 + V_2/75 = 0$

We also have the relationship between nodes in superr node $\rightarrow V_1 - V_2 = 25$


$$V_1 = -37.5 \text{ V}; V_2 = -62.5 \text{ V};$$

$$I_1 = V_1/50 = -37.5/50 = -0.75 \text{ A}$$

$$\text{KCL at node } V_1 \rightarrow 2 - 0.75 + I = 0 \rightarrow I = -1.25 \text{ A}$$


$$P_{25V} = V_1 \cdot I = (25) \cdot (-1.25) = -31.25 \text{ W delivered.}$$

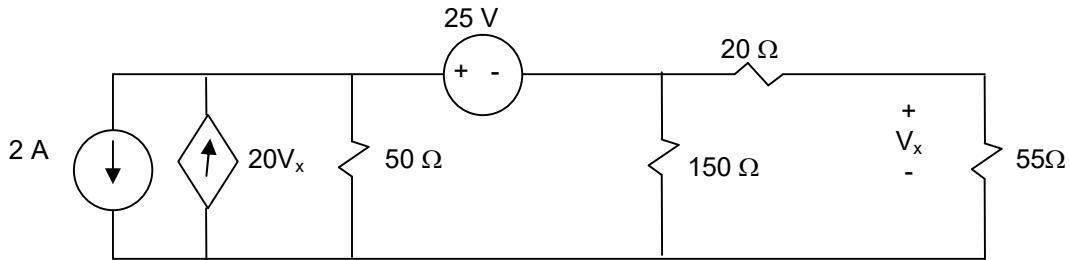4U. Use the node-voltage method to find V_x and the power consumed by the 55Ω resistor in the following circuit:




Solution:

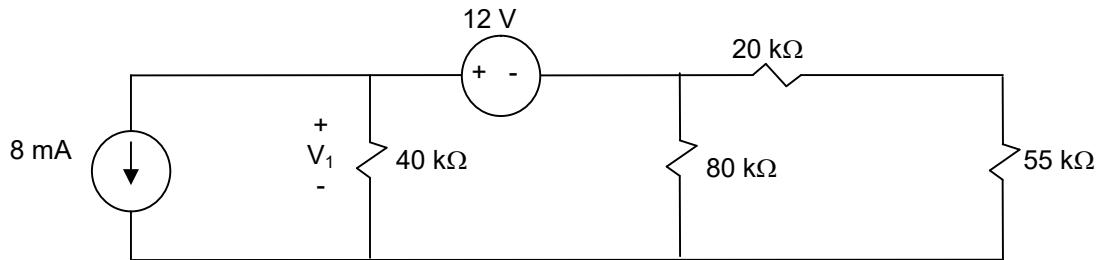4Sb. Use the node-voltage method to find V_1 in the following circuit,



Solution:

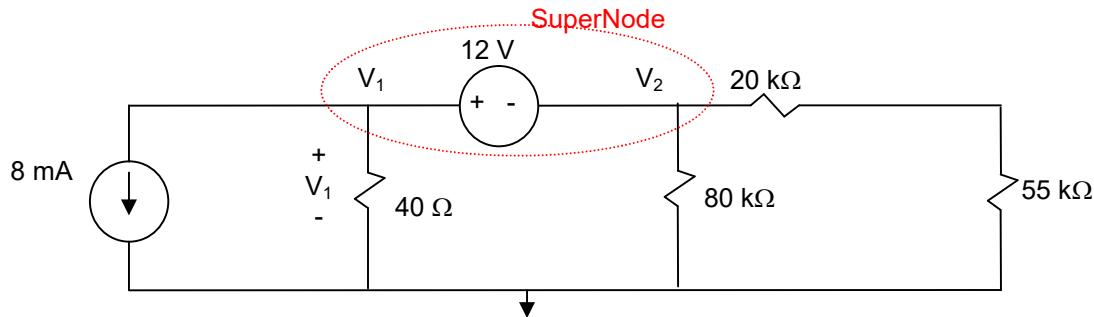

Use SuperNode technique (V_1 & V_2):


$$\text{KCL for Super Node (all current out of SuperNode)} \rightarrow 8 + V_1/40 + V_2/80 + V_2/75 = 0 \rightarrow (1/40)V_1 + (1/80 + 1/75)V_2 = -8$$

$$\text{We also have the relationship between nodes in super node} \rightarrow V_1 - V_2 = 12$$

$$\underline{V_1 = -151.3 \text{ V}}$$


5S. a) Use the mesh-current method to find the total power developed in the following circuit.

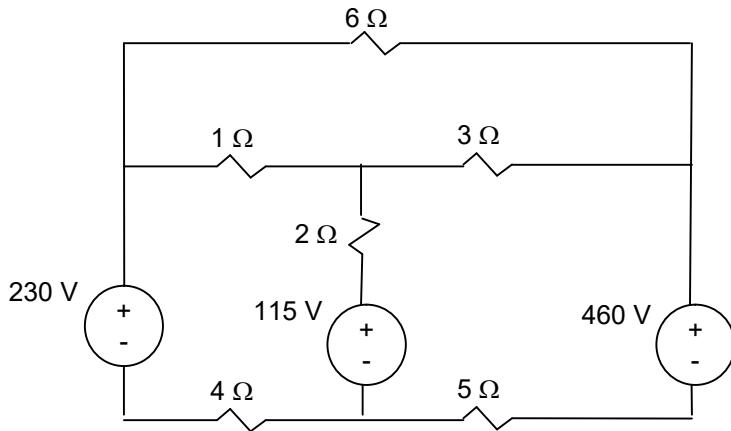b) Check your answer by showing that the total power developed equals the total power dissipated.



Solution:

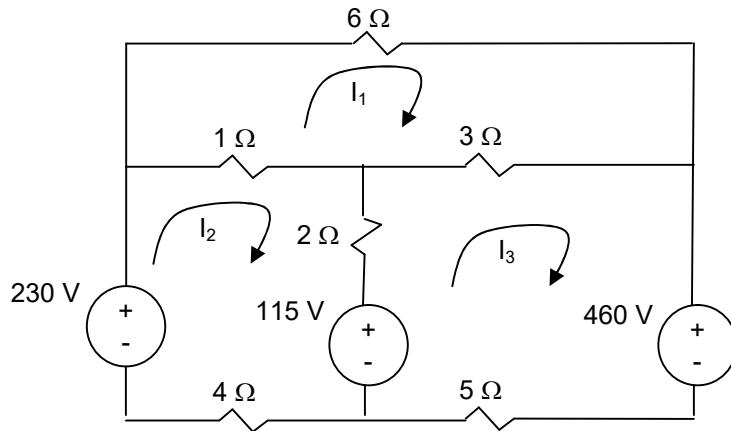a) Apply Mesh-Current to find total power developed



$$\text{Loop #1 KVL} \rightarrow 6I_1 + 3(I_1 - I_3) + (I_1 - I_2) = 0$$

$$\text{Loop #2 KVL} \rightarrow -230 + (I_2 - I_1) + 2(I_2 - I_3) + 115 + 4I_2 = 0$$

$$\text{Loop #3 KVL} \rightarrow 460 + 5I_3 - 115 + 2(I_3 - I_2) + 3(I_3 - I_1) = 0$$

$$I_1 = -10.6A; \quad I_2 = 4.4A; \quad I_3 = -36.8A;$$

$$P_{230V} = 230 * I_2 = 230 * (4.4) = -1,012 \text{ W Developed}$$

$$P_{115V} = 115 * (I_2 - I_3) = 115 * (4.4 - (-36.8)) = 4,738 \text{ W Consumed}$$

$$P_{460V} = 460 * I_2 = 460 * (-36.8) = -16,928 \text{ W Developed}$$

$$P_{\text{Total developed}} = P_{230V} + P_{460V} = -1,012 - 16,928 = 17,940 \text{ W}$$


b) $P_{\text{Total developed}} = P_{\text{Total consumed}}$?

$$\begin{aligned} P_{\text{Total consumed}} &= 6(I_1)^2 + 3(I_1 - I_3)^2 + (I_1 - I_2)^2 + 2(I_2 - I_3)^2 + 4(I_2)^2 + 5(I_3)^2 + P_{115V} \\ &= 6(-10.6)^2 + 3(-10.6 - (-36.8))^2 + (-10.6 - 4.4)^2 + 2(4.4 - (-36.8))^2 + 4(4.4)^2 + 5(-36.8)^2 + P_{115V} \end{aligned}$$

$$P_{\text{Total consumed}} = P_{\text{Total developed}} = 17940 \rightarrow \text{Answer checked.}$$


5U. a) Use the mesh-current method to find the total power developed in the following circuit.

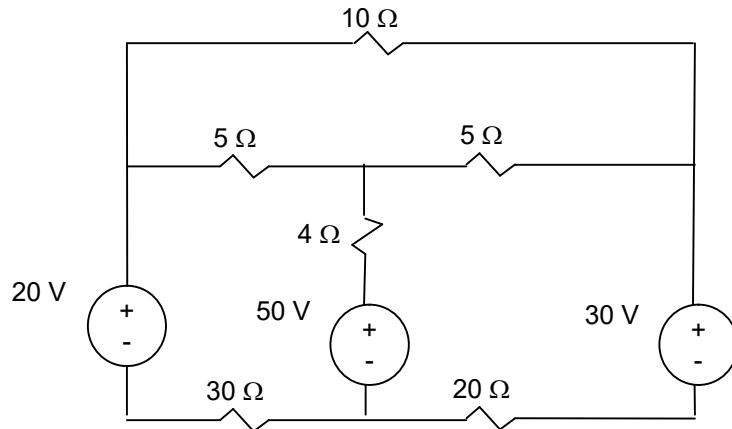b) Check your answer by showing that the magnitude of total power developed equals the total power dissipated.




Solution:

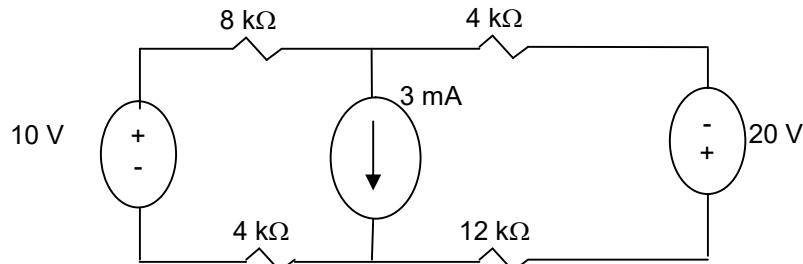5Sb. Use the mesh-current method to find the total power consumed in the circuit shown below.



Solution:

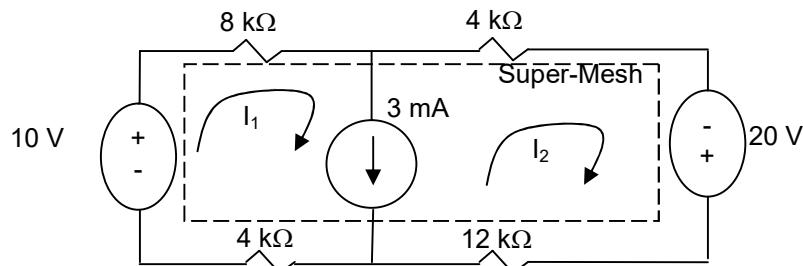

$$\text{Super-Mesh KVL} \rightarrow -10 + 8I_1 + 4I_2 - 20 + 12I_2 + 4I_1 = 0 \rightarrow 12I_1 + 16I_2 = 30$$

$$\text{Relationship of two mesh within super-mesh} \rightarrow I_1 - I_2 = 3$$


$$I_1 = 2.8 \text{ mA}; \quad I_2 = -0.2 \text{ mA};$$

Resistors and the 20v Source are consuming power

$$\begin{aligned} P_{\text{Total Dissipated}} &= \sum(I^2R) + P_{\text{20v Source}} \\ &= 8000*I_1^2 + 4000*I_2^2 + 12000*I_2^2 + 4000*I_1^2 = 12000*(0.0028)^2 + 16000*(0.0002)^2 + 20*(0.0002) \\ &= 0.095 + 0.004 \text{ W} \end{aligned}$$


-
- 6S. a) Use the mesh-current method to solve for I_Δ in the following circuit.
 b) Find the power delivered by the independent current source.

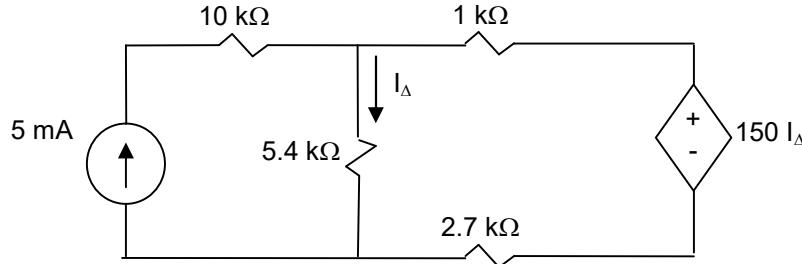c) Find the power delivered by the dependent voltage source.



Solution:

a) find I_Δ

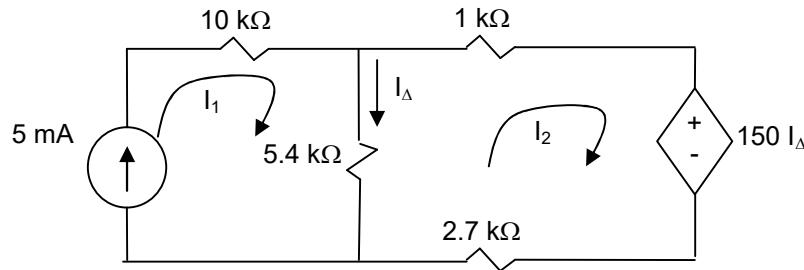

$$\text{We have } I_1 = 0.005 \text{ A} \quad & I_\Delta = I_1 - I_2$$

$$\text{Write KVL for Mesh #2} \rightarrow 5.4(I_2 - I_1) + I_2 + 150(I_1 - I_2) + 2.7I_2 = 0$$


$$\text{Insert } I_1 \text{ value to above equation} \rightarrow 5.4(I_2 - .005) + I_2 + 150(I_2 - .005) + 2.7 = 0$$

$$\rightarrow I_2 = 0.003 \text{ A} \rightarrow I_\Delta = I_1 - I_2 = 0.002 \text{ A}$$

b) $P_{0.005\text{A} \text{ source}} = I_1 * V_{0.005\text{A} \text{ source}} = -(0.005) * (10 * 5 + 5.4 * 2) = -0.304 \text{ W}$

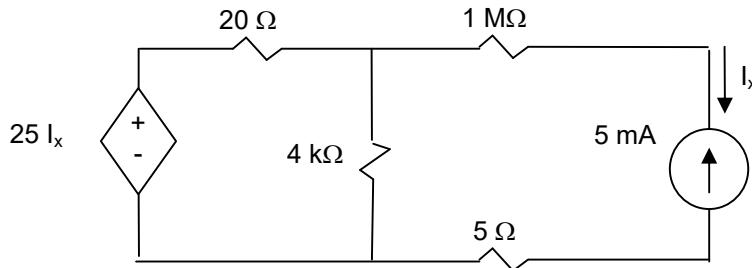c) $P_{0.150I_\Delta \text{ dependent source}} = I_2 * V_{0.005\text{A} \text{ source}} = (.003)*(150*0.002) = 0.9 \text{ mW consumed}$

6U. a) Use the mesh-current method to find I_x in the following circuit.




b) Find the power delivered by the independent current source.

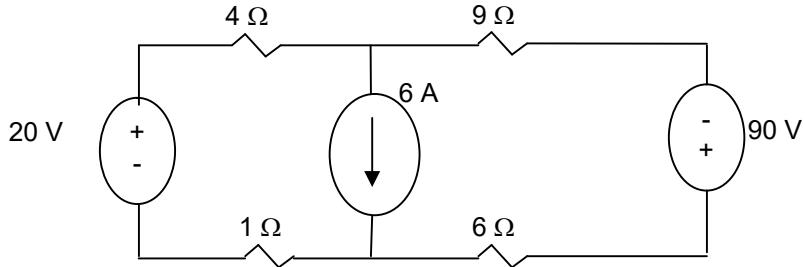c) Find the power delivered by the dependent voltage source.


Solution:

7S. Use the mesh-current method to find the total power dissipated in the circuit shown below.



Solution:

a)

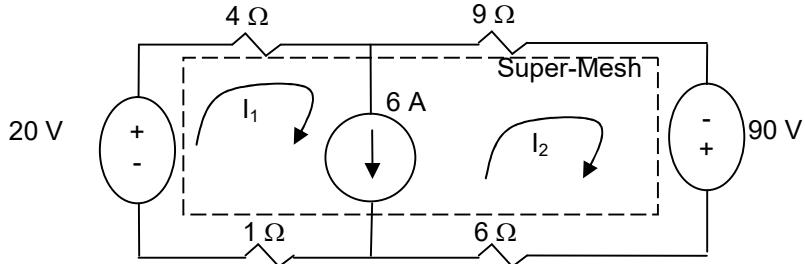


$$\text{Super-Mesh KVL} \rightarrow -20 + 4I_1 + 9I_2 - 90 + 6I_2 + I_1 = 0 \rightarrow 5I_1 + 15I_2 = 110$$

$$\text{Relationship of two mesh within super-mesh} \rightarrow I_1 - I_2 = 6$$

$$I_1 = 10 \text{ A}; \quad I_2 = 4 \text{ A};$$

$$P_{\text{Total Dissipated}} = \sum(I^2R) = 4*I_1^2 + 9*I_2^2 + 6*I_2^2 + I_1^2 = 4*10^2 + 9*4^2 + 6*4^2 + 1*10^2 = 740 \text{ W}$$

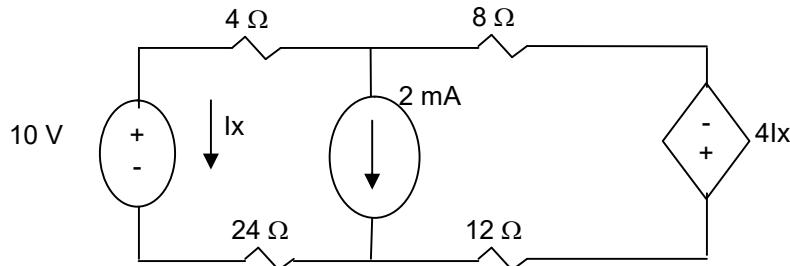7U. Use the mesh-current method to find the total power dissipated in the circuit shown below.




Solution:

8S. Assume you have been asked to find the power dissipated in the 10 Ω resistor in the following circuit.

- Which method of circuit analysis would you recommend? Explain why.
- Use your recommendation method of analysis to find the power dissipated in the 10 Ω resistor.
- Would you change your recommendation if the problem had been to find the power developed by the 4 A current source? Explain.

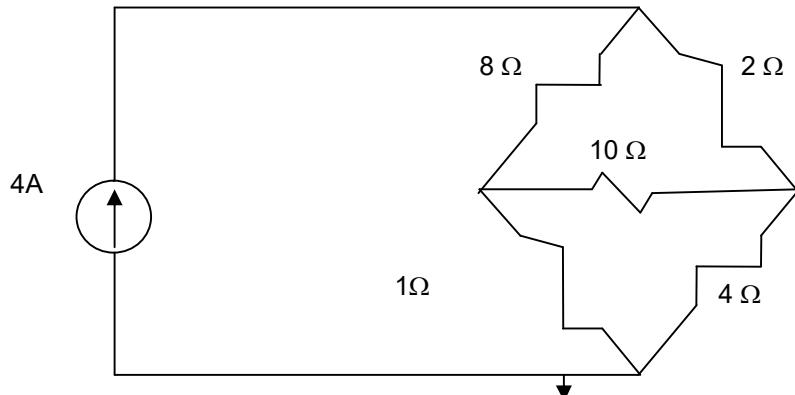d) Find the power delivered by the 4 A current source.



Solution:


a) Which method?

* 4 Essential nodes 3 node-voltage equations

* 6 Essential branches $(6 - (4-1)) = 3$ current-mesh equations

Mesh-Current since one of the Mesh currents is known so there are only two mesh-current equations.

b) $P_{10\Omega} = ?$

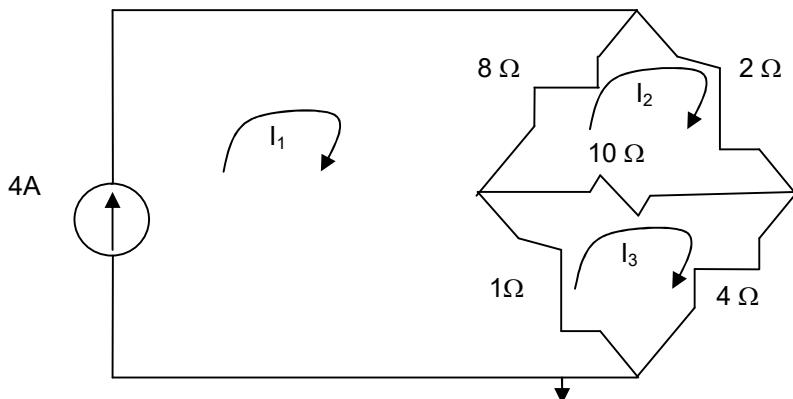

$$\text{KVL for Mesh\#1} \rightarrow I_1 = 4 \text{ A}$$

$$\text{KVL for Mesh\#2} \rightarrow 8(I_2 - I_1) + 2I_2 + 10(I_2 - I_3) = 0$$

$$\text{KVL for Mesh\#3} \rightarrow (I_3 - I_1) + 10(I_3 - I_2) + 4I_3 = 0$$

Inset I_1 value into equations #2 & #3

$$20I_2 - 10I_3 = 32$$

$$-10I_2 + 15I_3 = 4$$

$$I_2 = 2.6; \quad I_3 = 2 \text{ A}$$

$$P_{10\Omega} = R \cdot I^2 = (10) \cdot (2.6 - 2)^2 = 3.6 \text{ W}$$

c) No, since it is straight forward to calculate the voltage drop across the current source from mesh currents.


d) $P_{4\text{A sources}} = ?$

$$P_{4\text{A sources}} = I \cdot V = -4 \cdot (8 \cdot (I_1 - I_2) + 1 \cdot (I_1 - I_3)) = -4 \cdot (8 \cdot (4 - 2.6) + 1 \cdot (4 - 2))$$

$$P_{4\text{A sources}} = 52.8 \text{ W delivered}$$

8U. Assume you have been asked to find the power dissipated in the $20\ \Omega$ resistor in the following circuit.

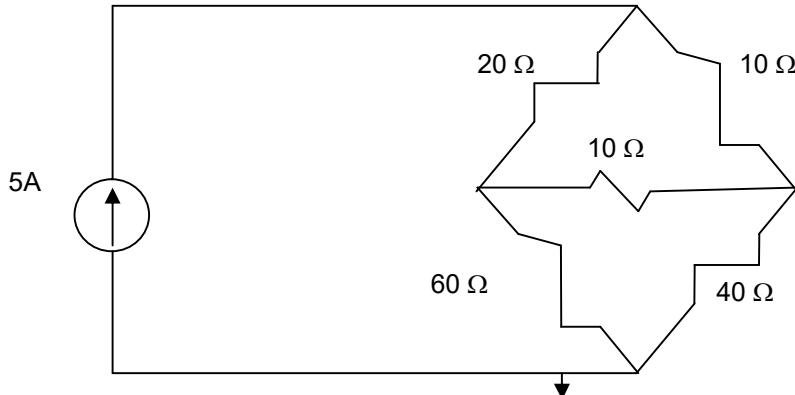
- Which method of circuit analysis would you recommend? Explain why.
- Use your recommendation method of analysis to find the power dissipated in the $20\ \Omega$ resistor.
- Would you change your recommendation if the problem had been to find the power developed by the 5 A current source? Explain.
- Find the power delivered by the 5 A current source.



Solution:

8Sb. a) Would you use the node-voltage or mesh-current method to find the power absorbed by the 20 V source in the following circuit? Explain your choice.

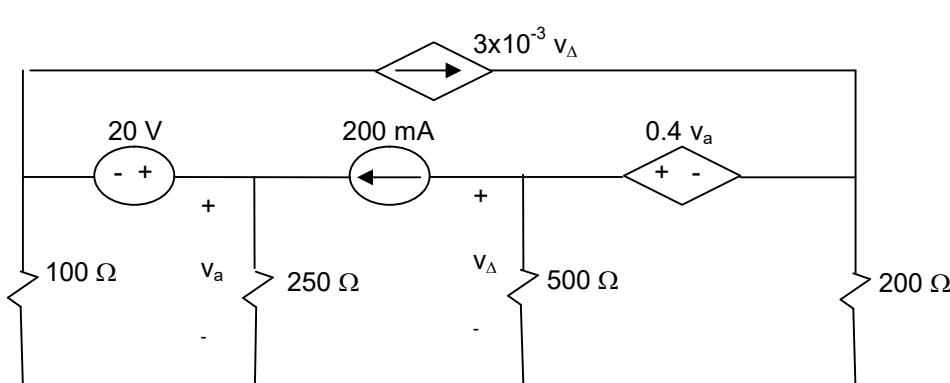- Use the method you selected in (a) to find the power.



Solution:


- Which method?

* 5 Essential nodes 4 node-voltage equations

* 8 Essential branches $(8 - (5-1)) = 4$ mesh-current equations

although number of equations are the same, Node-voltage is a better choice. This is driven by the fact that with the two super nodes and easier constraint equation formulation.

b) $P_{20V \text{ sources}} = ?$

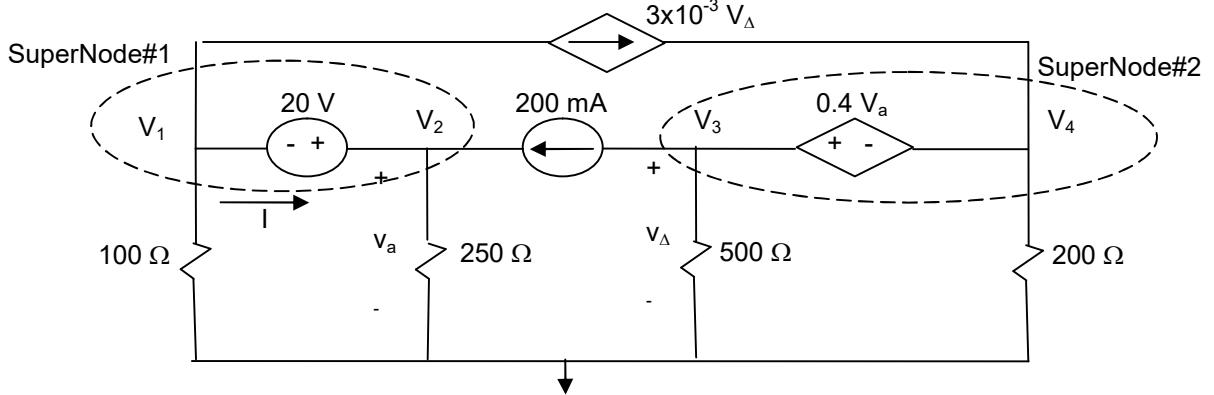

$$\text{Super Node #1 KCL} \rightarrow -0.2 + .003V_\Delta + V_1/100 + V_2/250 = 0$$

$$\text{Relationship} \rightarrow V_2 - V_1 = 20$$

$$\text{Super Node #2 KCL} \rightarrow +0.2 - .003V_\Delta + V_4/200 + V_3/500 = 0$$

$$\text{Relationship} \rightarrow V_3 - V_4 = 0.4 V_a$$

Constraint equations in term of node voltages

$$V_a = V_2$$

$$V_\Delta = V_3$$

Simplified equation:

$$0.01 V_1 + 0.004 V_2 + 0.003 V_3 = 0.2$$

$$-V_1 + V_2 = 20$$

$$-0.001 V_3 + 0.005 V_4 = -0.2$$

$$+0.4 V_2 - V_3 + V_4 = 0$$


$$V_1 = 15.48 \text{ V}; \quad V_2 = 35.482 \text{ V}; \quad V_3 = -32.23 \text{ V}; \quad V_4 = -46.45 \text{ V}$$

Note: I can be found by apply KCL at node V_1

$$P_{20V \text{ Source}} = -(20)I = -20(V_1/100 + 0.003V_3) = -20(15.48/100 + 0.003*(-32.28)) = -1.16 \text{ W}$$


9S. a) Use a series of source transformations to find i_o in the following circuit

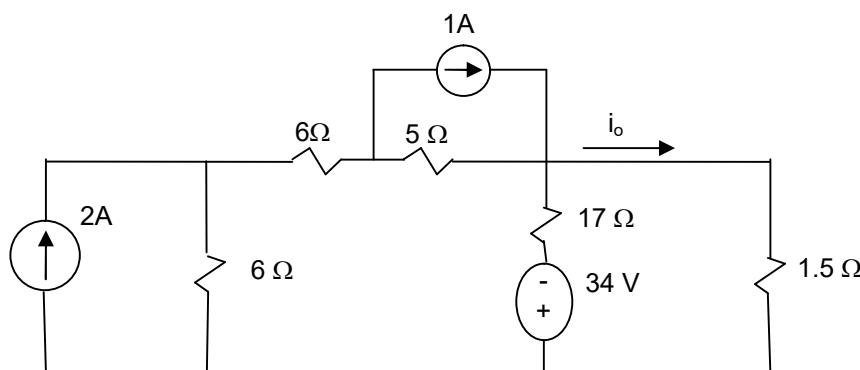b) Verify your solution by using the mesh-current method to find i_o .




Solution:

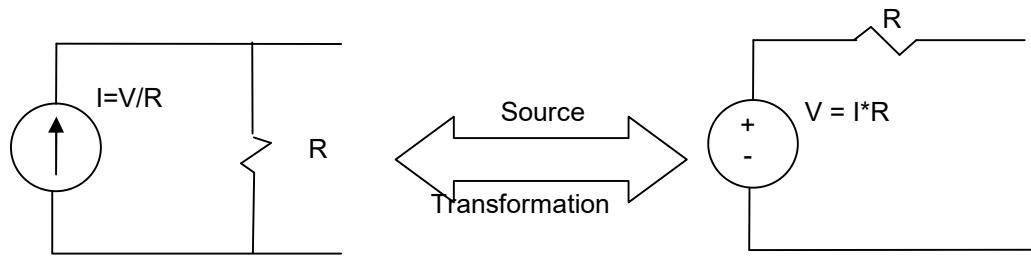a) Use the following transformation rule:




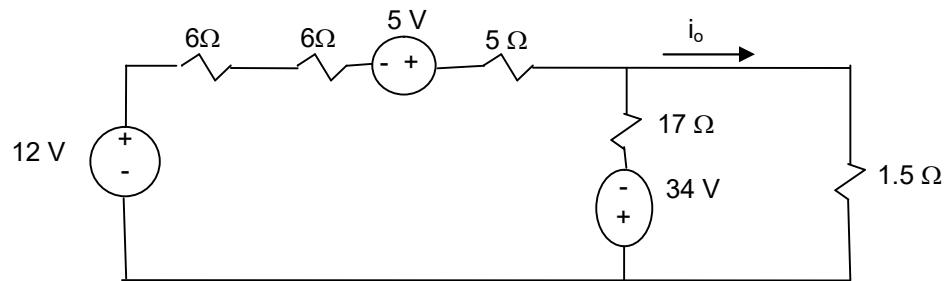First Set of transformations ($2A, 6\Omega \rightarrow 12V$; $1A, 5\Omega \rightarrow 5V$)




Second Set of transformations

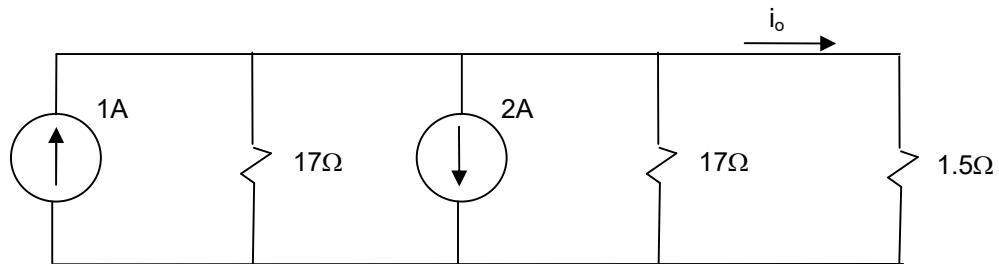$(12+5V, 12+5\Omega \rightarrow 1A; 34V, 17\Omega \rightarrow 2A;)$




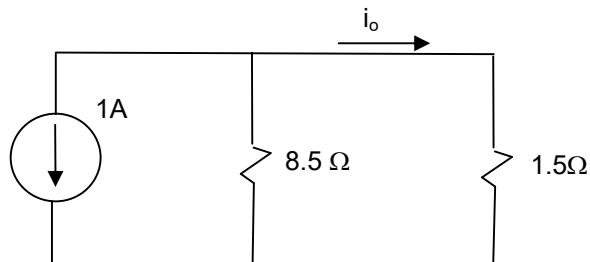Simplify by adding current source and Req for $17 \parallel 17 = 8.5 \Omega$



$$i_o = -1 * (8.5 / (1.5 + 8.5)) = -0.85 A$$

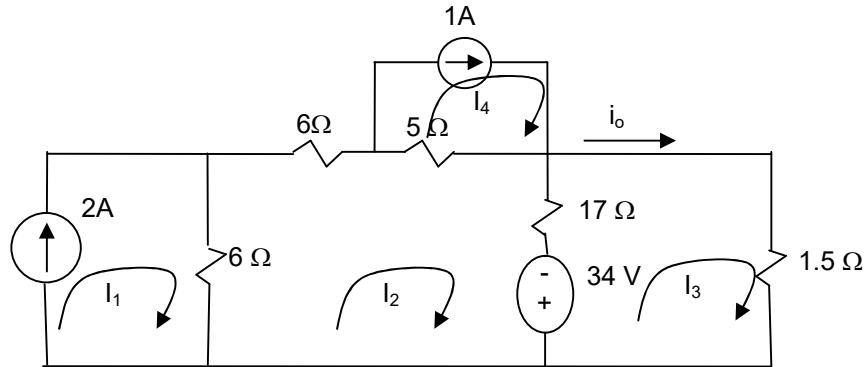b) Find i_o using mesh-current technique.



$$\text{KVL for Mesh #1} \rightarrow I_1 = 2 \text{ A}$$

$$\text{KVL for Mesh #2} \rightarrow 6(I_2 - I_1) + 6 I_2 + 5(I_2 - I_4) + 17 (I_2 - I_3) - 34 = 0$$

$$\text{KVL for Mesh #3} \rightarrow +34 + 17 (I_3 - I_2) + 1.5 I_3 = 0$$

$$\text{KVL for Mesh #4} \rightarrow I_4 = 1 \text{ A}$$


$$34I_2 - 17I_3 - 5I_4 = 46$$

$$-17I_2 + 18.5I_3 = -34$$

$$I_3 = I_o = -0.85 \text{ A}$$


9U. a) Use a series of source transformations to find V_x in the following circuit

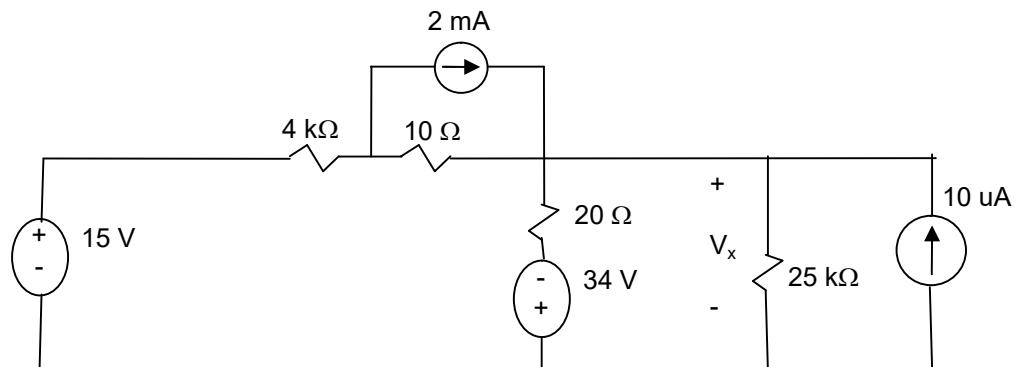b) Verify your solution by using the Node-Voltage method to find V_x .




Solution:

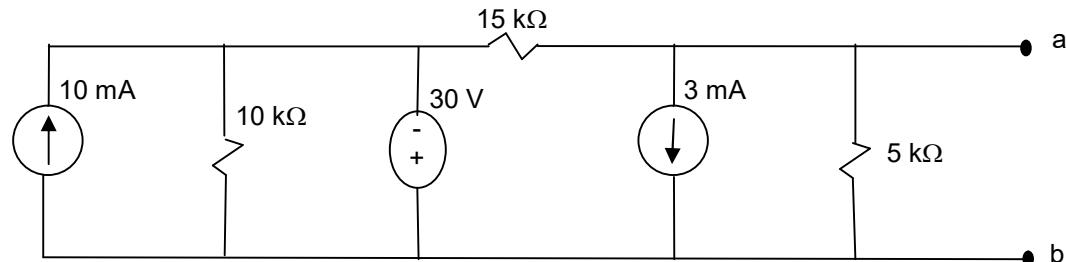10 S. Find the Norton equivalent with respect to the terminals a,b in the following circuit.



Solution:

Step 1 -- Find I_{SC} (a-b shorted)

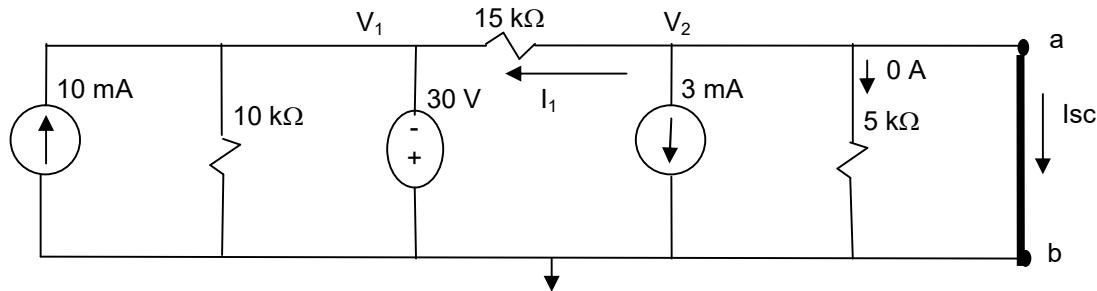

$$V_1 = -30 \text{ V}$$


$$V_2 = 0 \text{ V}$$

$$I_1 = (V_2 - V_1) / 15\text{K} = 2 \text{ mA}$$

$$\text{KCL at } V_2 \rightarrow I_{sc} + 0 + 3 + I_1 = 0 \rightarrow I_{sc} = -5 \text{ mA}$$


Step 2 – Find $R_{th} = R_{th}$ by deactivating sources

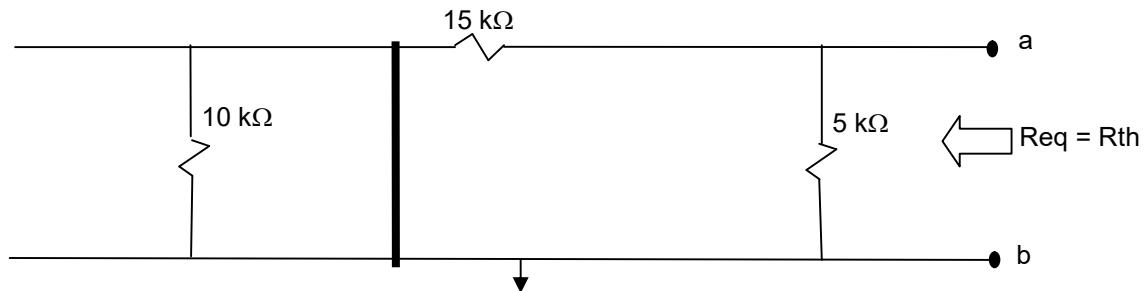(Current Source \rightarrow Open $I=0$; Voltage Source \rightarrow short $V=0$)




$$R_{th} = ((10 \parallel 0) + 15) \parallel 5 = 3.75 \text{ k}\Omega$$

Step 3 – Draw Norton Equivalent

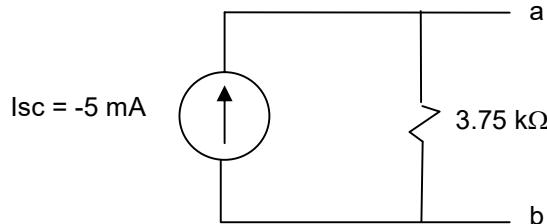


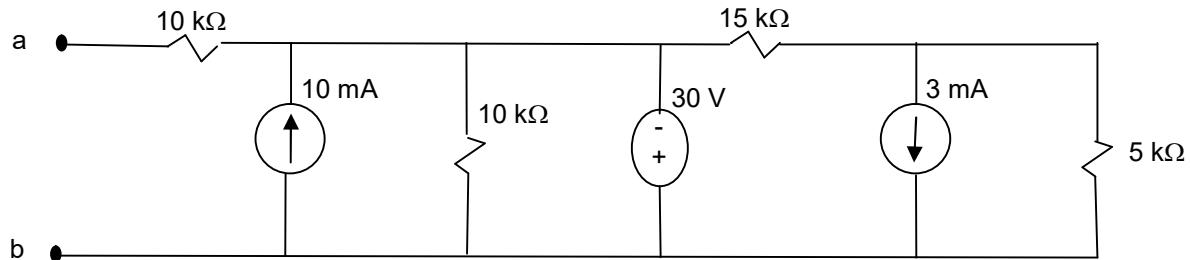10U. Find the Norton equivalent with respect to the terminals a,b in the following circuit.



Solution:

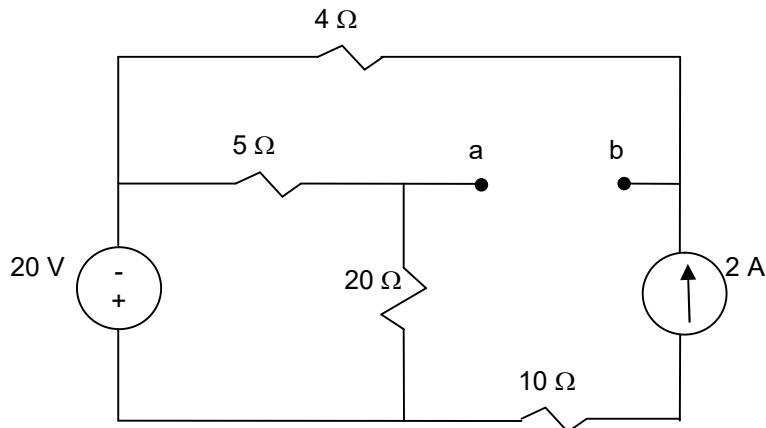10S. Find and draw the Norton equivalent of the following circuit at terminals a and b.




Solution:

Deactivate sources to find $R_{th} = R_{ab}$

$$R_{th} = R_{ab} = (4 + (5 \parallel 20)) = 8 \Omega$$

Find $I_{sc} = I_{ab}$

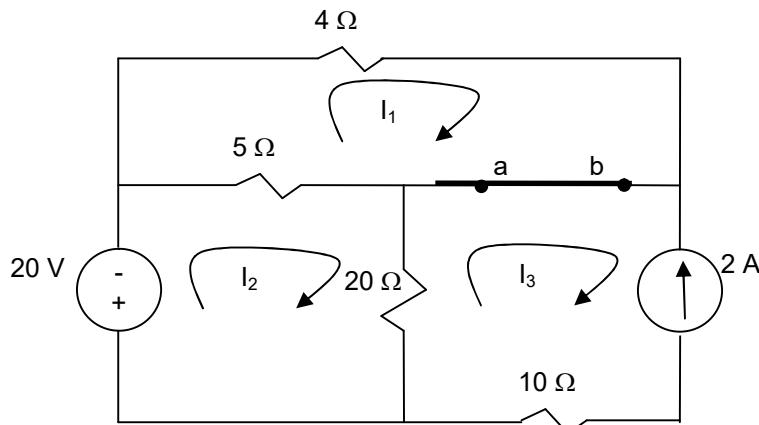

$$\text{Mesh } \#1 \rightarrow 4I_1 + 5(I_1 - I_2) = 0 \rightarrow$$

$$\text{Mesh } \#2 \rightarrow +20 + 5(I_2 - I_1) + 20(I_2 - I_3) = 0$$

$$\text{Mesh } \#3 \rightarrow I_3 = -2$$


$$9I_1 - 5I_2 = 0 \rightarrow I_2 = 9I_1/5$$

$$-5I_1 + 25I_2 = -60$$

$$\rightarrow -5I_1 + 45I_1 = 60 \rightarrow I_1 = -1.5$$


$$\text{Find } I_{sc} = I_{ab} = I_3 - I_1 = -0.5$$

Norton Equivalent:

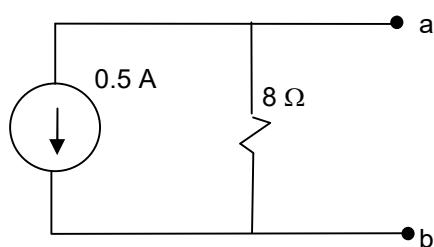

- 11S. The Wheatstone bridge in the circuit shown below, is balanced when R_3 equals 500Ω . If the galvanometer had a resistance of 50Ω , how much current will the galvanometer detect when the bridge is unbalanced by setting R_3 to 501Ω .

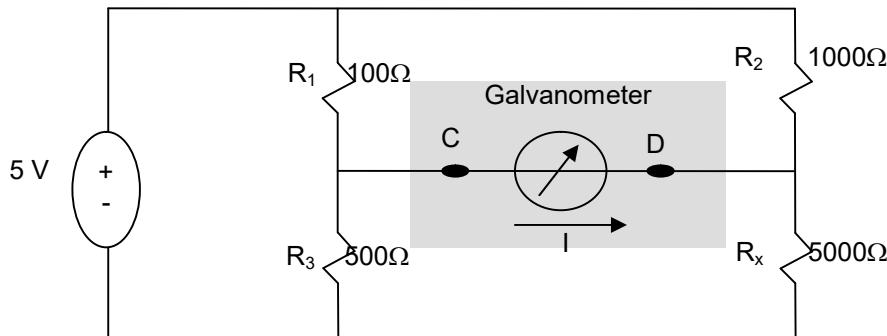Hint: Find the Thevenin equivalent with respect to the galvanometer terminals when $R_3=501\Omega$. Note that once we have found this Thevenin equivalent, it is easy to find the amount of unbalanced current in the galvanometer branch for different galvanometer movements.




Solution:

Given: Balanced $I=0$ when $R_3 = 500 \Omega \rightarrow V_{CD} = 0$; $R_g = 50 \Omega$

Find: I if $R = 501\Omega$

Step 1 – Find Thevenin Equivalent with respect to C and D

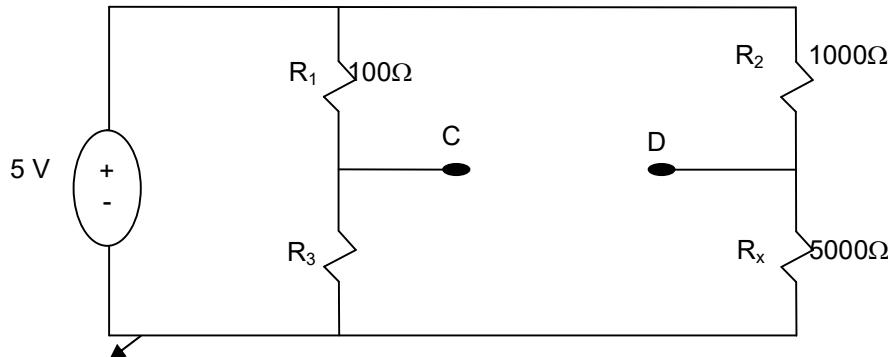A. Open CD and find $V_{open\ CD} = V_{th}$




Use the voltage divider to find V_C and V_D

$$V_C = 5 * R_3 / (R_3 + 100)$$

$$V_D = 5 * 5000 / (5000 + 1000) = 25/6$$


$$V_{th} = V_{CD} = V_C - V_D = 5 * R_3 / (R_3 + 100) - 25/6$$

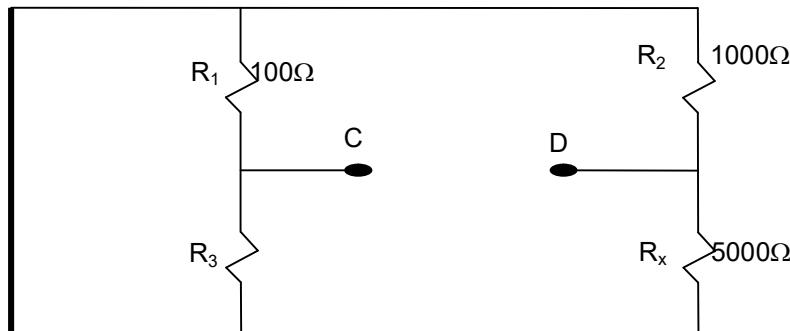B. Deactivate source ($V=0$ short) and find $R_{eq} = R_{th}$



$$R_{CD\text{ eq}} = R_{th} = (100 \parallel R_3) + (1000 \parallel 5000) = 100R_3/(100+R_3) + 5000/6$$

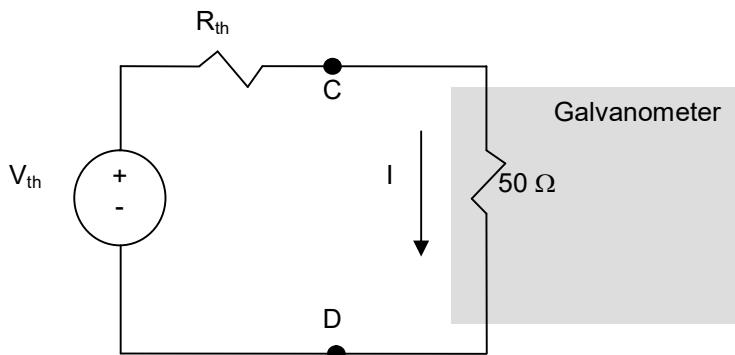
Step 2 – Use Thevenin Equivalent to find current through Galvanometer when $R_3 = 501$



$$I = V_{th} / (R_{th} + 50) = (5 \cdot R_3 / (R_3 + 100) - 25/6) / ((5000/6 + 100R_3/(100+R_3) + 50) \text{ when } R_3 = 501)$$


$$I = 1.43 \mu\text{A}$$

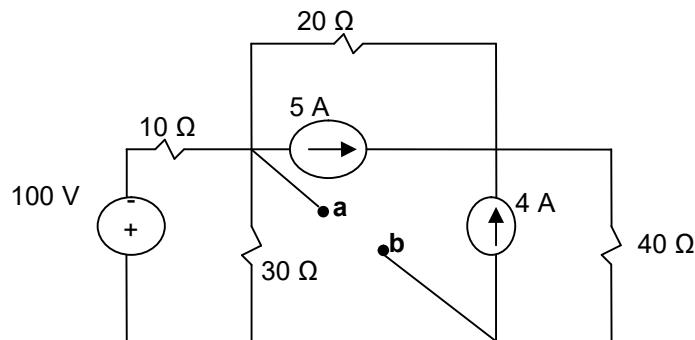11U. Draw and determine the value of components in the Thevenin Equivalent for the following circuit at terminals a and b.




Solution:

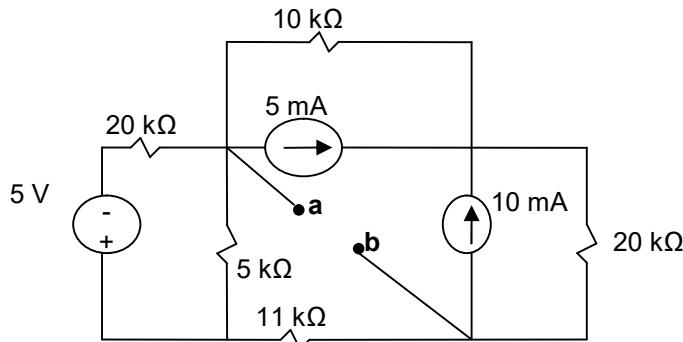11Sb. Draw and determine the value of components in the Thevenin Equivalent for the following circuit with respect to ab terminals. Use Superposition to find V_{th} .



Solution:

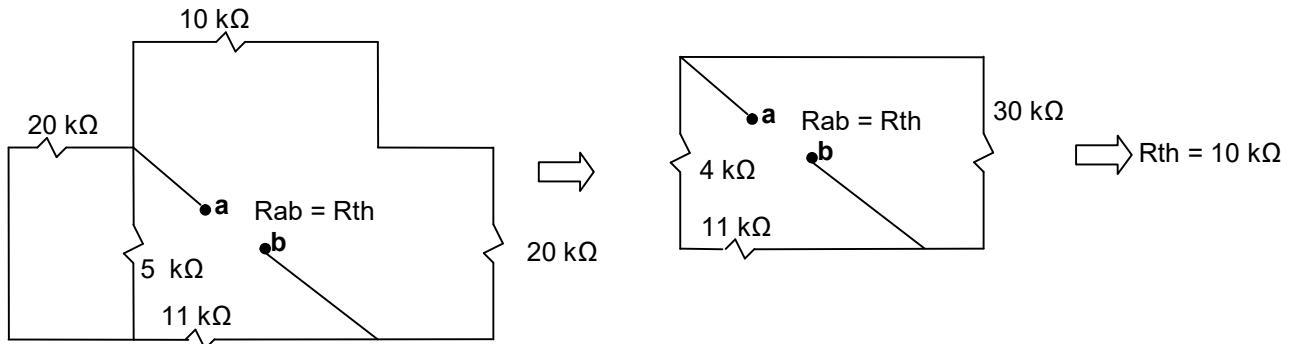
Since sources are all independent sources then deactivate all sources and find R_{th}



Now find Open circuit voltage (V_{th}):

Apply SuperPosition →

Only 5V source is active:

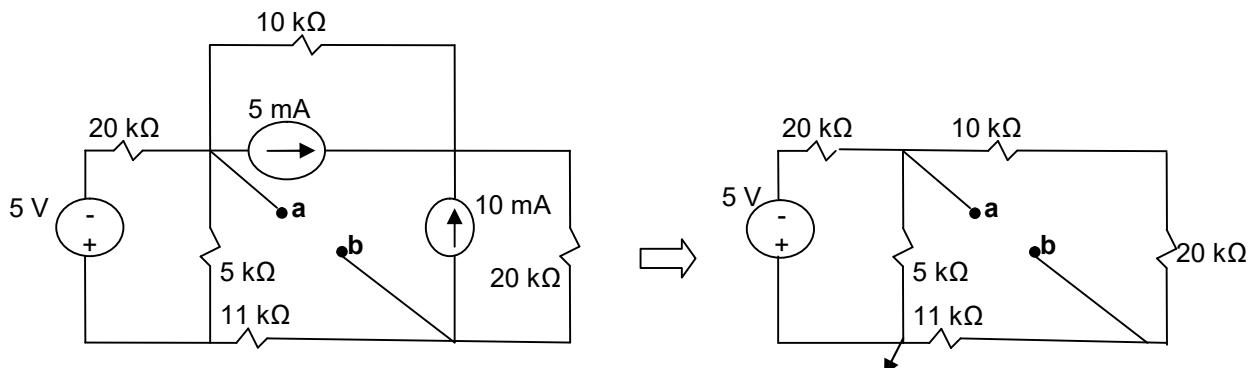


$$(V_a - (-5)) / 20 + (V_a - V_b) / 30 + V_a / 5 = 0 \quad 17 V_a - 2 V_b = -15$$

$$(V_b - V_a) / 30 + V_b / 11 = 0 \quad -11 V_a + 41 V_b = 0$$

$$V_a = -0.9, V_b = -0.2 \rightarrow V_{ab1} = -0.7 \text{ V for } 5\text{v Supply}$$

Only 5 mA source is active

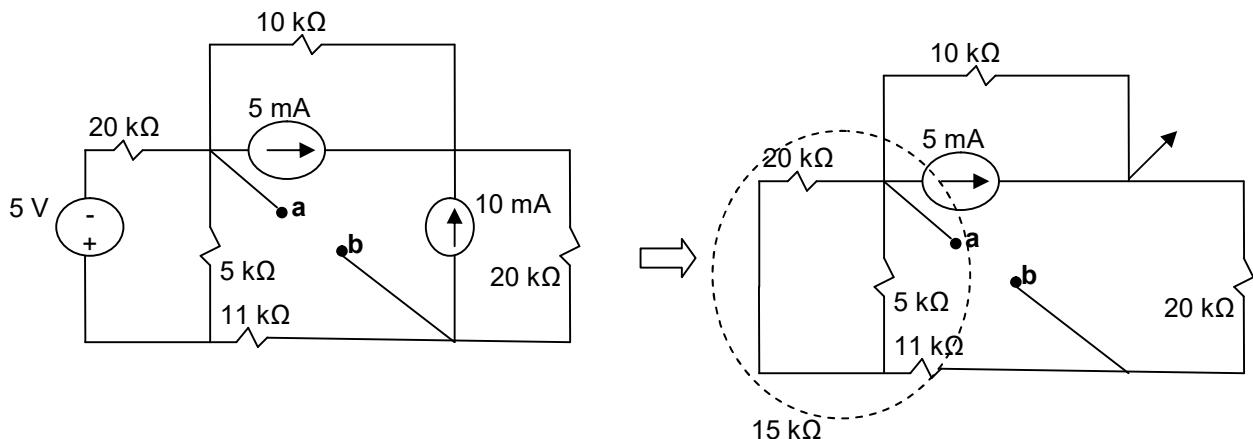


$$(V_a - V_b) / 15 + 5 + V_a / 10 = 0 \rightarrow 5V_a - 2V_b = -150$$

$$(V_b - V_a) / 15 + V_b / 20 = 0 \rightarrow -4V_a + 7V_b = 0$$

$$\text{Solve } \rightarrow V_a = -38.9 \text{ & } V_b = -22.2 \rightarrow V_{ab2} = (-38.9) - (-22.2) = -16.7 \text{ v}$$

Only 10 mA source is active

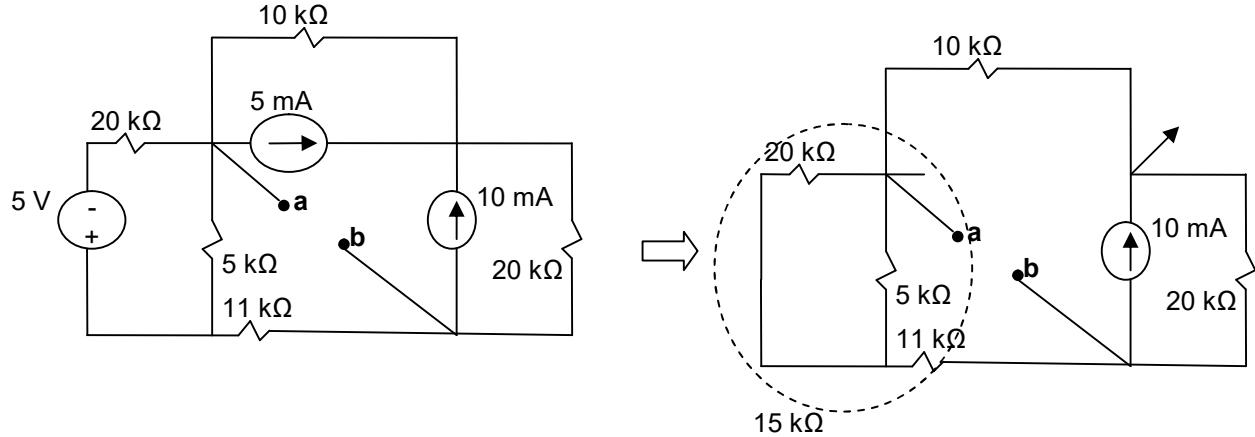


$$(V_a - V_b)/15 + V_a/10 = 0 \rightarrow 5V_a - 2V_b = 0$$


$$(V_b - V_a)/15 + 10 + V_b/20 = 0 \rightarrow -4V_a + 7V_b = -600$$

$$\text{Solve} \rightarrow V_a = -44.4 \text{ & } V_b = -111.1 \rightarrow V_{ab} = (-44.4) - (-111.1) = +66.7\text{v}$$

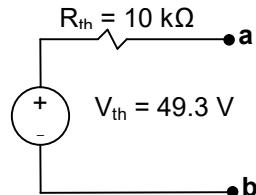Therefore $V_{th} = V_{ab1} + V_{ab2} + V_{ab3} = -0.7 - 16.7 + 66.7 = 49.3\text{ v}$ and $R_{th} = 10\text{ k}\Omega$



11Sc.

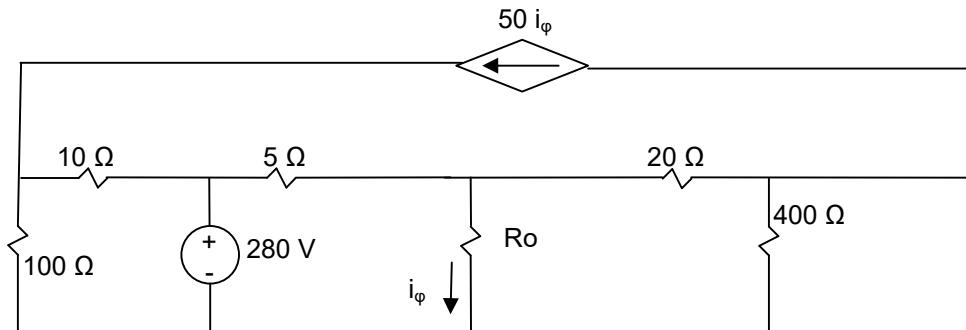


For the above circuit, find the Thevenin equivalent with respect to terminals of R_o .

Solution:

a) Thevenin equivalent

Find V_{oc} (Open Circuit $i_\phi=0$)

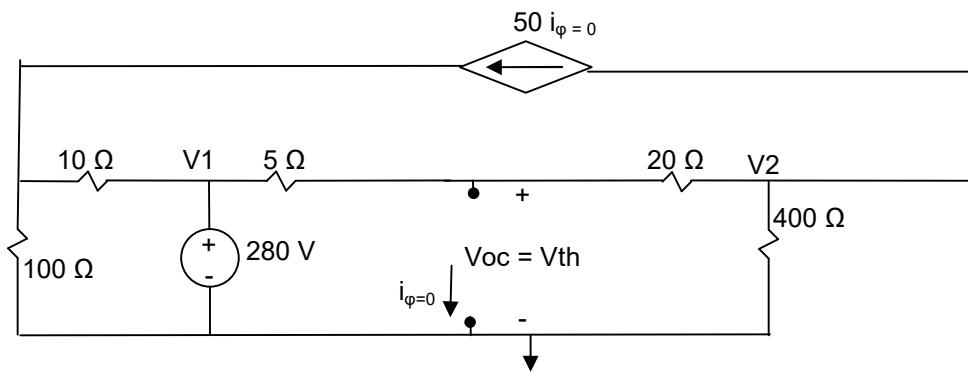

From the circuit:


$$V_1 = 280\text{ V}$$

$$i_{\phi=0} = 0$$

$$\text{KCL at } V_2 \rightarrow (V_2 - 280)/25 + V_2/400 = 0 \rightarrow V_2 = 264\text{ V}$$

$$V_{th} = V_{oc} = V_1 - 5(V_1 - V_2)/25 = 280 - 5(280 - 264)/25 = 277\text{ V}$$

Find I_{sc}

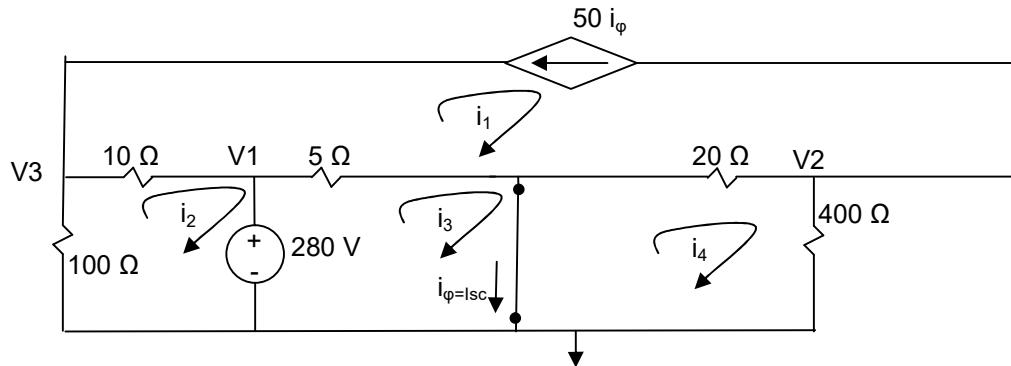

Mesh Current Analysis equations:

$$\begin{aligned} i_1 &= -50 i_\phi = -50(i_3 - i_4) = 50 i_4 - 50 i_3 \\ +280 + 100 i_2 + 10(i_2 - i_1) &= 0 \\ -280 + 5(i_3 - i_1) &= 0 \\ 20(i_4 - i_1) + 400 i_4 &= 0 \end{aligned}$$


Simplify to 4 equations and 4 unknowns:

$$\begin{aligned} i_1 + 50 i_3 - 50 i_4 &= 0 \\ -10i_1 + 110i_2 &= -280 \\ -5i_1 + 5 i_3 &= 280 \\ -20i_1 + 420 i_4 &= 0 \end{aligned}$$

Solve the equations:


$$i_1 = -57.6\text{ A}; i_2 = -7.8\text{ A}; i_3 = -1.6\text{ A}; i_4 = -2.7\text{ A} \rightarrow i_{sc} = i_3 - i_4 = -1.6 - (-2.7) = 1.1\text{ A}$$
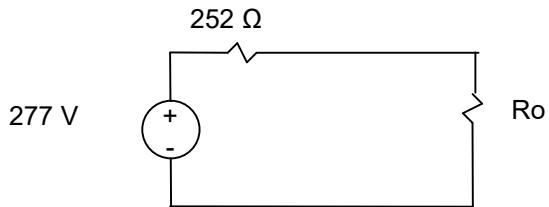
$$R_{th} = V_{oc} / I_{sc} = 277 / 1.1 = 252 \Omega$$



11sd. Using Node-Voltage Method for the following circuit:

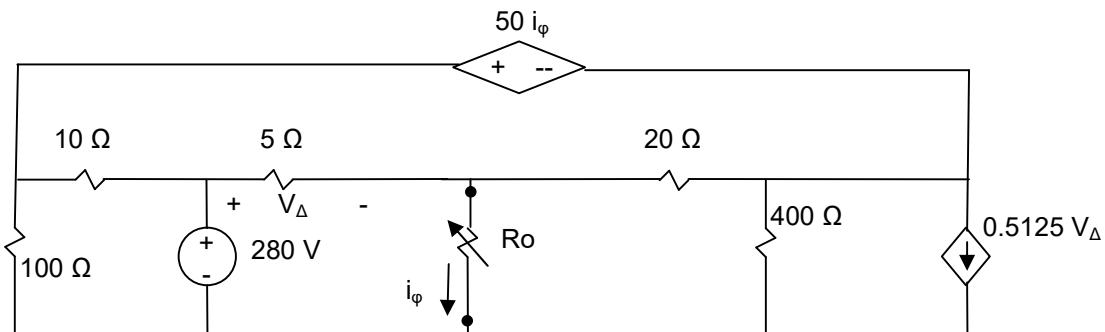
- Find the Thevenin equivalent with respect to terminals of R_o .
- Find the R_o value that results in maximum power delivery to R_o .



Solution

a) Thevenin equivalent

First find V_{oc}

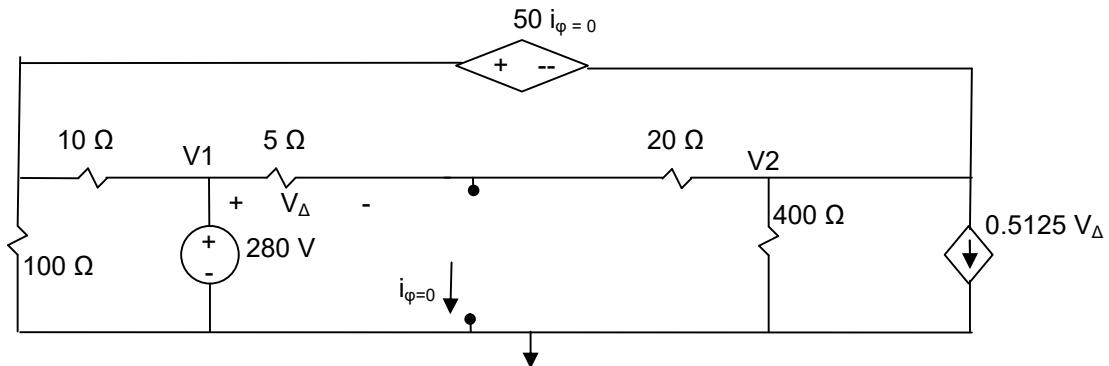

KCL at $V_1=280$ V


$$\text{KCL at } V_2 \rightarrow (V_2 - 280)/25 + V_2/400 + (V_2 - 280)/10 + V_2/100 + 0.5125 V_\Delta = 0 \rightarrow V_2 = 257 \text{ V}$$

$$V_\Delta = (V_1 - V_2)/5 = (280 - 257)/5 = 23/5 = 4.6 \text{ V}$$

$$V_\Delta = (280 - V_2)/5 = (280 - 257)/5 = 23/5 = 4.6 \text{ V}$$

$$V_{oc} = V_{th} = V_1 - V_\Delta = 275.4$$

First find I_{sc}

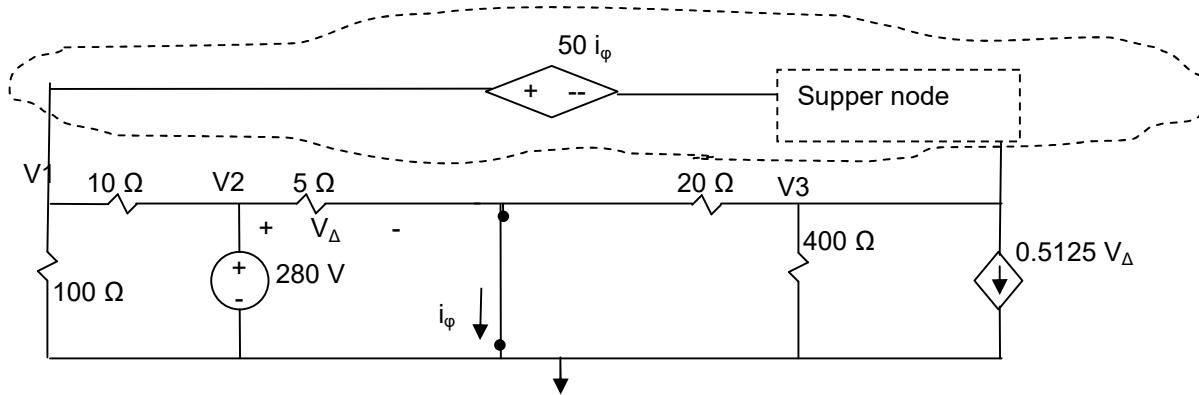

$$\text{KCL at } V_2 = 280 \text{ V} \rightarrow V_2 = V_\Delta = 280 \text{ V}$$

$$i_\phi = (V_2) / 5 + (V_3) / 20$$

$$\text{Supper Node Equation } V_1 - V_3 = 50 i_\phi = (V_2) / 5 + (V_3) / 20 = 10 V_2 + 2.5 V_3 \rightarrow V_1 = 2800 + 3.5 V_3$$


$$\text{KCL at Supper Node} \rightarrow V_3/400 + V_3/20 + 0.5125 V_\Delta + V_1/100 + (V_1 - V_2)/10 = 0$$

Substitute known values \rightarrow


$$V_3/400 + V_3/20 + 0.5125 * 280 + (2800 + 3.5 V_3)/100 + (2800 + 3.5 V_3 - 280)/10 = 0$$

$$\text{Find } V_3 = -945.14 \rightarrow V_1 = -508 \rightarrow I_{sc} = I_\phi = (V_1 - V_3)/30 = 8.7 \text{ A}$$
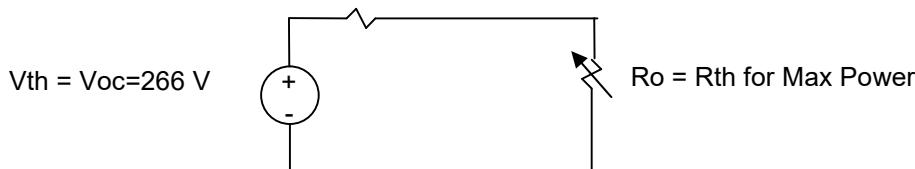
$$R_{th} = V_{oc} / I_{sc} = 275.4 / 8.7 = 31.65 \Omega$$




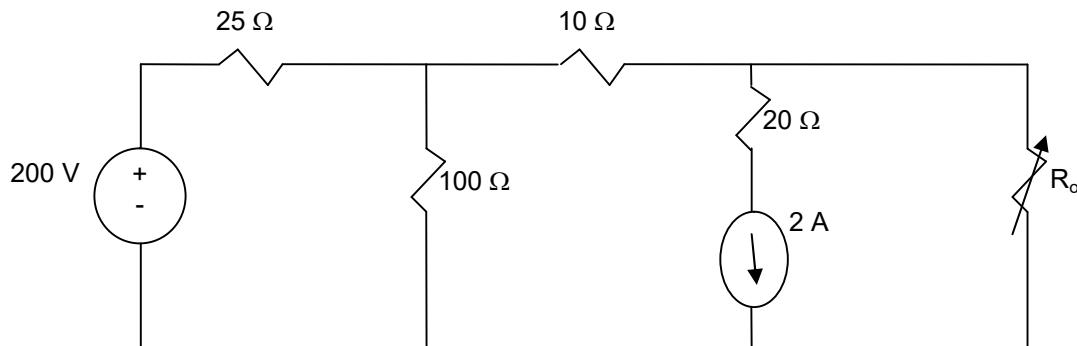- 12S. The variable resistor (R_o) in the following circuit is adjusted until the power dissipated in the resistor is 50 W. Find the values of R_o that satisfy this condition.



Solution:

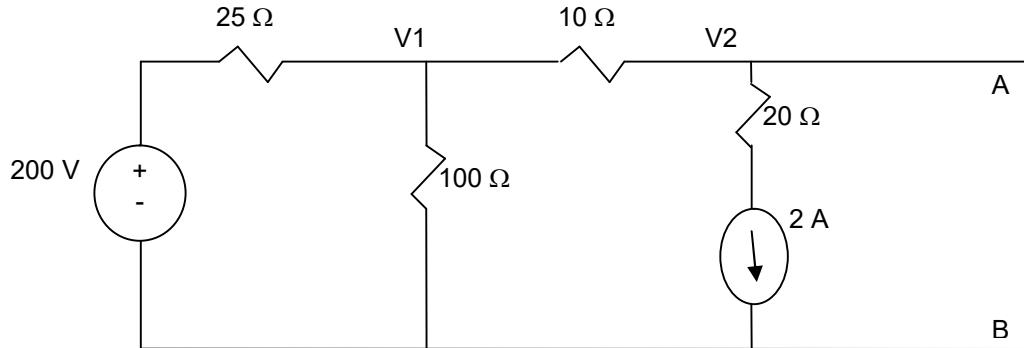1) Find Thevenin equivalent – $V_{oc}=V_{th}$



$$\text{KCL at } V_1 \rightarrow (V_1 - 200)/25 + V_1/100 + (V_1 - V_2)/10 = 0$$

$$\text{KCL at } V_2 \rightarrow 2 + (V_2 - V_1)/10 = 0$$


→

$$15V_1 - 10V_2 = 800$$


$$V_1 - V_2 = 20$$

$$\rightarrow V_{th} = V_{oc} = V_2 = 100 \text{ V}$$

2) Deactivate Sources to find R_{th}

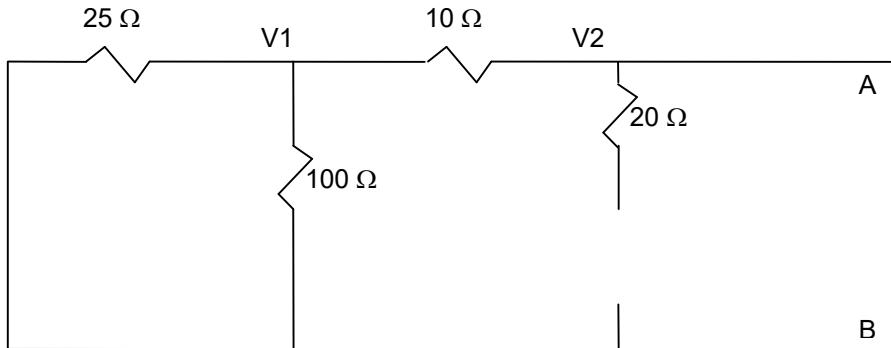
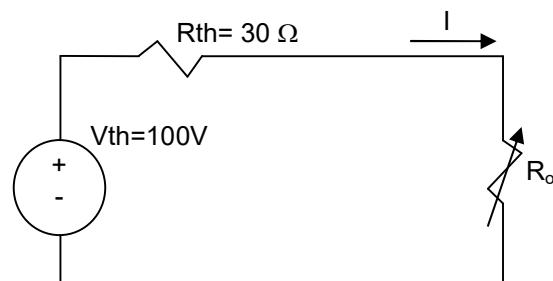
$$R_{th} = (25 \parallel 100) + 10 = 30 \Omega$$




$$P_{Ro} = 50 \text{ W} \rightarrow 50 = I^2 R_o \rightarrow R_o = 50/I^2$$

$$\text{KVL} \rightarrow -100 + 30I + I R_o = 0 \quad \rightarrow -100 + 30I + 50/I = 0 \quad \rightarrow 30I^2 - 100I + 50 = 0$$

$$I = \frac{100 \pm \sqrt{10,000 - 6,000}}{60} = \frac{100 \pm 200}{60} = 5A \quad \text{or} \quad -1.67A$$


$$R_o = 50/I^2 = 2\Omega \text{ or } 18\Omega$$

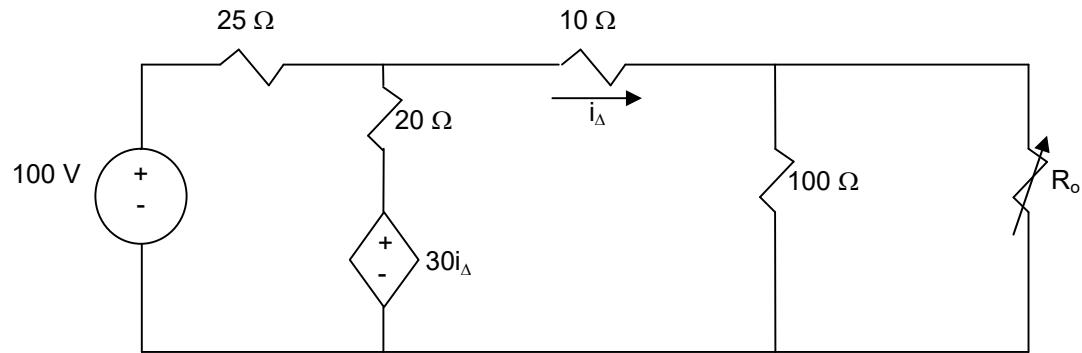12U. The variable resistor (R_o) in the following circuit is adjusted until the power dissipated in the resistor is 25 W. Find the values of R_o that satisfy this condition.




Solution:

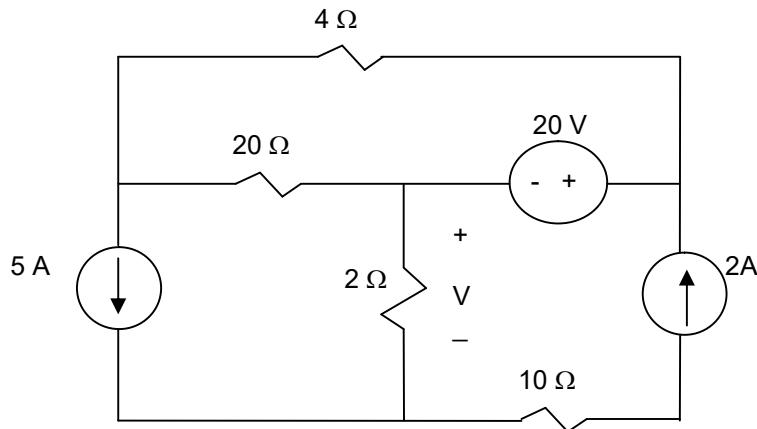13S. Use the principle of superposition to find the voltage v in the following circuit.




Solution:

1) Activate only 2A source

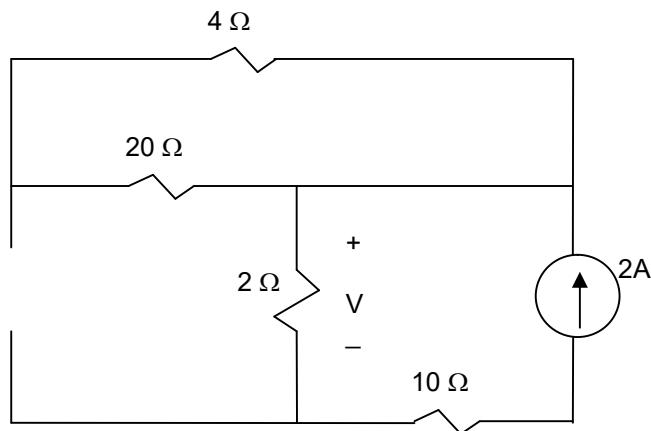


$$V_{2A} = 2 \times 2 = 4V$$

2) Activate only 5A source

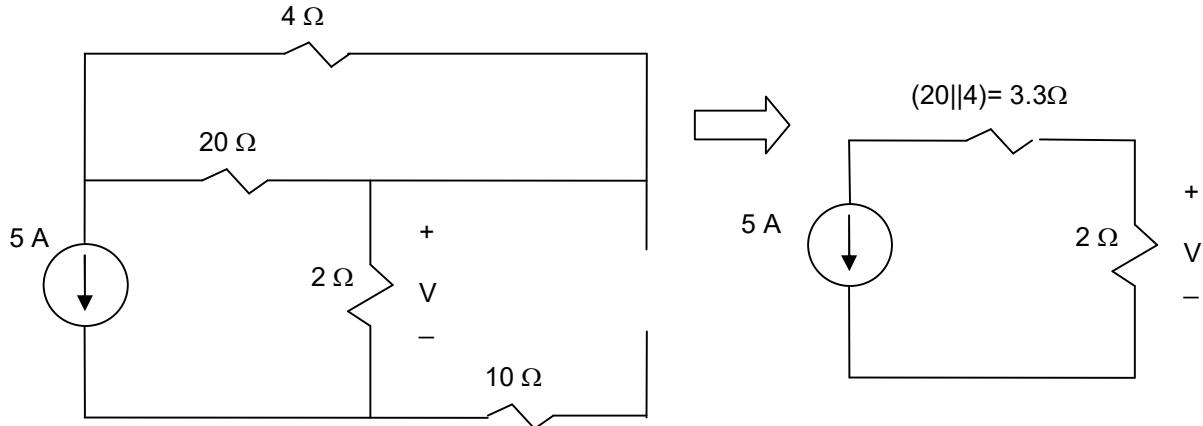

$$V_{5A} = -5 \times 2 = -10V$$


3) Activate only 20V source

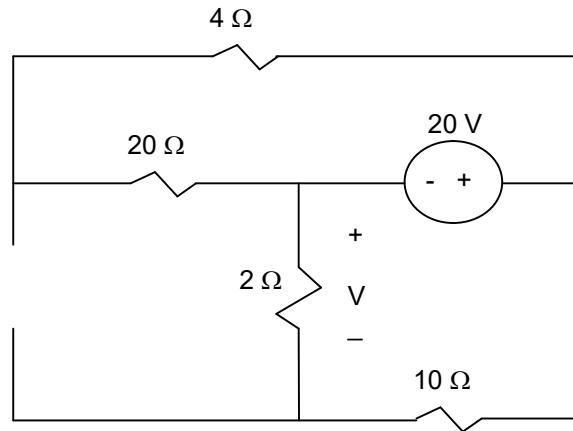

$$V_{20V} = 0$$


$$\text{Total response, } V = V_{2A} + V_{5A} + V_{20V} = 4 - 10 + 0 = -6V$$

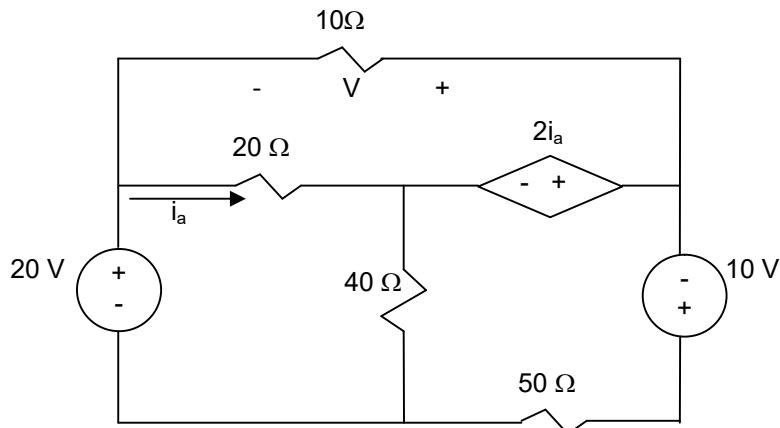13U. Use the principle of superposition to find the voltage V in the following circuit.




Solution:

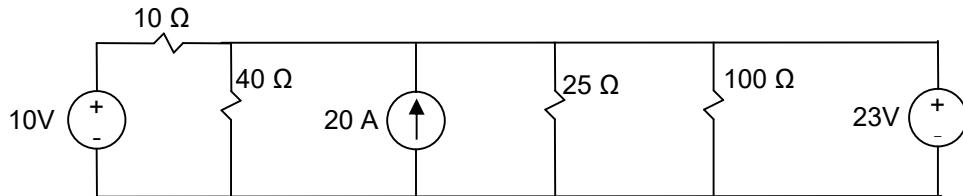13Sb. What is the value of current through $40\ \Omega$ resistor that is directly attributable to the 10 V voltage source.




Solution:

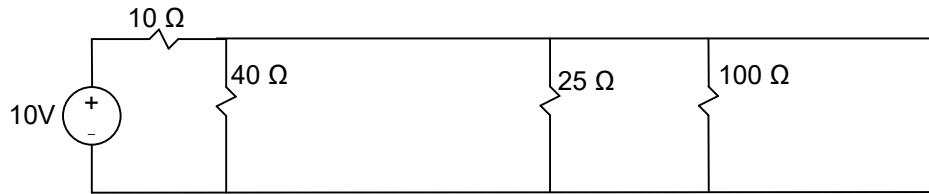- De-activate all the sources except the 10 v




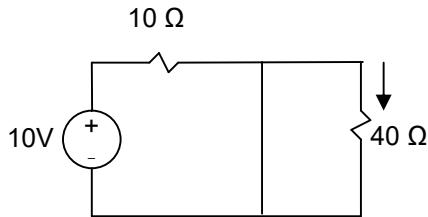- Simplify and find the current resulting from the 10 v supply.



Current through the $40\ \Omega$ is zero since all the current goes through the short.

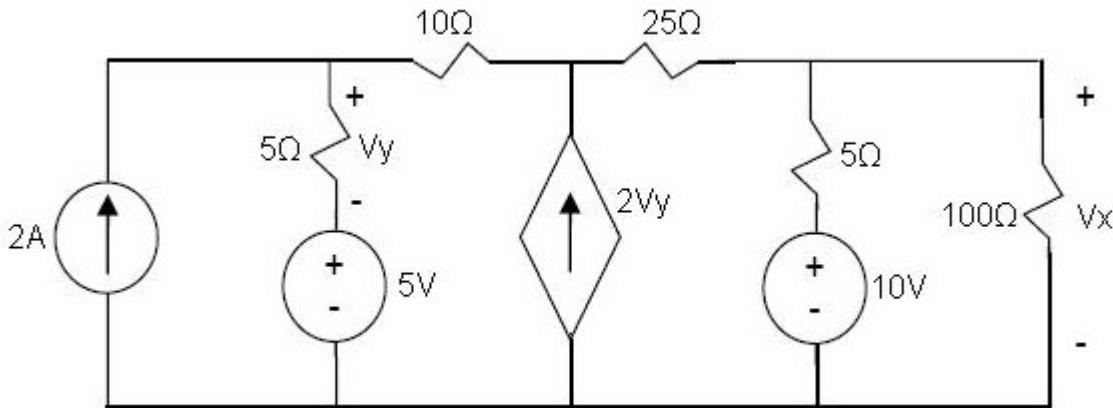
13Sc Use the Super-Position principle to find V_x in the following circuit.



Solution:

Deactivate all independent sources.

Activate 2 A source and redraw:

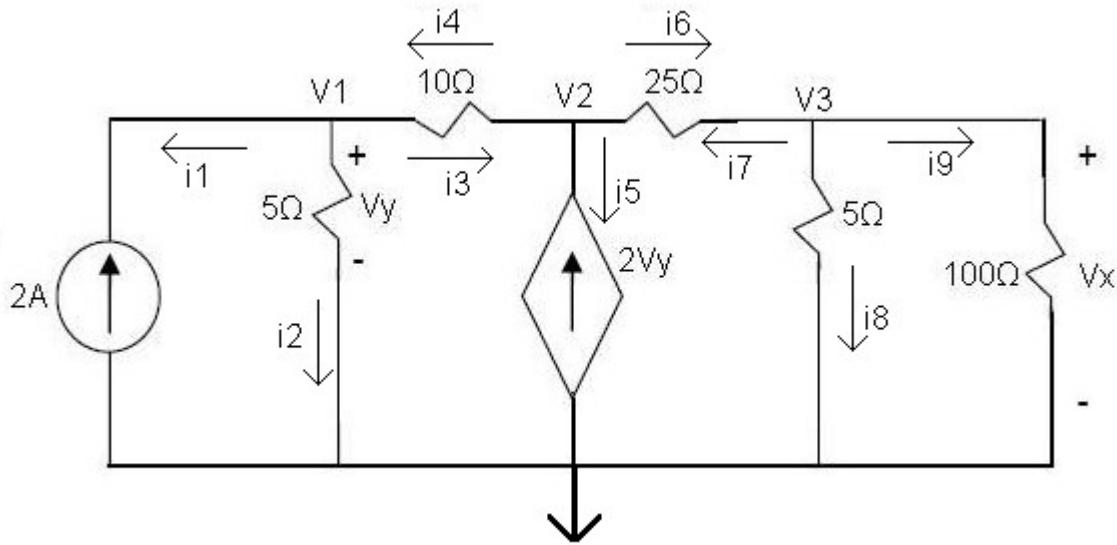

Use KCL to find V_x .

$$\begin{aligned} \text{KCL @ } V_1 &\rightarrow i_1 + i_2 + i_3 = 0 \\ &\rightarrow -2 + V_1 / 5 + (V_1 - V_2) / 10 = 0 \end{aligned}$$

$$\begin{aligned} \text{KCL @ } V_2 &\rightarrow i_4 + i_5 + i_6 = 0 \\ &\rightarrow (V_2 - V_1) / 10 + (-2V_y) + (V_2 - V_3) / 25 = 0 \end{aligned}$$

$$\begin{aligned} \text{KCL @ } V_3 &\rightarrow i_7 + i_8 + i_9 = 0 \\ &\rightarrow (V_3 - V_2) / 25 + V_3 / 5 + V_3 / 100 = 0 \end{aligned}$$


Dependent equation: $V_y = V_1 / 5$

Simplify and solve.

$$\begin{aligned} (3/10)V_1 - (1/10)V_2 &= 2 \\ (3.5/25)V_2 - (1/2)V_1 - (1/25)V_3 &= 0 \\ (1/4)V_3 - (1/25)V_2 &= 0 \end{aligned}$$

$$V_3 = V_x = -20.1V$$

Activate 5V source and redraw:

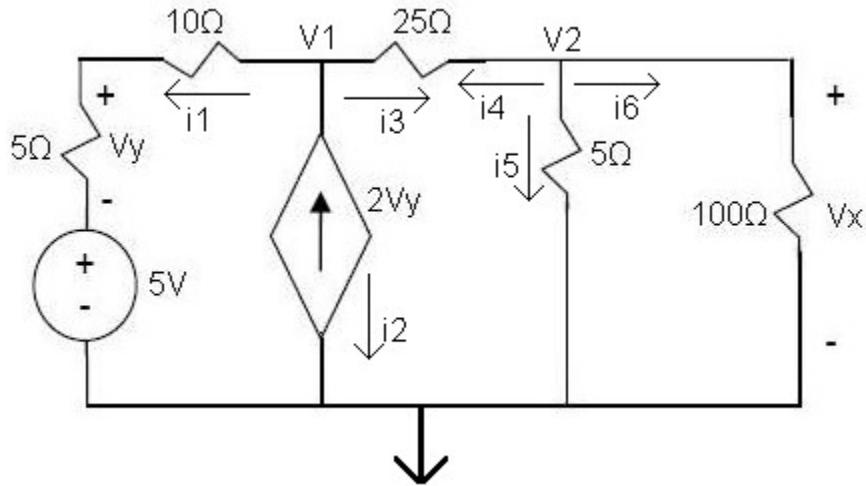

Use KCL to find V_x .

$$\begin{aligned} \text{KCL @ } V_1 &\rightarrow I_1 + I_2 + I_3 = 0 \\ &\rightarrow (V_1 - 5) / (10 + 5) + (-2*V_y) + (V_1 - V_2) / 25 = 0 \end{aligned}$$

$$\begin{aligned} \text{KCL @ } V_2 &\rightarrow I_4 + I_5 + I_6 = 0 \\ &\rightarrow (V_2 - V_1) / 25 + V_2 / 5 + V_2 / 100 = 0 \end{aligned}$$


$$\text{Dependent equation: } V_y = (V_1 - 5) / 3$$

Simplify and solve.

$$\begin{aligned} (-48 / 75)*V_1 - (V_2 / 25) + 3 &= 0 \\ (V_2 / 4) - (V_1 / 25) &= 0 \end{aligned}$$

$$V_2 = V_{x_2} = 0.743V$$

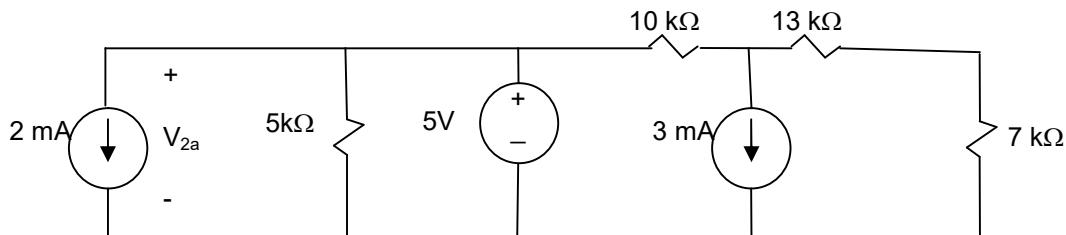
13Sc. Use the principle of superposition to find voltage V_{2a} in the following circuit:



Solution:


Deactivate all except 2 mA

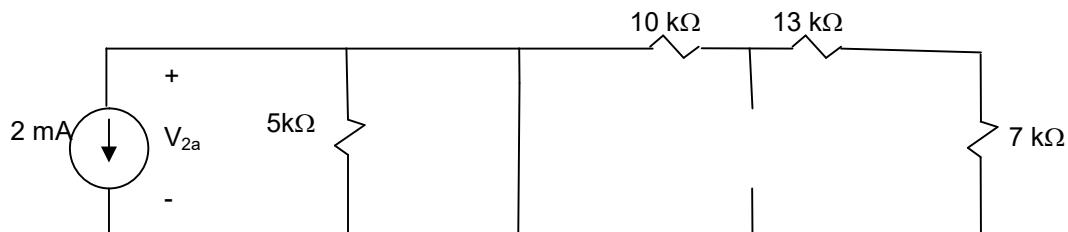Note: Voltage source deactivates when $V=0 \rightarrow$ short; Current source deactivates when $I=0 \rightarrow$ Open




$$R_{eq} = 0 \text{ k}\Omega \rightarrow V_{2a} = 0 \text{ V}$$

Deactivate all except 5V

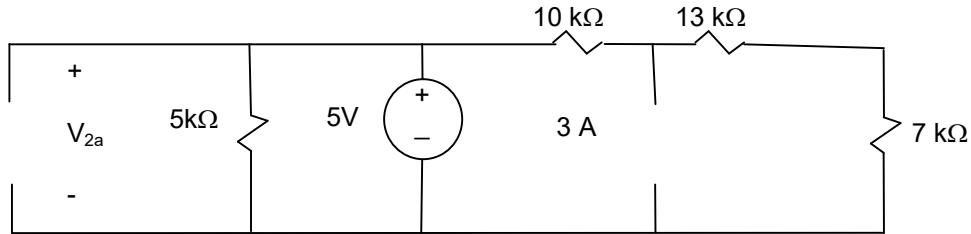

$$V_{2a} = + 5 \text{ V}$$


Deactivate all except 3 mA

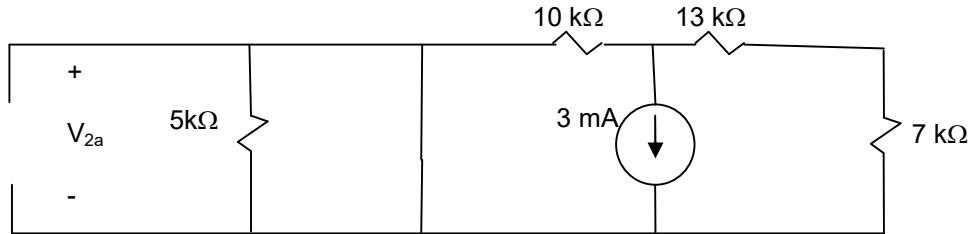

$$R_{eq} = 0 \text{ k}\Omega \rightarrow V_{2a} = 0 \text{ V}$$


Super positioned input (total Response) = $0 + 5 + 0 = 5\text{V}$.

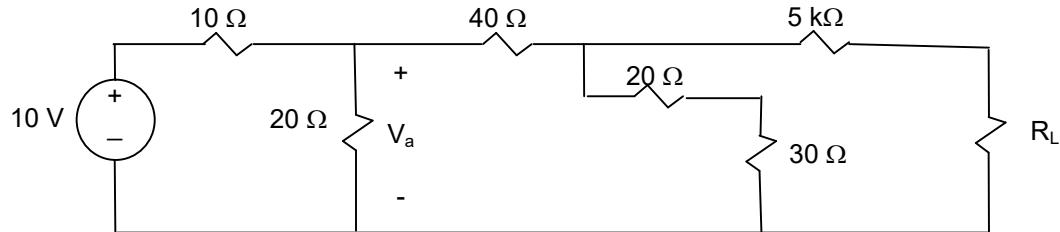14S. In the following circuit, find R_L value such that R_L consumes maximum power.



Solution:

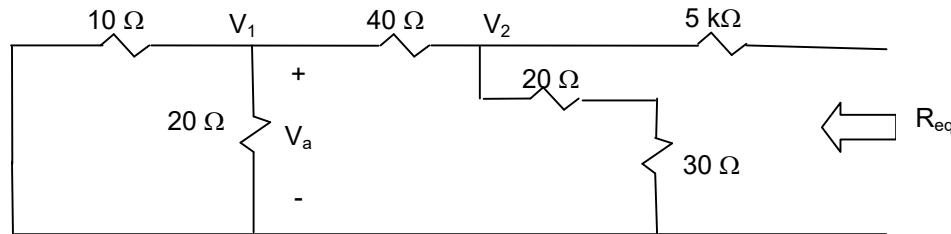
1) Find R_{th} by Deactivating source ($v=0$ or open)



$$R_{eq} = (((10 \parallel 20) + 40) \parallel (20 + 30)) + 5000 = 5024.15 \text{ }\Omega$$

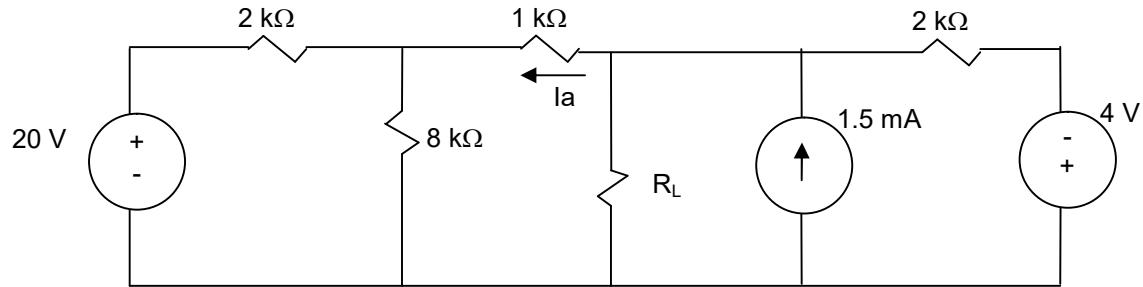2) Maximum power Requires $R_L = R_{th} = 5024.15 \text{ }\Omega$


14U. In the following circuit, find R_L value such that R_L consumes maximum power..



Hint: Find R_{th} with respect to R_L terminals First.


Solution:

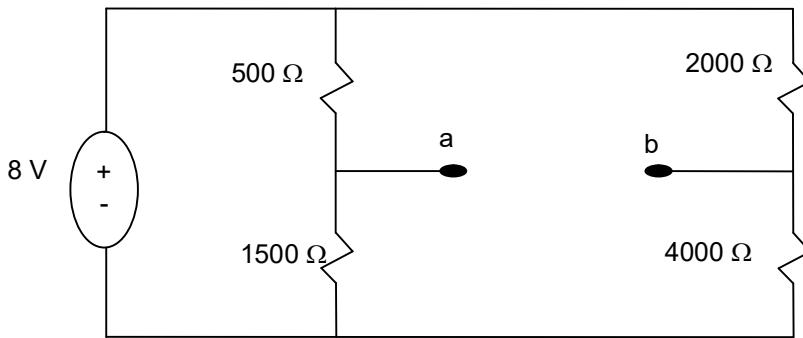14Sb. Find value of a resistor between terminals a and b such that it would consume maximum power:



Solution:

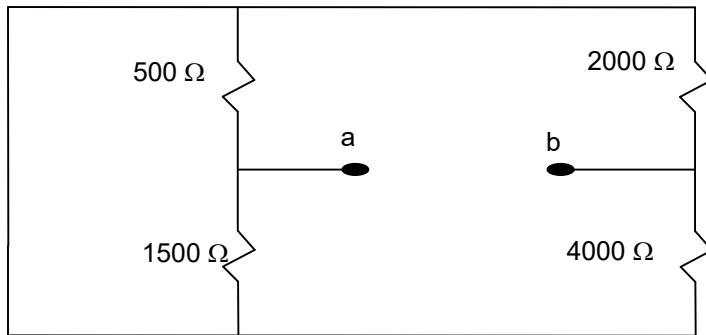Find R_{th} with respect to terminals a and b by deactivating the independent voltage source



$$R_{th} = (500 \parallel 1500) + (2000 \parallel 4000) = 1708 \Omega$$

For Maximum power, R_{ab} must be equal to R_{th} or 1708Ω