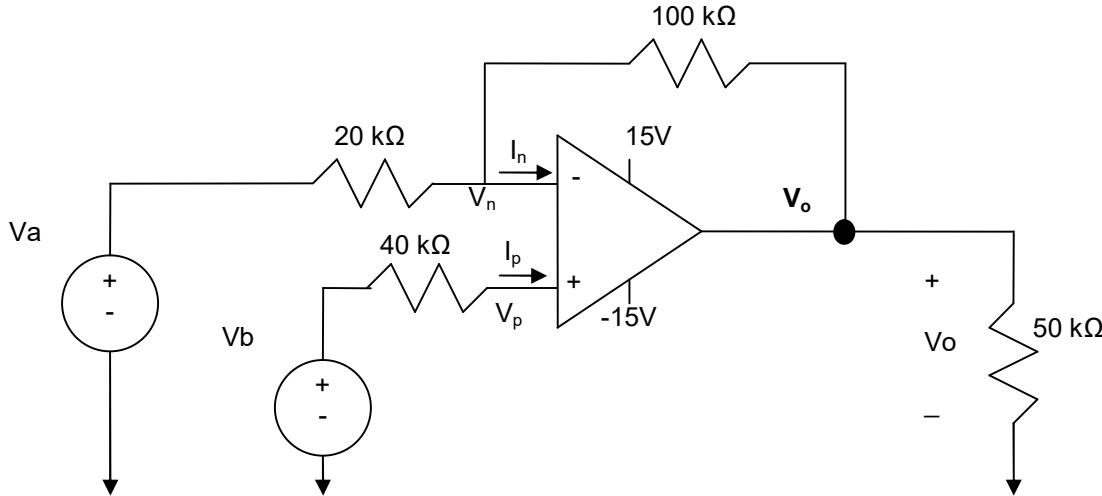


# Fundamentals of Electrical Circuits - Chapter 5

1S. The Op Amp in the circuit shown below is ideal.

- Calculate  $V_o$  if  $V_a = 4 \text{ V}$  and  $V_b = 0 \text{ V}$ .
- Calculate  $V_o$  if  $V_a = 2 \text{ V}$  and  $V_b = 0 \text{ V}$ .
- Calculate  $V_o$  if  $V_a = 2 \text{ V}$  and  $V_b = 1 \text{ V}$ .
- Calculate  $V_o$  if  $V_a = 1 \text{ V}$  and  $V_b = 2 \text{ V}$ .
- If  $V_b = 1.6 \text{ V}$ , specify the range of  $V_a$  such that the amplifier does not saturate.



**Solution:**

a, b, c and d)

$$\text{KCL at Node } V_n \rightarrow \frac{V_n - V_a}{20} + \frac{V_n - V_o}{100} = 0$$

$$\text{Ideal Op Amp} \rightarrow I_p = I_n = 0 \rightarrow V_n = V_p = V_b$$

$$\text{Apply to KCL equation} \rightarrow \frac{V_n - V_a}{20} + \frac{V_n - V_o}{100} = 0 \rightarrow \frac{V_b - V_a}{20} + \frac{V_b - V_o}{100} = 0$$

$$\rightarrow V_o = 6V_b - 5V_a$$

Use the above relationship to answer the problem parts a, b, c and d. Note that calculated value of  $V_o$  must be limited by the  $V_{CC}$  limits (-15 and +15)

Part	$V_a (\text{V})$	$V_b (\text{V})$	$V_o (\text{V})$	Comment
a	4	0	-20	$V_o$ will be limited to -15V due to saturation
b	2	0	-10	Linear Region
c	2	1	-4	Linear Region
d	1	2	7	Linear Region

e)


In order for the Op Amp not to saturate its output must satisfy  $-15 \leq V_o \leq 15$   
given  $V_b = 1.6 \text{ V}$

$$\rightarrow -15 \leq 6V_b - 5V_a \leq 15 \rightarrow -1.08 \leq V_a \leq 4.92$$

1U. The Op Amp in the circuit shown below is ideal.


- Calculate  $V_o$  if  $V_a = 2 \text{ mV}$  and  $V_b = 0 \text{ V}$ .
- Calculate  $V_o$  if  $V_a = 100 \text{ mV}$  and  $V_b = 20 \text{ mV}$ .

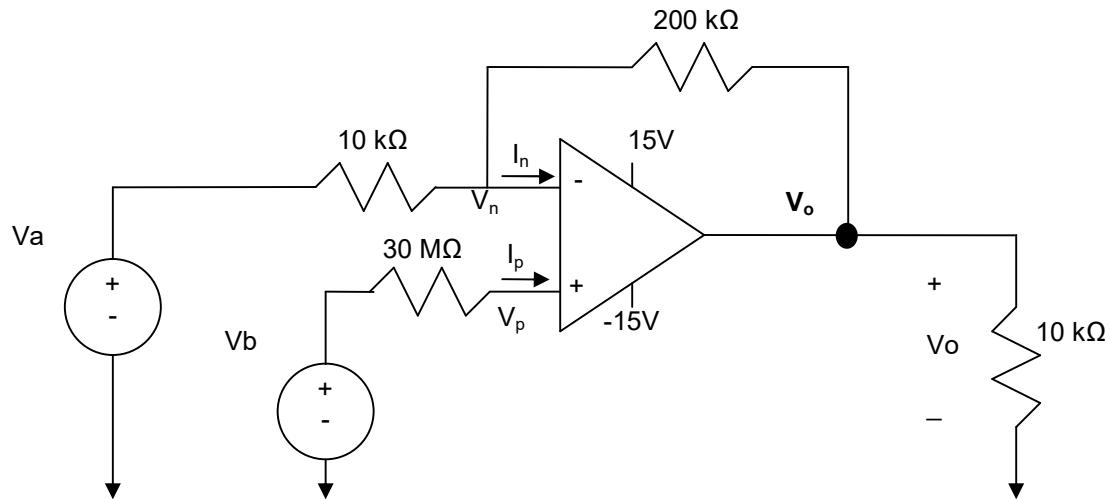- c) Calculate  $V_o$  if  $V_a = 2 \text{ V}$  and  $V_b = 1 \text{ V}$ .  
d) Calculate  $V_o$  if  $V_a = 2 \text{ V}$  and  $V_b = 2.1 \text{ V}$ .  
e) If  $V_b = 1.2 \text{ V}$ , specify the range of  $V_a$  such that the amplifier does not saturate.




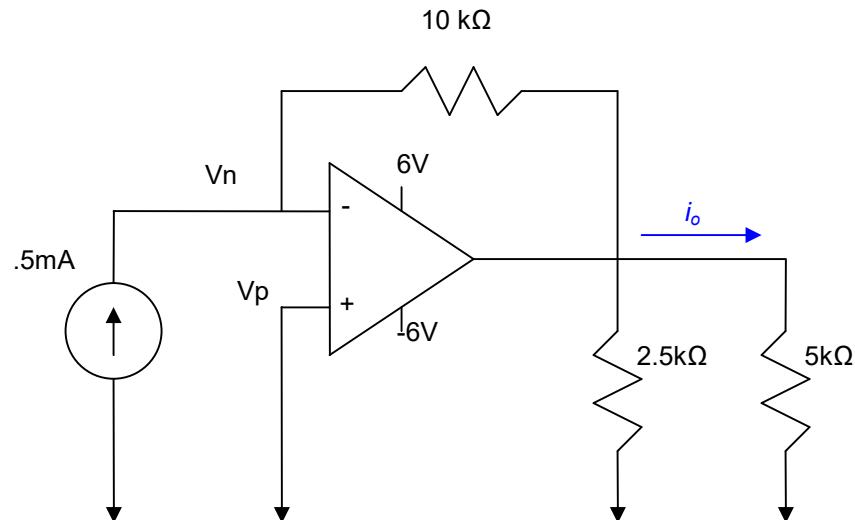**Solution:**

2S. Find  $i_o$  in the following circuit if the Op Amp is ideal



**Solution:**

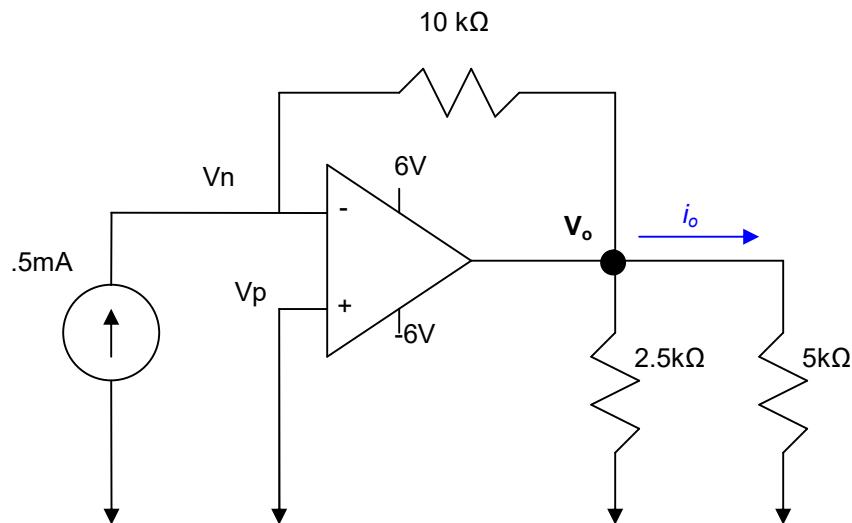


$$KCL \text{ at Node } V_n \rightarrow -0.5 + \frac{V_n - V_o}{10} = 0$$

Ideal Op Amp  $\rightarrow I_p = I_n = 0 \rightarrow V_n = V_p = 0$

Apply to KCL equation  $\rightarrow V_o = -5 V$

$$\rightarrow I_o = \frac{V_o}{R} = \frac{-5}{5} = -1 \text{ mA}$$

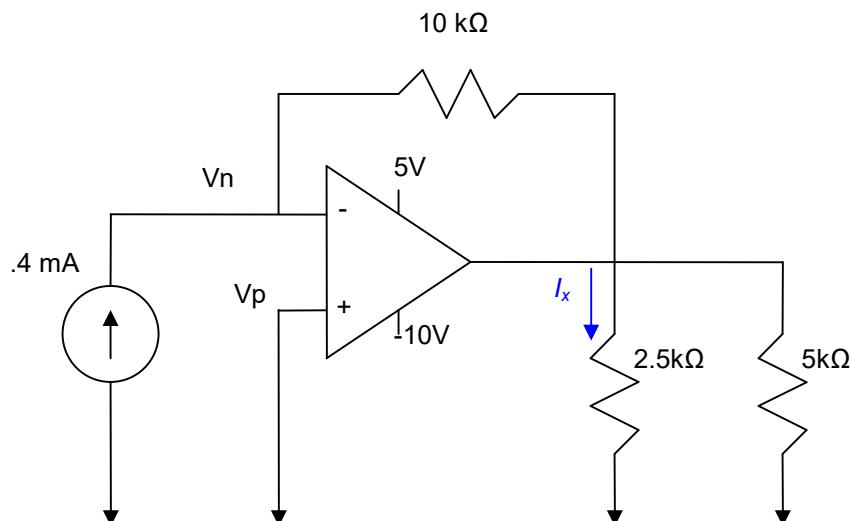2U. Find  $I_x$  in the following circuit if the Op Amp is ideal




**Solution:**

3S. The Op Amp in the following circuit is ideal

- a) What Op Amp circuit configuration is this?

b) Calculate  $V_o$

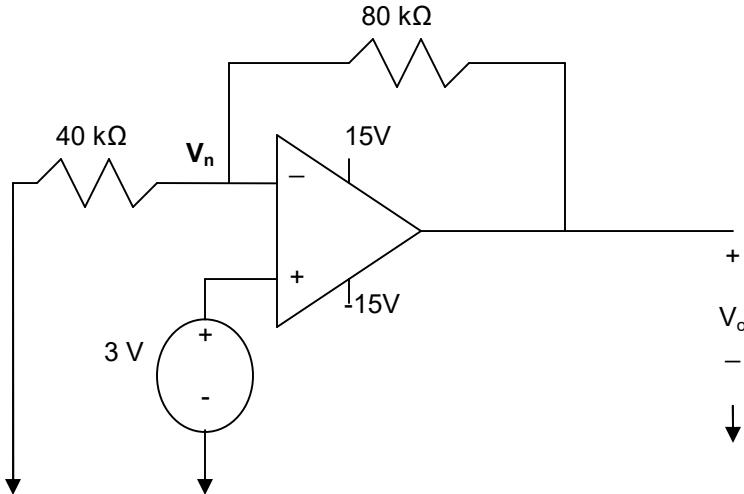

**Solution:**

a) non-Inverting amplifier – Source is connected to positive input terminal

b)  $V_o = ?$


$$KCL \text{ at Node } V_n \rightarrow \frac{V_n}{40} + \frac{V_n - V_o}{80} = 0$$

$$\text{Ideal Op Amp} \rightarrow I_p = I_n = 0 \rightarrow V_n = V_p = 3$$

$$\text{Apply to KCL equation} \rightarrow \frac{3}{40} + \frac{3 - V_o}{80} = 0 \rightarrow V_o = 9 \text{ V}$$

3U. The Op Amp in the following circuit is ideal

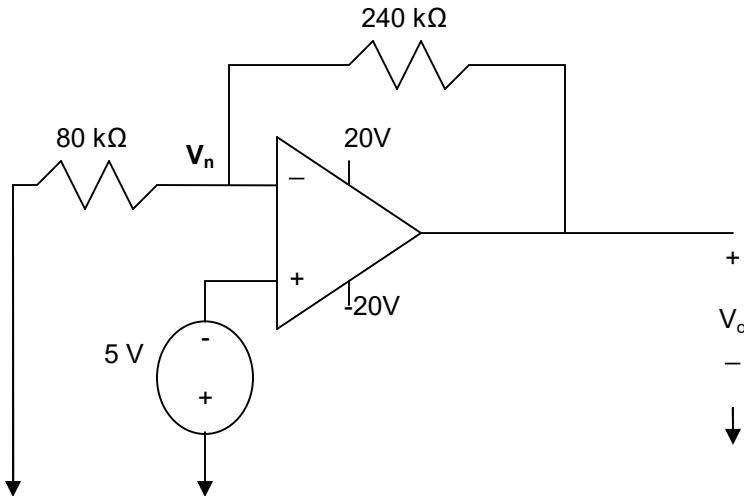- a) What Op Amp circuit configuration is this?
- b) Calculate  $V_o$




**Solution:**

4S. The Op Amp in the following figure is ideal.

- a) What circuit configuration is shown in the figure?
- b) Find  $V_o$  if  $V_a = 1.2 \text{ V}$ ,  $V_b = -1.5 \text{ V}$  and  $V_c = 4 \text{ V}$ .
- c) The voltage  $V_a$  and  $V_c$  remain at 1.2 V and 4 V, respectively. What are the limits on  $V_b$  if the Op Amp

operates within its linear region?

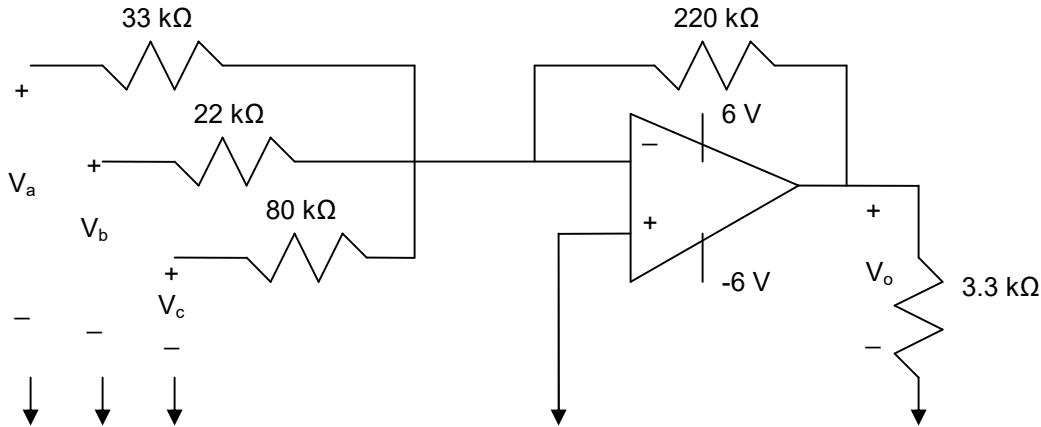

**Solution:**

a) Inverting summing amplifier – Multiple sources are connected to negative input terminal

b) Find  $V_o$ ?

$$KCL \text{ at Node } V_n \rightarrow \frac{V_n - V_a}{33} + \frac{V_n - V_b}{22} + \frac{V_n - V_c}{80} + \frac{V_n - V_o}{220} = 0$$

$$\text{Ideal Op Amp} \rightarrow I_p = I_n = 0 \rightarrow V_n = V_p = 0$$

$$\text{Apply to KCL equation} \rightarrow -\frac{V_a}{33} - \frac{V_b}{22} - \frac{V_c}{80} - \frac{V_o}{220} = 0 \rightarrow V_o = -220 \left( \frac{V_a}{33} + \frac{V_b}{22} + \frac{V_c}{80} \right)$$

$$V_o = -4 \text{ V}$$

c) Limits of  $V_b$  if  $V_a$  and  $V_c$  remain unchanged

We can rewrite  $V_o$  and set it to  $V_{CC}$  limit to ensure linearity

$$-6 \leq V_o \leq 6$$

$$-6 \leq -220(+1.2/33 + V_b/22 + 4/80) \leq 6$$

$$-6 \leq -10V_b - 19 \leq 6$$


$$-2.5 \leq V_b \leq -1.3$$

4U. The Op Amp in the following figure is ideal.

a) What circuit configuration is shown in the figure?

b) Find  $V_o$  if  $V_a = 2 \text{ V}$ ,  $V_b = -2 \text{ V}$  and  $V_c = 4 \text{ V}$ .

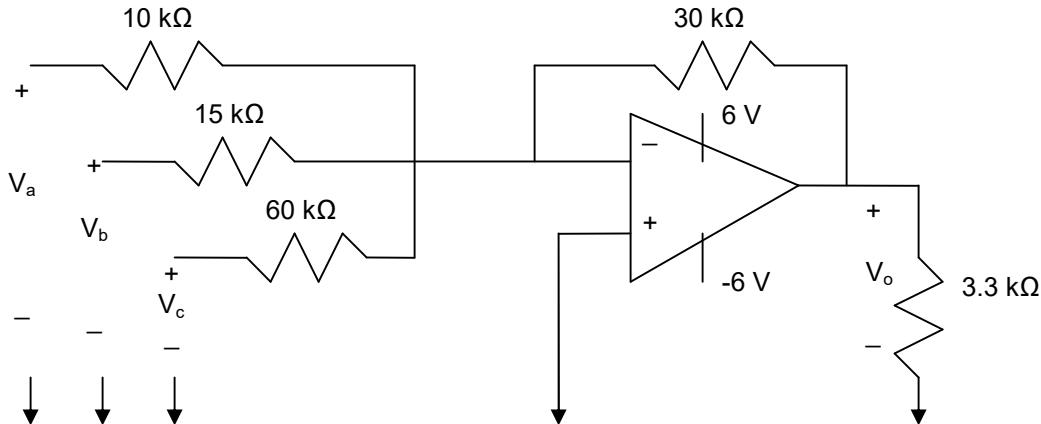
c) The voltage  $V_a$  and  $V_c$  remain at 2 V and 4 V, respectively. What are the limits on  $V_b$  if the Op Amp operates within its linear region?



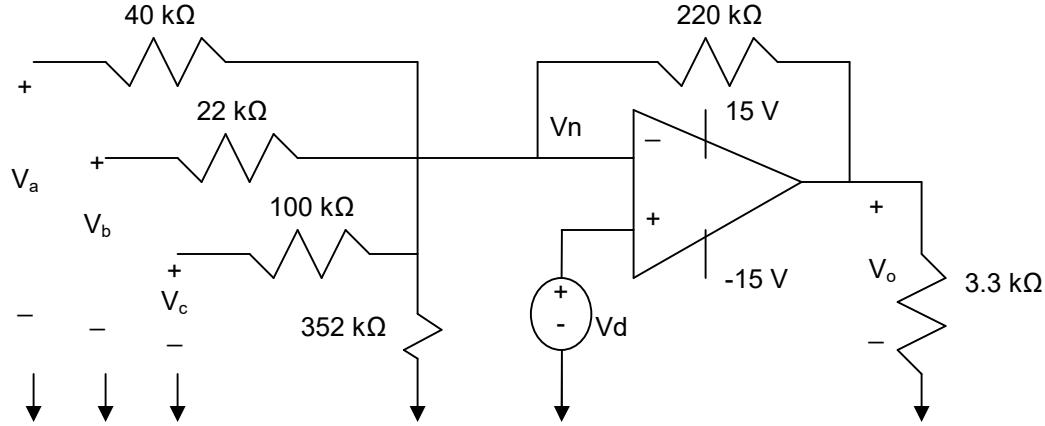**Solution:**

4Sb.

- The Op Amp in the following circuit is ideal. Find  $V_o$  if  $V_a=4V$ ,  $V_b=9V$ ,  $V_c=13V$  and  $V_d=8V$ .
- Assume  $V_b$ ,  $V_c$ ,  $V_d$  retain their values from part (a). Specify the range  $V_a$  such that the Op Amp operates within its linear region.



**Solution:**

- Find  $V_o$  where  $V_a=4V$ ,  $V_b=9V$ ,  $V_c=13V$ ,  $V_d=8V$

$$KCL \text{ at Node } V_n \rightarrow \frac{V_n - V_a}{40} + \frac{V_n - V_b}{22} + \frac{V_n - V_c}{100} + \frac{V_n}{352} + \frac{V_n - V_o}{220} = 0$$

$$\text{Ideal Op Amp} \rightarrow I_p = I_n = 0 \rightarrow V_n = V_p = 8$$

$$\text{Apply to KCL equation} \rightarrow \frac{8-4}{40} + \frac{8-9}{22} + \frac{8-13}{100} + \frac{8}{352} + \frac{8-V_o}{220} = 0$$

$$V_o = 14V$$

- Range of  $V_a$  so Op Amp is in linear region if all else stay the same as (a)

We can rewrite  $V_o$  in term of  $V_a$  and set it to  $V_{CC}$  limit to ensure linearity

$$\frac{8-V_a}{40} + \frac{8-9}{22} + \frac{8-13}{100} + \frac{8}{352} + \frac{8-V_o}{220} = 0$$


$$V_o = 36 - 5.5V_a$$

$$-15 \leq V_o = 36 - 5.5V_a \leq 15 \quad \text{for linearity}$$

$$3.8 \leq V_a \leq 9.3$$

5S. The Op Amp in the following circuit is ideal.

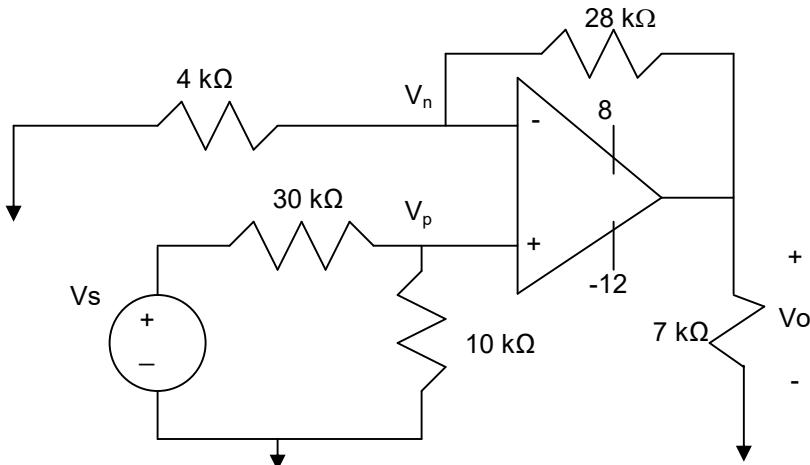- What Op Amp circuit configuration is this?
- Find  $V_o$  in term of  $V_s$ .
- Find the range of values for  $V_s$  such that  $V_o$  does not saturate and the Op Amp remains in its linear region of operation.



**Solution:**

a) Non-inverting, source is connected to positive input terminal

b) Find  $V_o$  in-terms of  $V_s$

$$KCL \text{ at Node } V_n \rightarrow \frac{V_n}{4} + \frac{V_n - V_o}{28} = 0$$

$$\text{Ideal Op Amp} \rightarrow I_p = I_n = 0 \rightarrow V_n = V_p$$

$$\text{Voltage-divider} \rightarrow V_p = \left( \frac{V_s}{30+10} \right) * 10 = \frac{V_s}{4} = V_n$$


$$\text{Apply to KCL equation} \rightarrow \frac{V_s}{16} + \frac{\frac{V_s}{4} - V_o}{28} = 0 \rightarrow V_o = 2V_s$$

c) Range of  $V_s$  so Op Amp is in linear region (not saturated)

$$-12 \leq V_o = 2V_s \leq 8 \quad \text{for linearity}$$


$$-6 \leq V_s \leq 4$$

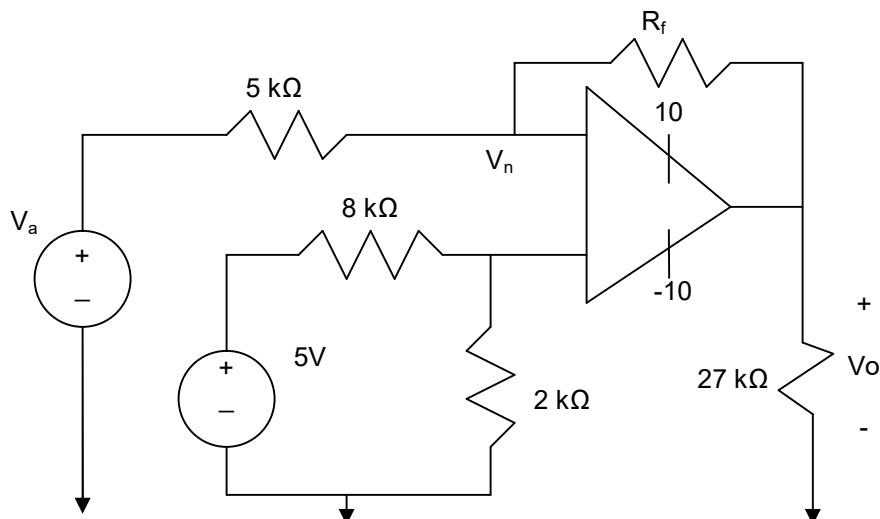5U. The Op Amp in the circuit shown below is ideal. What value of  $R_f$  will give the equation  $\{V_o = 5 - 4V_a\}$  for this circuit.



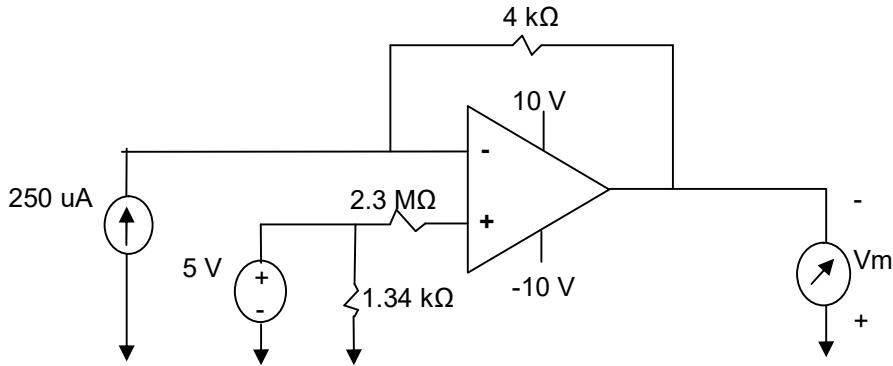**Solution:**

6S. A voltmeter with a full-scale reading of 20 V and  $10 \text{ M}\Omega$  internal resistances is used to measure the output voltage in the following circuit. Assuming the Op Amp is ideal, what is the reading of the voltmeter ( $V_m$ )?



**Solution:**

$$\text{KCL at } V_n \rightarrow -250 \times 10^{-6} + (V_n - (-V_m)/4000 + I_n = 0$$

Ideal Op Amp  $\rightarrow I_n = I_p = 0; V_n = V_p = 5V$ .


Combine the above two equations

$$-250 \times 10^{-6} + (5 + V_m)/4000 + 0 = 0 \rightarrow V_m = -4 \text{ V}$$

Voltmeter Reads -4 V.

6U. Suppose the strain gage resistors in the bridge shown in following figure have the value of  $120 \Omega \pm 1\%$  ( $\Delta R = 1.2 \Omega$ ). The power supplies to the Op Amp  $\pm 10 \text{ V}$ , and the reference voltage,  $V_{ref}$ , is taken from the positive power supply.

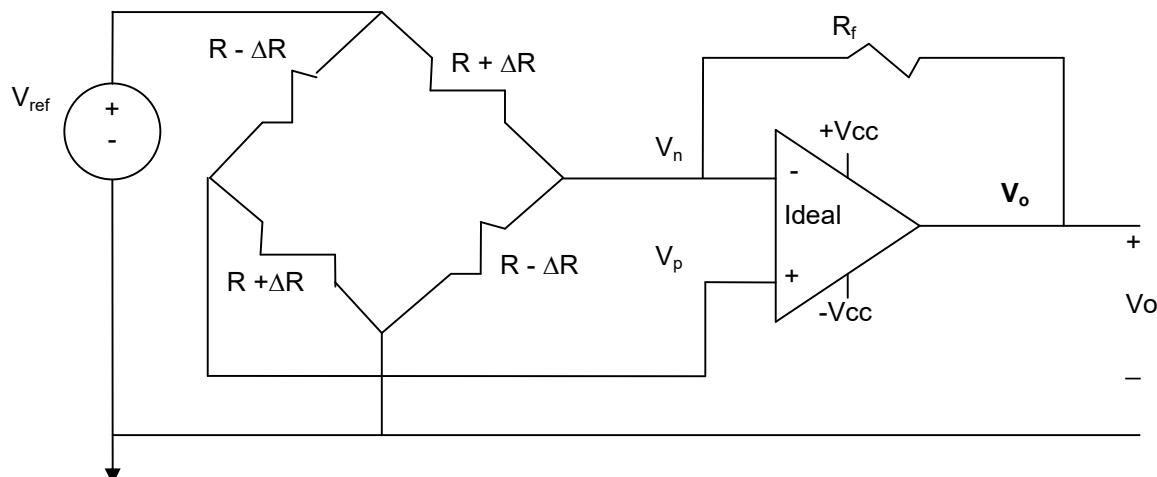- Calculate the value of  $R_f$  so that when the strain gage that is lengthening reaches its maximum length, the output voltage is 5 V.
- Suppose that we can accurately measure 50 mV changes in the output voltage. What change in strain gage resistance can be detected in millionohms?



**Solution:**


6Sb. Strain gage (SG) resistance is 350 ohms and is layed out on flat surface about 18 mm long SG's resistance increases by 10% when stretched by 1 mm and conversely, its resistance decreases by 10% when shrunk by 1 mm. Two SGs are attached to left and right side of a column at point of deflection.

a) Design a circuit using resistors, 12 v battery, Op Amps (Ideal), LEDs and SGs to turn on a red LED when the column is bending to the right and turn the green LED when the column is bending to the left.


b) For the the designed circuit, calculate  $V_{oG}$  (Voltage at the Green LED) and  $V_{oR}$  (Voltage at the Red LED) when the column is deflect at point of SG attachment by 1 mm.

**Solution:**

One Possible solution:

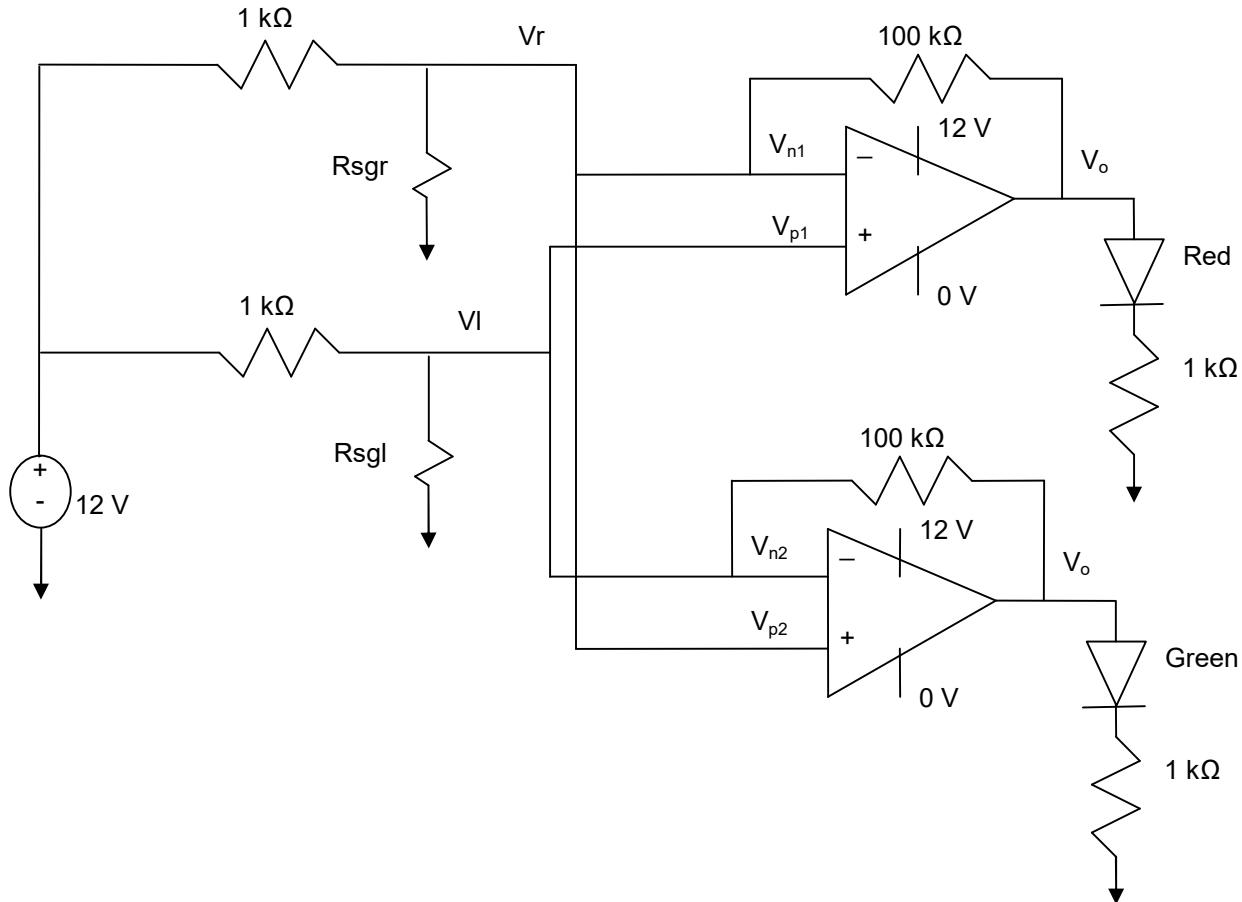

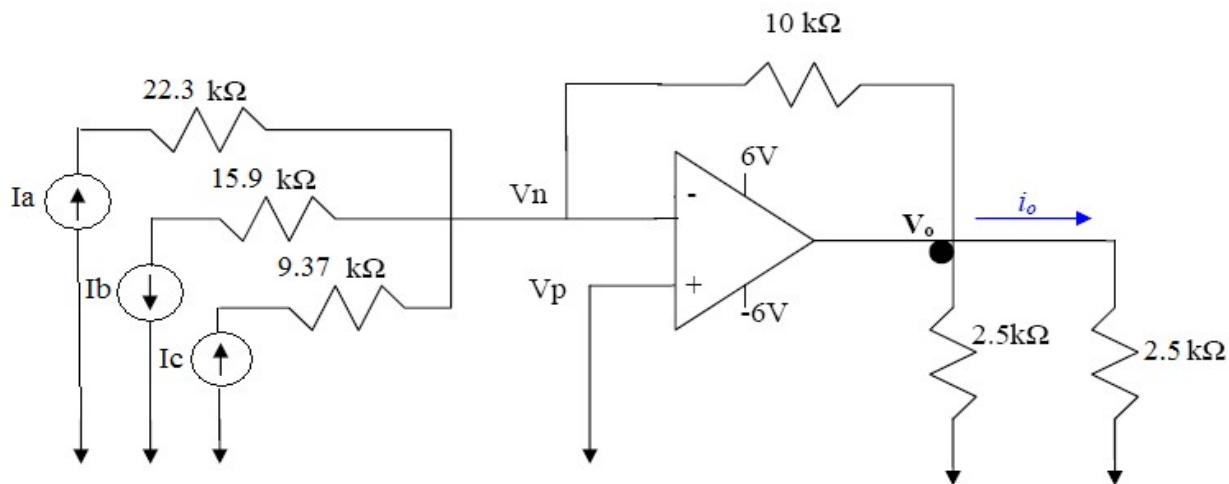6Sc. Find  $i_o$  in the following circuit. Assume an Ideal Op Amp. Current at  $I_a = 0.55\text{mA}$ , at  $I_b = 0.75\text{mA}$ , and at  $I_c = 0.25\text{mA}$ .



**Solution:**


$$\text{KCL @ } V_n \quad -0.55 + 0.75 - 0.25 + (V_n - V_o)/10 = 0$$

$$\begin{aligned} \text{Ideal Op Amp states: } I_n &= I_p = 0 \quad \& \quad V_n = V_p = 0 \\ -0.05 &= V_o/10 \\ V_o &= -0.5 \text{ V} \end{aligned}$$

$$I_o = V_o/R = -0.5/2.5 = -1/5 = -0.20 \text{ mA}$$

7S. For the following circuit and using ideal OpAmp Model:

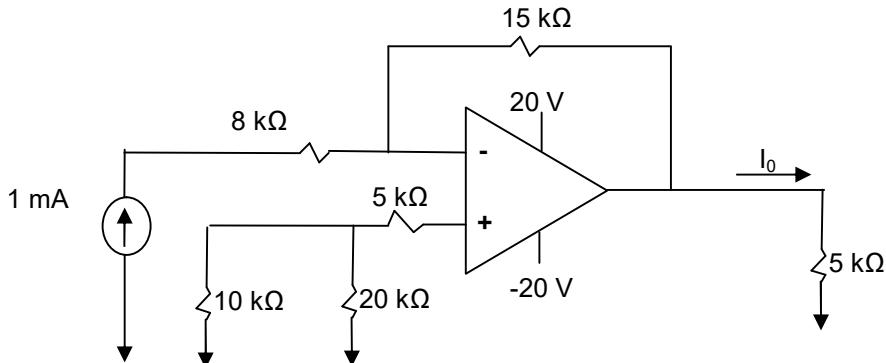- What Op Amp configuration is this?
- Find  $i_o$ .



**Solution:**

a) The circuit is an inverting amplifier, because the source is connected to the negative input terminal.


b) KCL at  $V_n$ :  $-1 + (V_n - V_o)/15 + I_n = 0$

Apply Ideal Op Amp:  $I_p = I_n = 0$  and  $V_n = V_p = 0$

So,  $V_o/15 = 1 \rightarrow V_o = -15 \text{ V}$

Now,  $I_o = V_o/5 = -15/5 \rightarrow I_o = -3 \text{ mA}$

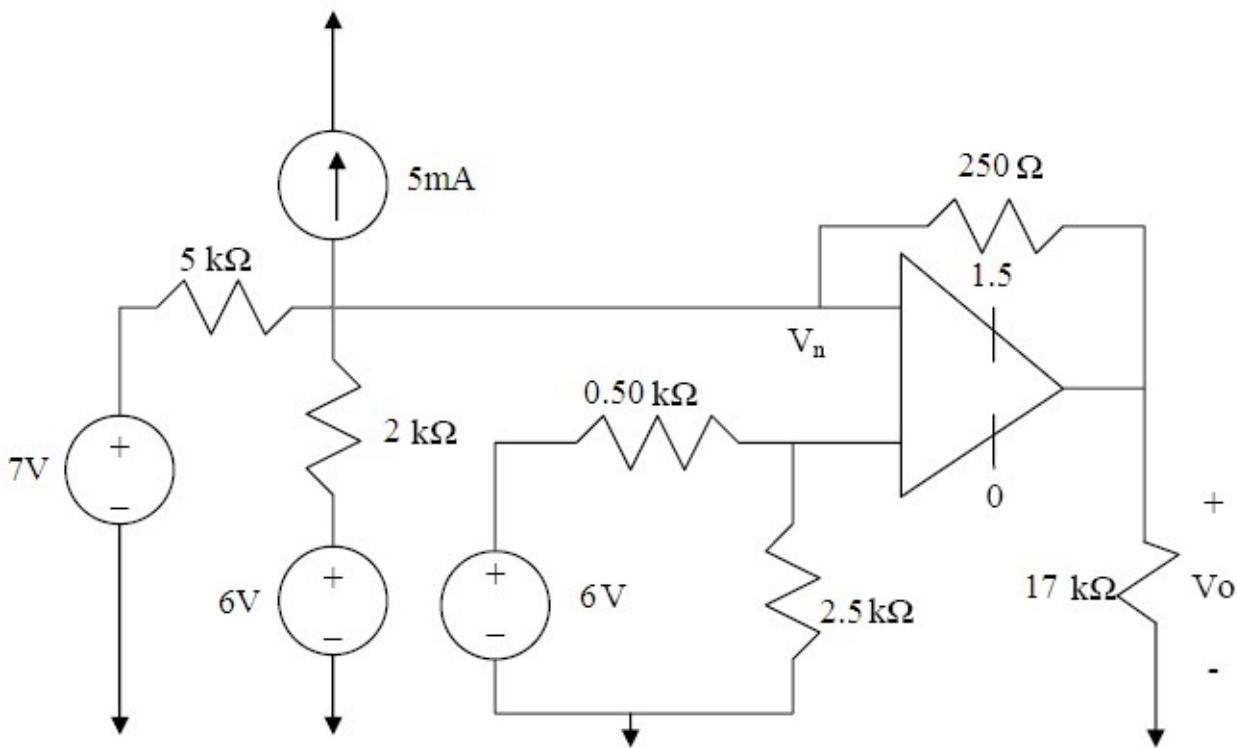7U. Find  $V_o$  assuming an Ideal Op Amp.




Solution:

$$\begin{aligned} \text{KCL at } V_n &\rightarrow (V_n - 7)/5 + (V_n - 6)/2 + 5 + (V_n - V_o)/0.250 = 0 \\ \text{KCL at } V_p &\rightarrow (V_p - 6) / 0.5 + V_p / 2.5 = 0 \end{aligned}$$

$$\text{Ideal Op Amp} \rightarrow I_n = I_p = 0 \quad \& \quad V_p = V_n$$

To be completed

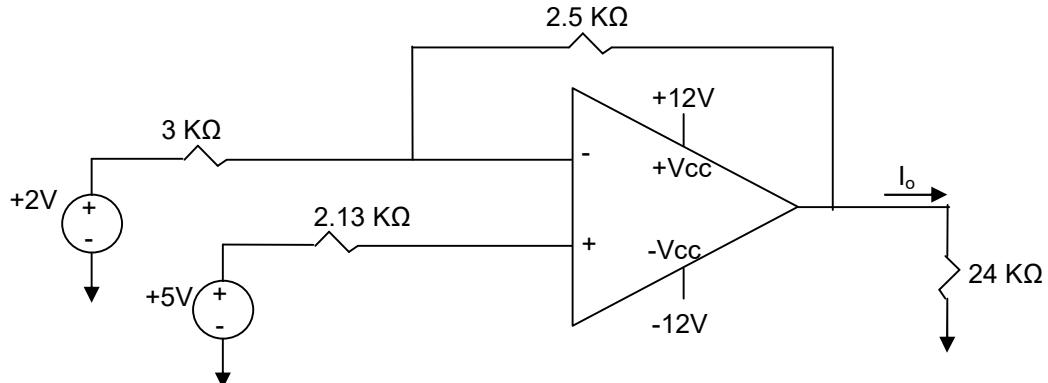7Sc. Calculate the value of  $I_o$  for the difference-amplifier circuit shown below (Ideal Op Amp).




Solution:

$$\text{KCL at } V_n \rightarrow \frac{V_n - 2}{3} + \frac{V_n - V_o}{2.5} = 0$$

Ideal Op Amp  $\rightarrow I_p = I_n = 0$  &  $V_n = V_p = 5$

$$\text{Therefore: } \frac{5 - 2}{3} + \frac{5 - V_o}{2.5} = 0 \rightarrow V_o = 7.5 \rightarrow I_o = V_o / 24 \text{ K} = 0.3125 \text{ mA}$$

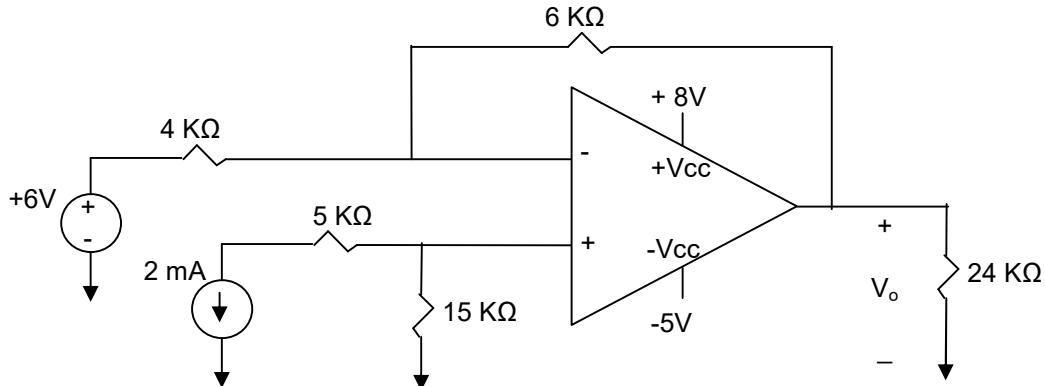7Sd. Calculate the value of  $V_o$  for the difference-amplifier circuit shown below (Using Idea OpAmp Model):



### Solution

$$\text{KCL at } V_n \rightarrow \frac{V_n - 6}{4} + \frac{V_n - V_o}{6} = 0$$


Ideal Op Amp  $\rightarrow I_p = 0$ ,  $I_n = 0$  &  $V_p = V_n \rightarrow V_p = -15 \times 2 = -30 \text{ V}$

$$\text{Therefore: } \frac{-30 - 6}{4} + \frac{-30 - V_o}{6} = 0 \rightarrow V_o = -84 \text{ V}$$

The OpAmp saturates at -5 V  $\rightarrow V_o = -5 \text{ V}$

7Se. In the following circuit, using ideal Op Amp model:

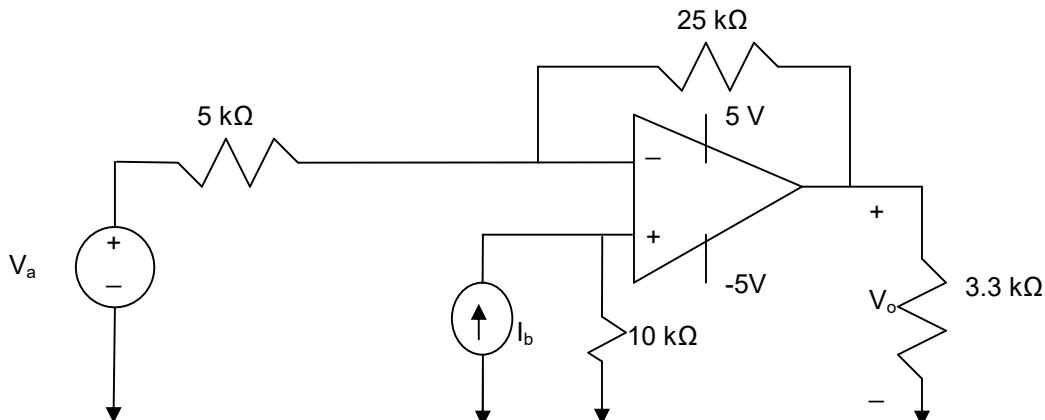- Find  $V_o$  in terms of  $V_a$  and  $I_b$
- Calculate  $V_o$  for  $V_a = 0.1 \text{ V}$  and  $I_b = 2 \text{ mA}$




### Solution:

- KCL at  $V_n \rightarrow (V_n - V_a)/5000 + (V_n - V_o)/25000 = 0$   
 $V_n = V_p = 10000I_b$


$$(10000 I_b - V_a)/5000 + (10000 I_b - V_o)/25000 = 0 \rightarrow V_o = 60000I_b - 5V_a$$

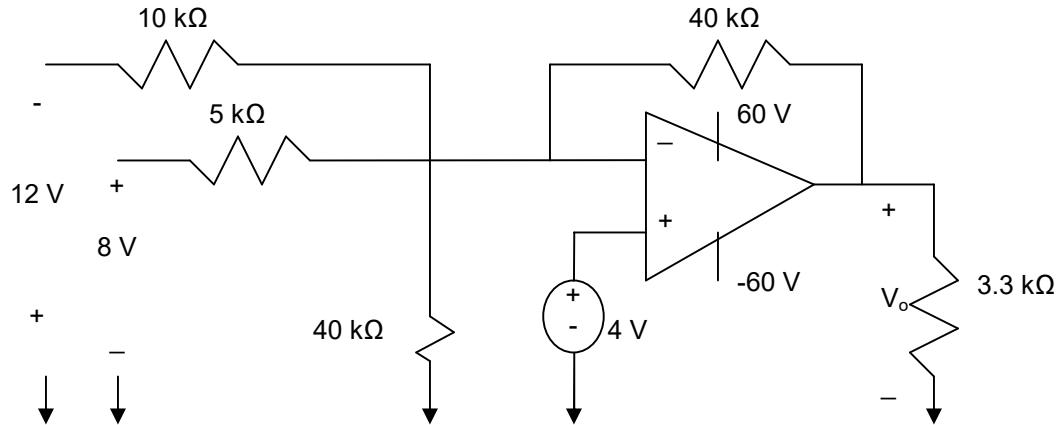b)  $V_o = 5 \text{ V}$  (limited by the rail – saturated)

7Sf. For the following Op Amp circuit, Find  $V_o$  using an Ideal op Amp model.



**Solution:**

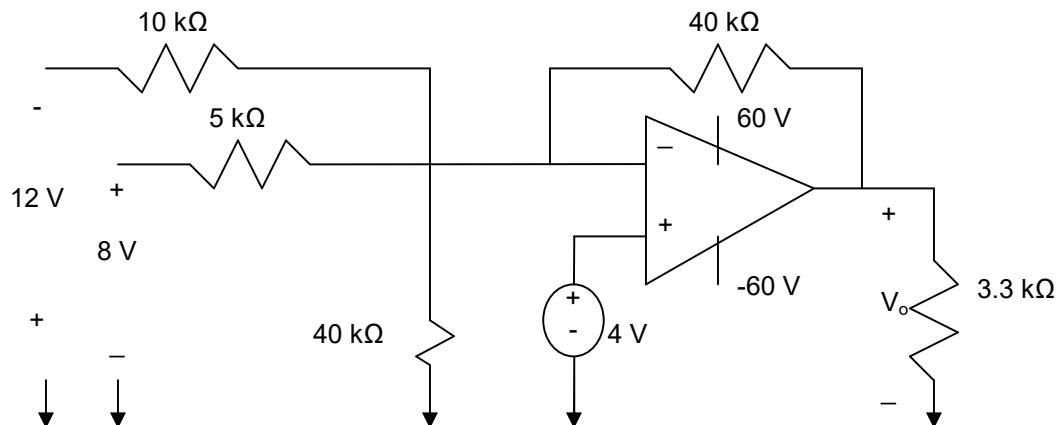

$$\text{KCL at Node } V_n \rightarrow \frac{V_n + 12}{10} + \frac{V_n - 8}{5} + \frac{V_n}{40} + \frac{V_n - V_o}{40} = 0$$

$$\text{Ideal Op Amp} \rightarrow I_p = I_n = 0 \rightarrow V_n = V_p = 4$$

$$\text{Apply to KCL equation} \rightarrow \frac{4+12}{10} + \frac{4-8}{5} + \frac{4}{40} + \frac{4-V_o}{40} = 0$$


$$V_o = 40 \text{ V}$$

The output within the rail voltages...

8S. In the difference amplifier shown below, compute

- a) the differential mode gain
- b) the common mode gain

c) the CMRR

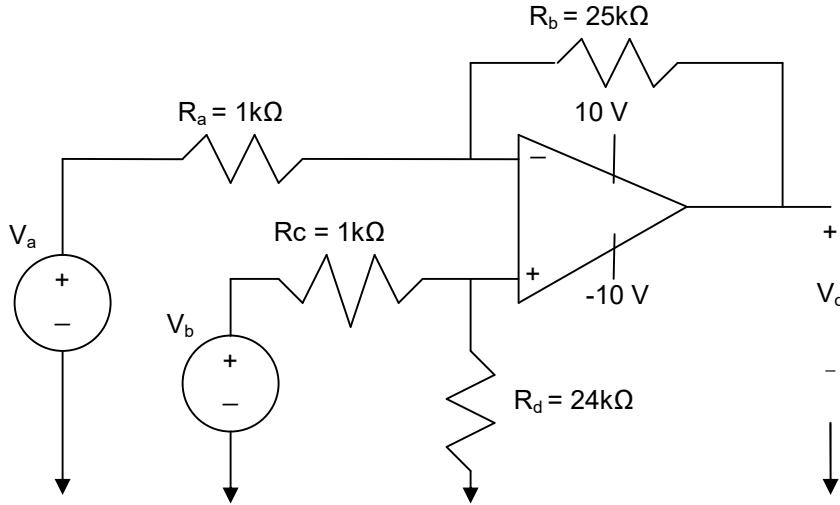

**Solution:**

$$a) \text{ Common Mode Gain} = A_{cm} = \frac{V_o}{V_{cm}} = \frac{R_a R_d - R_b R_c}{R_a (R_c + R_d)} = \frac{24 - 25}{1 * (1 + 24)} = -\frac{1}{25}$$


b) Difference Mode Gain

$$A_{dm} = \frac{V_o}{V_{dm}} = \frac{R_d (R_a + R_b) + R_b (R_c + R_d)}{2 R_a (R_c + R_d)} = \frac{24(1 + 25) + 25(1 + 24)}{2 * 1 * (1 + 24)} = 24.98$$

$$c) \text{ Common Mode Rejection Ratio} = \text{CMRR} = \left| \frac{A_{dm}}{A_{cm}} \right| = \left| \frac{24.98}{-\frac{1}{25}} \right| = 624.5$$


8U. In the difference amplifier shown below, compute

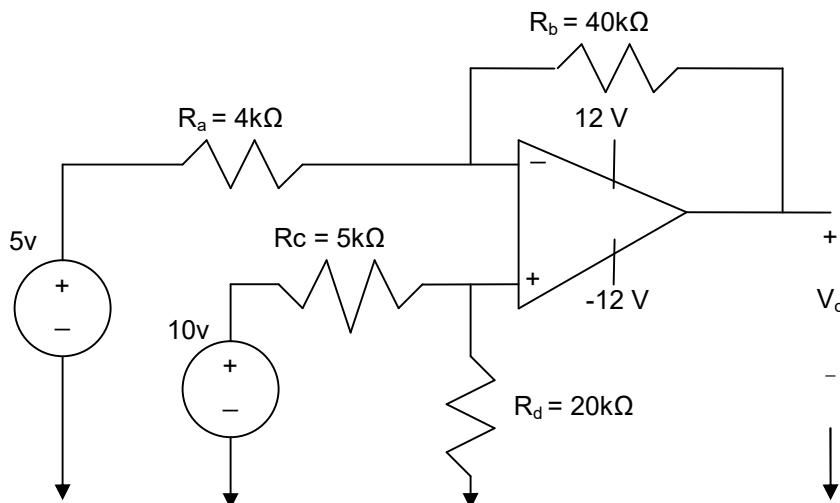- a) the differential mode gain
- b) the common mode gain
- c) the CMRR



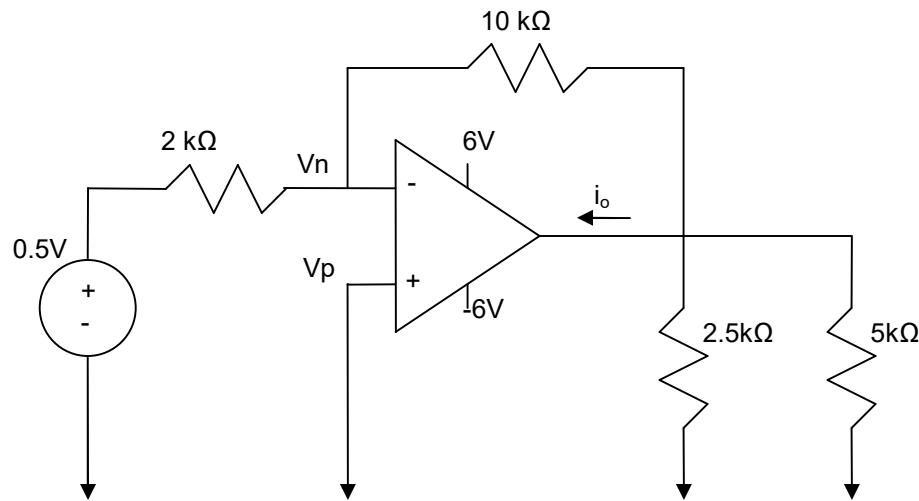
**Solution:**

9S. Find  $i_o$  in the following circuit using Op Amp DC Model where open loop gain,  $A= 10,000$ , Input resistance,  $R_i$  of  $200 \text{ k}\Omega$  and output resistance,  $R_o$  of  $50 \Omega$ .



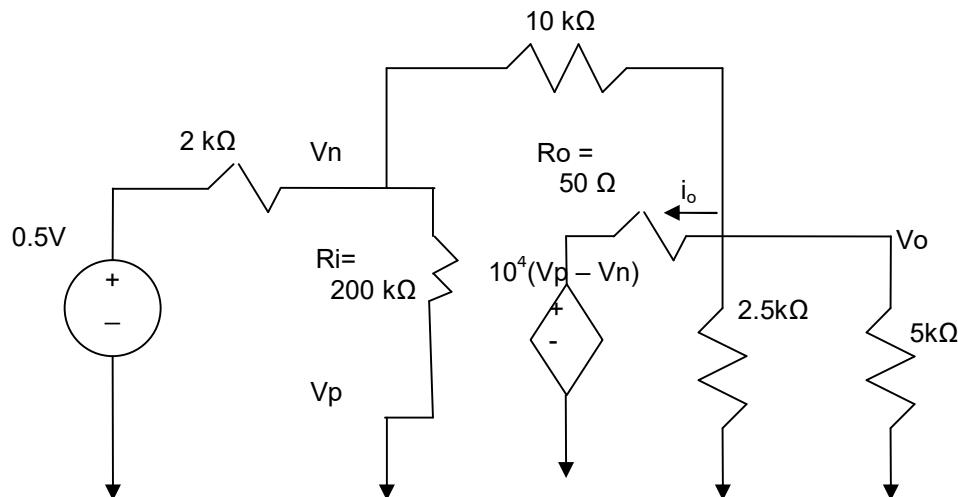**Solution:**

redraw the circuit with Op Amp DC Mode and use Node Voltage to analyze the circuit:



3 essential nodes  $V_o$ ,  $V_n$  & reference node.

$$\text{KCL at } V_n \rightarrow (V_n - 0.5)/2,000 + V_n/200,000 + (V_n - V_o)/10,000 = 0$$

$$\text{KCL at } V_o \rightarrow (V_o - V_n)/10,000 + V_o/5,000 + V_o/2,500 + (V_o - 10^4(-V_n))/50 = 0$$


Simplify the equations:

$$121V_n - 20V_o = -50$$

$$(2 \times 10^6 - 1)V_n - 207V_o = 0$$

Solve to find  $V_o$  &  $i_o$

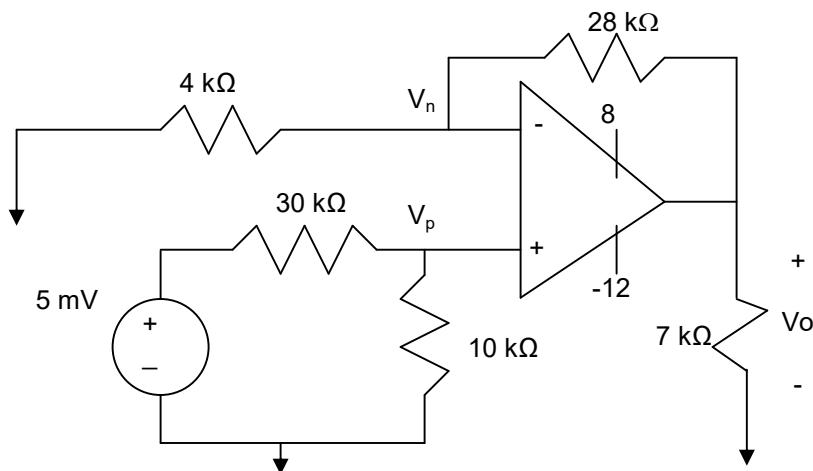9U. Find  $V_o$  in the following circuit using LM 324 Op Amp DC Model where open loop gain,  $A= 10^5$ , Input resistance,  $R_i$  of  $2 \text{ M}\Omega$  and output resistance,  $R_o$  of  $75 \Omega$ .



**Solution:**