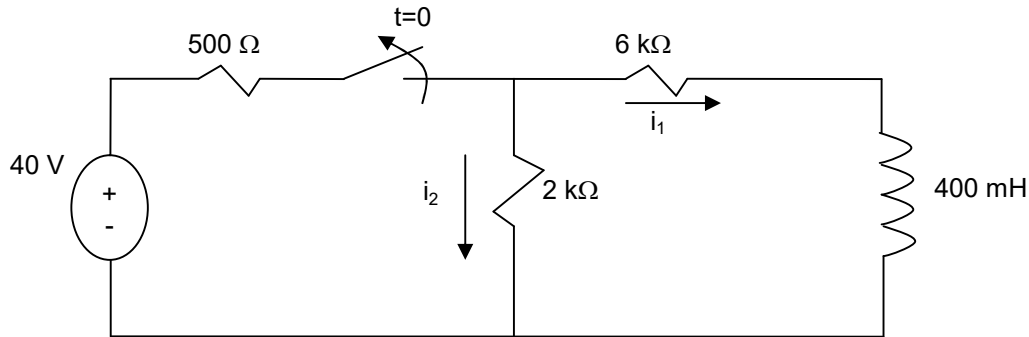


Fundamentals of Electrical Circuits - Chapter 7

1S. In the following circuit, the switch is opened at $t=0$, after the switch being closed for a long time.




- Find $i_1(0^-)$ and $i_2(0^-)$.
- Find $i_1(0^+)$ and $i_2(0^+)$.
- Find $i_1(t)$ for $t \geq 0$.
- Find $i_2(t)$ for $t \geq 0$.
- Explain why $i_2(0^-) \neq i_2(0^+)$.

Solution:

- Find $i_1(0^-)$ and $i_2(0^-)$.

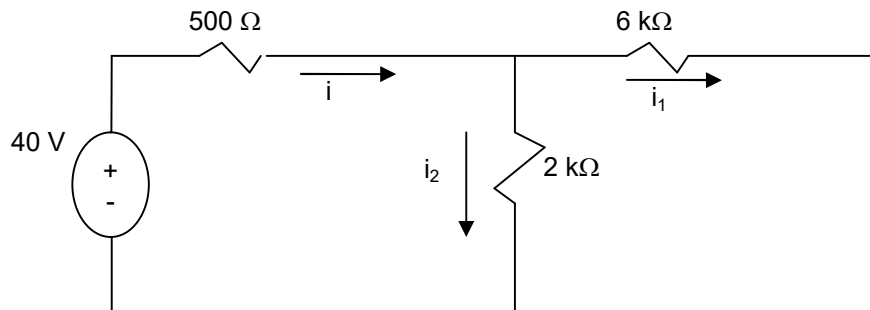At $t=0^-$, the switch has been closed for a long time. Therefore the inductor appears as a short..



Apply KVL \rightarrow

$$-40 + 500i + 2000(i - i_1) = 0 \rightarrow 2500i - 2000i_1 = 40$$

$$6000i_1 + 2000(i_1 - i) = 0 \rightarrow -2000i + 8000i_1 = 0$$

Solve and we know $i = i_1 + i_2$


$$i(0^-) = 0.020 \text{ A}$$

$$i_1(0^-) = 0.005 \text{ A}$$

$$i_2(0^-) = 0.015 \text{ A}$$


- Find $i_1(0^+)$ and $i_2(0^+)$.

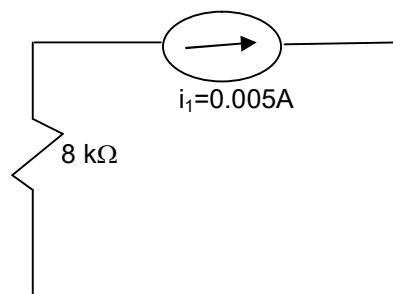Immediately after switch is Opened at $t=0^+$, the inductor supplies $i_1(0^+) = i_1(0^-) = 0.005 \text{ A}$ current.



$$i_2(0^+) = -i_1(0^+) = -0.005 \text{ A}$$

c) Find $i_1(t)$ for $t \geq 0$.

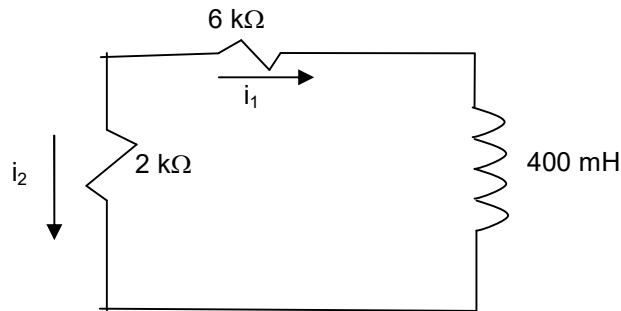

Apply the Natural Response relationships $\rightarrow i(t) = i(0)e^{-(R/L)t}$ for $t \geq 0$

$$i_1(t) = i_1(0^+)e^{-(R/L)t} = 0.005e^{-(8000/0.4)t} \text{ for } t \geq 0$$

$$i_1(t) = 0.005e^{-20000t} \text{ A for } t \geq 0$$

d) Find $i_2(t)$ for $t \geq 0^+$.


$$i_2(t) = -i_1(t) = -0.005e^{-20000t} \text{ for } t \geq 0^+$$

The only difference with part c is that t cannot be equal to 0.

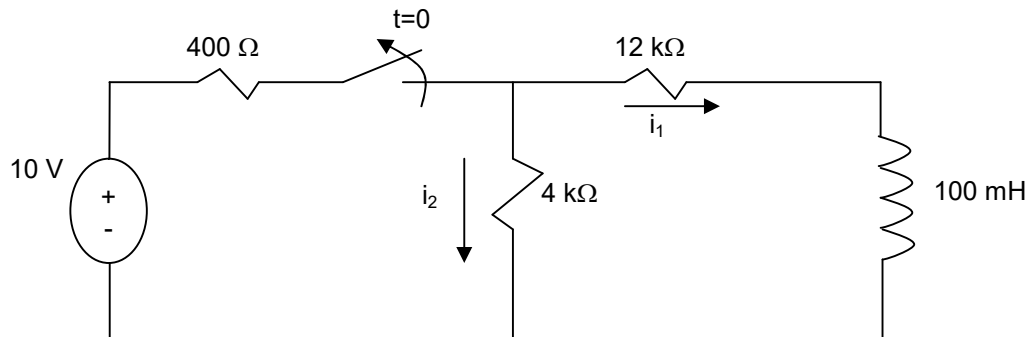e) Explain why $i_2(0^-) \neq i_2(0^+)$.

The current in resistor changes instantly. While the switching operation forces $i_2(0^-)$ to be 0.015 A and $i_2(0^+)$ to be -0.005 A

1U. In the following circuit, the switch is opened at $t=0$, after the switch being closed for a long time.



a) Find $i_1(0^-)$ and $i_2(0^-)$.

b) Find $i_1(0^+)$ and $i_2(0^+)$.


c) Find $i_1(t)$ for $t \geq 0$.

d) Find $i_2(t)$ for $t \geq 0$.

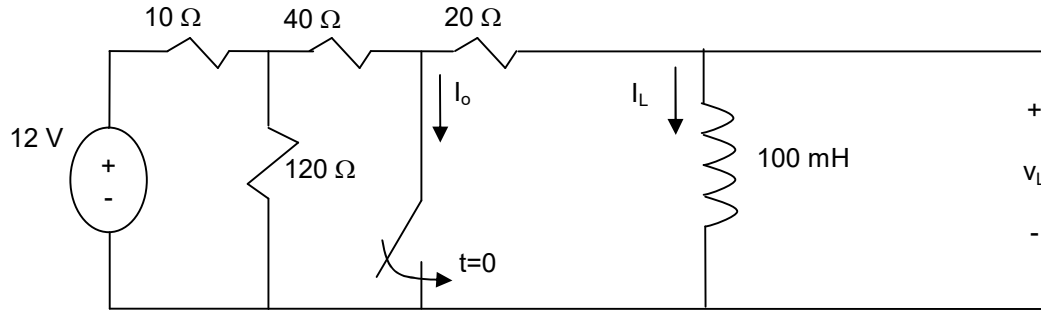e) Explain why $i_2(0^-) \neq i_2(0^+)$.

Solution:

2S. The switch shown in the following figure has been open a long time before closing at $t=0$.




- Find $i_o(0^-)$.
- Find $i_L(0^-)$.
- Find $i_o(0^+)$.
- Find $i_L(0^+)$.
- Find $i_o(\infty)$.
- Find $i_L(\infty)$.
- Write the expression for $i_L(t)$ for $t \geq 0$.
- Find $V_L(0^-)$.
- Find $V_L(0^+)$.
- Find $V_L(\infty)$.
- Write the expression for $V_L(t)$ for $t \geq 0^+$.
- Write the expression for $i_o(t)$ for $t \geq 0^+$.

Solution:

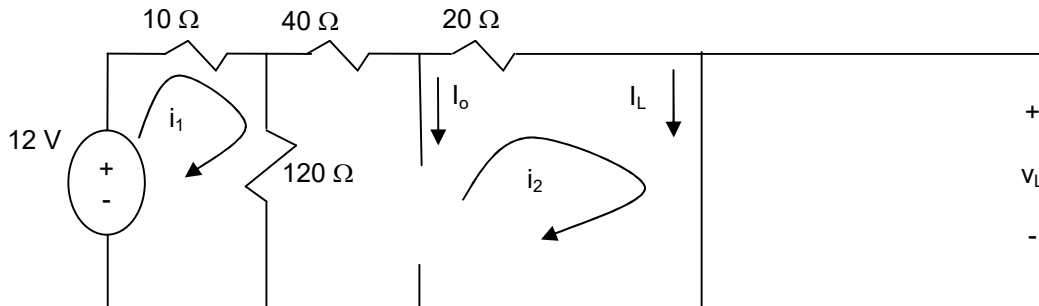- a) Find $i_o(0^-)$.

at $t=0^- \rightarrow$ circuit before the switch is closed and the inductor appear as a short.



$i_o(0^-)=0$ since the switch is open.

- b) Find $i_L(0^-)$.

$$\text{KVL} \rightarrow -12 + 10i_1 + 120(i_1 - i_2) = 0 \rightarrow 130i_1 - 120i_2 = 12$$

$$\text{KVL} \rightarrow 20i_2 + 40i_2 + 120(i_2 - i_1) = 0 \rightarrow -120i_1 + 180i_2 = 0$$


Solve

$$i_1 = 0.24 \text{ A}; i_2 = 0.16 \text{ A};$$

$$\rightarrow i_L(0^-) = i_2 = 0.16 \text{ A}$$

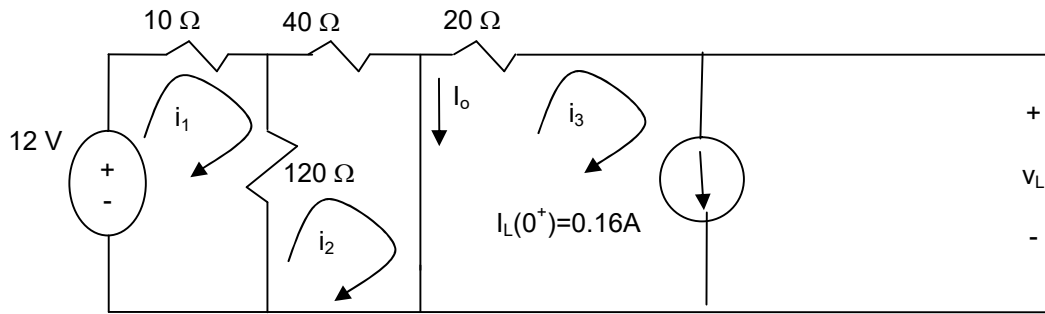- c) Find $i_o(0^+)$.

at $t=0^+ \rightarrow$ circuit after the switch is closed and the inductor appear as a current source.



KVL @ $i_1 \rightarrow -12 + 10i_1 + 120(i_1 - i_2) = 0 \rightarrow 130i_1 - 120i_2 = 12 \rightarrow 520i_2/3 - 120i_2 = 12 \rightarrow i_2 = 0.225 \text{ A}$
 KVL @ $i_2 \rightarrow 120(i_2 - i_1) + 40i_2 = 0 \rightarrow -120i_1 + 160i_2 = 0 \rightarrow i_1 = 4i_2/3$
 KVL @ $i_3 \rightarrow i_3 = 0.16$


$i_o = i_o(0^+) = i_2 - i_3 = 0.065 \text{ A}$

d) Find $i_L(0^+)$.

$i_L(0^+) = i_L(0^-) = 0.16 \text{ A}$

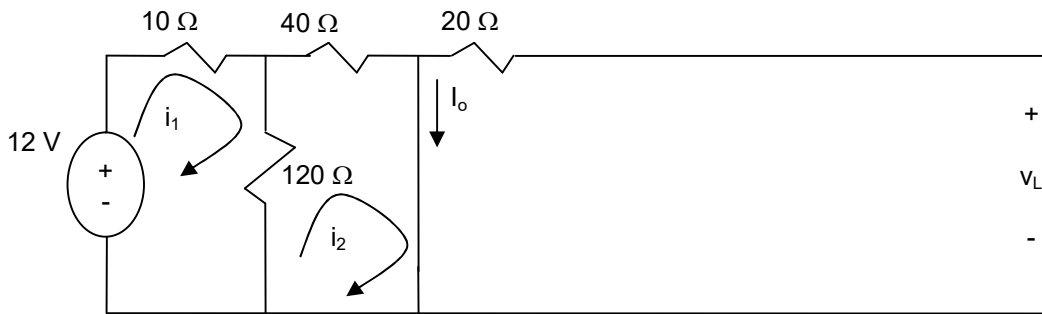e) Find $i_o(\infty)$.

Inductor will have current of 0 (open) after long period of switch being closed




Same as part d $\rightarrow i_o(\infty) = i_2 = 0.225 \text{ A}$

f) Find $i_L(\infty)$.

$i_L(\infty) = 0;$

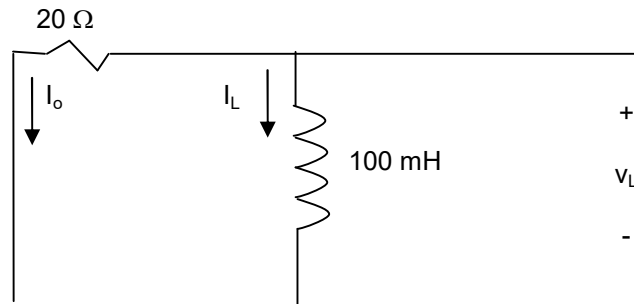g) Write the expression for $i_L(t)$ for $t \geq 0$.



Apply the Natural Response relationships $\rightarrow i(t) = i(0)e^{-(R/L)t}$ for $t \geq 0$

$i_L(t) = 0.16e^{-(20/.1)t}$ for $t \geq 0$

$i_L(t) = 0.16e^{-200t}$

h) Find $V_L(0^-)$.

$$V_L(0^-) = 0$$

i) Find $V_L(0^+)$.

refer to circuit in part c and write KVL around the most right loop \rightarrow

$$20 \cdot (0.16) + V_L(0^+) = 0 \rightarrow V_L(0^+) = -3.2 \text{ V}$$

j) Find $V_L(\infty)$.

$$V_L(\infty) = 0$$

k) Write the expression for $V_L(t)$ for $t \geq 0^+$.


$$v_L(t) = L \frac{di_L}{dt} = (0.1) \frac{di_L}{dt} = 0.1 \cdot 0.16 \cdot (-200) e^{-(20/.1)t} \text{ for } t \geq 0$$

$$v_L(t) = -3.2 e^{-200t}$$

l) Write the expression for $i_o(t)$ for $t \geq 0^+$.

$$i_o(t) = i_2(t) - i_L(t) = 0.225 - 0.16 e^{-200t} \text{ A}$$

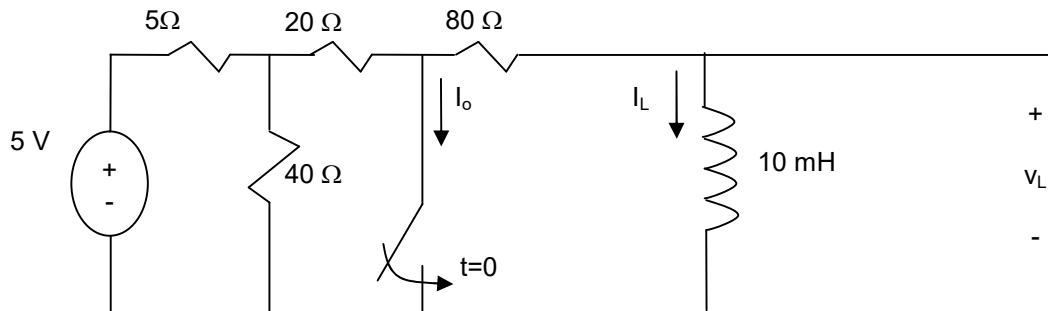2U. The switch shown in the following figure has been open a long time before closing at $t=0$.



a) Find $i_o(0^-)$.

b) Find $i_L(0^-)$.

c) Find $i_o(0^+)$.

d) Find $i_L(0^+)$.

e) Find $i_o(\infty)$.

f) Find $i_L(\infty)$.

g) Write the expression for $i_L(t)$ for $t \geq 0$.

h) Find $V_L(0^-)$.

i) Find $V_L(0^+)$.


j) Find $V_L(\infty)$.

k) Write the expression for $V_L(t)$ for $t \geq 0^+$.

l) Write the expression for $i_o(t)$ for $t \geq 0^+$.

Solution:

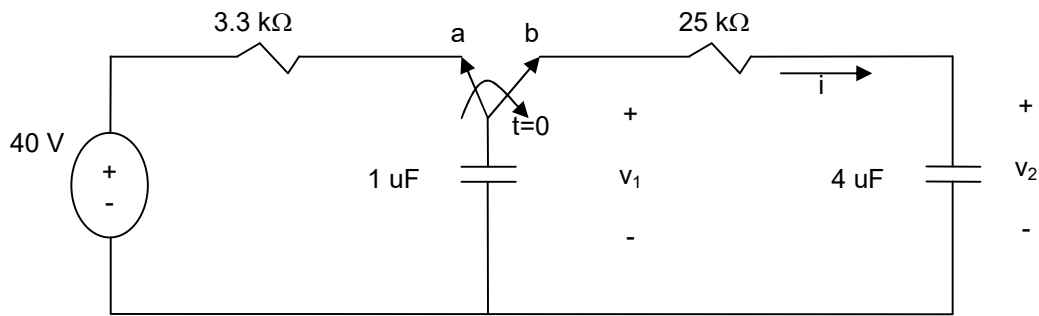3S. The switch in the following circuit has been in position for a long time. At $t=0$, the switch is thrown to position b.



Calculate:

- i , v_1 and v_2 for $t \geq 0^+$.
- energy stored in the capacitors at $t = 0$.
- energy trapped in the circuit and the total energy dissipated in the $25\text{ k}\Omega$ resistor if the switch remains in position b indefinitely.

Solution:

- i , v_1 and v_2 for $t \geq 0^+$.

After a long time with switch in position a results in capacitor appear as opening

$$\rightarrow v_1(0^-) = v_1(0^+) = 40\text{ V}; \quad v_2(0^-) = 0\text{ V};$$


When switch is put to position b, voltage is applied to $4\mu\text{F}$ which would appear open at $t=0^+$

$$\rightarrow v_1(0^+) = 40\text{ V}$$


$$\rightarrow i(0^+) = 0$$

$$\rightarrow v_2(0^+) = 40\text{ V}$$

After Switch is changes from a to b

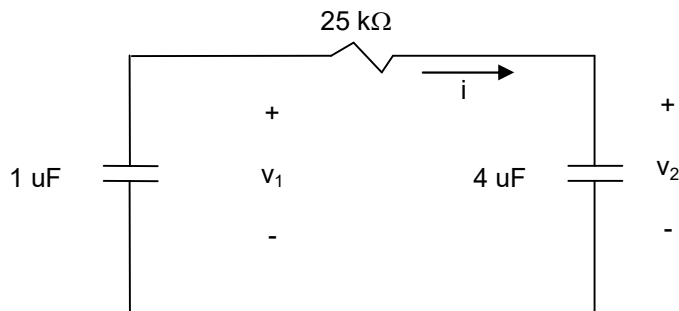

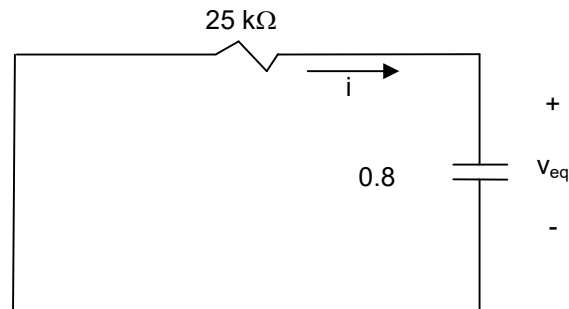
$$C_{eq} = 1/(1/1 + 1/4) = 0.8\text{ }\mu\text{F}$$



Apply the Natural Response relationships $v(t) = v(0)e^{-t/RC}$ for $t \geq 0$

$$i = C \frac{dv}{dt} = -C \frac{v(0)}{RC} e^{-t/RC} = -\frac{v(0)}{R} e^{-t/RC} \quad \text{for } t \geq 0$$
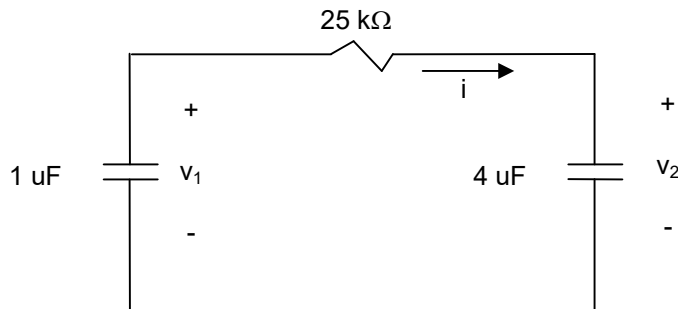
$$i(t) = -\frac{40}{25000} e^{-t/(25 \times 10^3 \times 0.8 \times 10^{-6})} = -1.6 e^{-50t} \text{ mA} \quad \text{for } t \geq 0$$



$$v_1 = \frac{1}{C} \int_0^t i(\tau) d\tau + v(0^-) = \frac{1}{1 \times 10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50\tau} d\tau + 40 = -32 e^{-50t} + 72 \text{ V} \quad \text{for } t \geq 0$$

$$v_2 = \frac{1}{C} \int_0^t i(\tau) d\tau + v(0^-) = \frac{1}{4 \times 10^{-6}} \int_0^t -1.6 \times 10^{-3} e^{-50\tau} d\tau + 0 = 8 e^{-50t} - 8 \text{ V} \quad \text{for } t \geq 0$$

- b) Energy stored in the capacitor at $t = 0$.

The only capacitor with energy is 1 μF capacitor

$$w(0) = \frac{1}{2} C v(0)^2 = 0.5 \times 10^{-6} \times (40)^2 = 800 \text{ μJ}$$


- c) Energy trapped in the circuit and the total energy dissipated in the 25 kΩ resistor if the switch remains in position b indefinitely.

$$w_{\text{trapped}}(\infty) = \frac{1}{2} C_1 v_1^2 + \frac{1}{2} C_2 v_2^2 = 0.5 \times 10^{-6} \times (72)^2 + 0.5 \times 4 \times 10^{-6} \times (8)^2 = 2624 \text{ μJ}$$

The energy that R will dissipate is equal to the amount of energy that was in the equivalent C at $t=0+$ since after a long-time the stored energy in the combined capacitor will be zero:

$$w_{\text{Ceq}}(0) = \frac{1}{2} C v(0)^2 = 0.5 \times 0.8 \times 10^{-6} \times (40)^2 = 640 \text{ μJ}$$

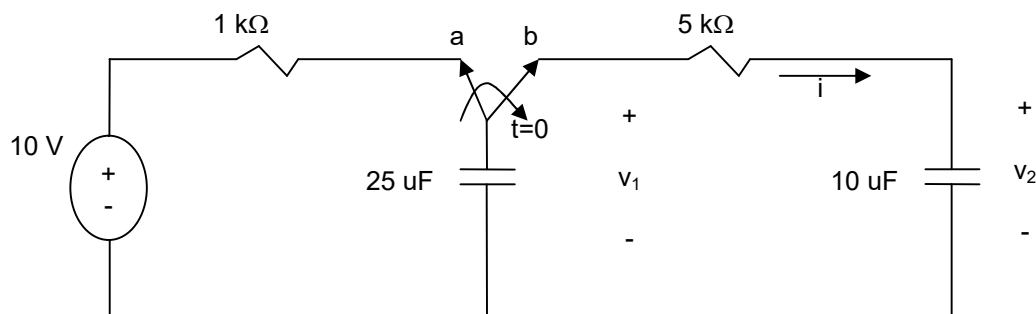3U. The switch in the following circuit has been in position for a long time. At $t=0$, the switch is thrown to position b.




Calculate

- i , v_1 and v_2 for $t \geq 0^+$.
- energy stored in the capacitor at $t = 0$.
- energy trapped in the circuit and the total energy dissipated in the 5 kΩ resistor if the switch remains in position b indefinitely.

Solution:

4S. The switch in the following circuit has been in position a for a long time. At $t=0$, the switch moves instantaneously to position b.

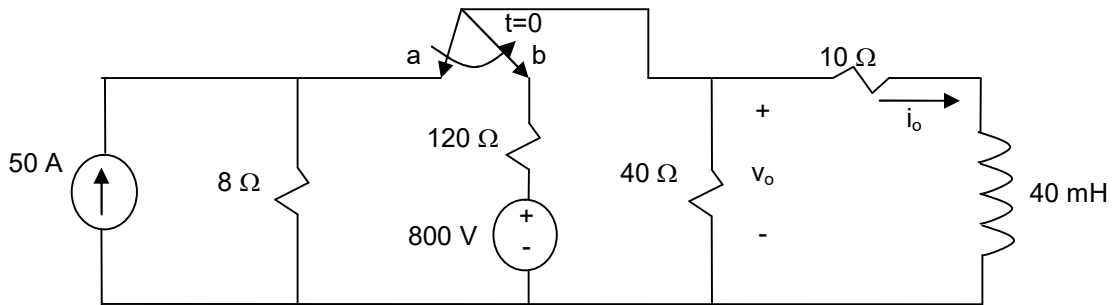
- Find the numerical expression for $i_o(t)$ where $t \geq 0$.
- Find the numerical expression for $v_o(t)$ where $t \geq 0^+$.



Solution:

- Find the numerical expression for $i_o(t)$ where $t \geq 0$.

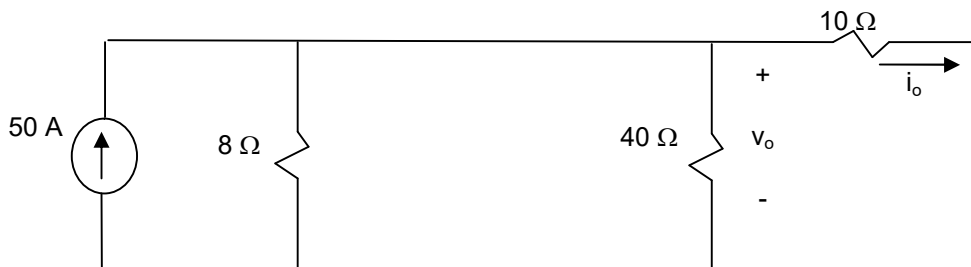
When the switch has been in position a for a long-time \rightarrow Inductor will appear as a short




Simplified circuit $\rightarrow V(o^-) = 50 \times 4 = 200\text{V}$

Original circuit $\rightarrow i_o(o^-) = 200 / 10 = 20\text{ A}$

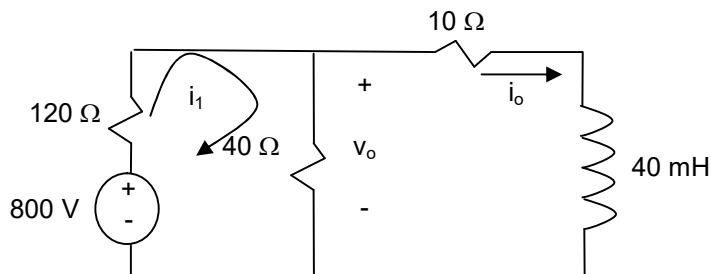After the switch is change to position b , circuit is redrawn and find the Thevenin equivalent with respect to Inductor terminals:




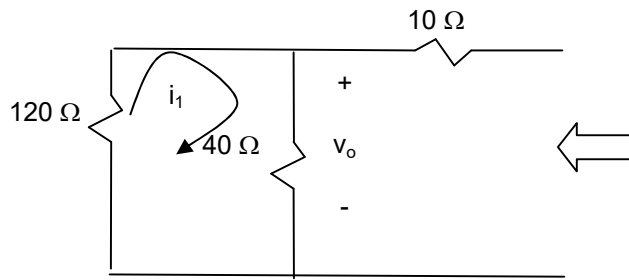To Find R_{th} disable Voltage source (short)




$$R_{th} = (120 \parallel 40) + 10 = 40 \Omega$$

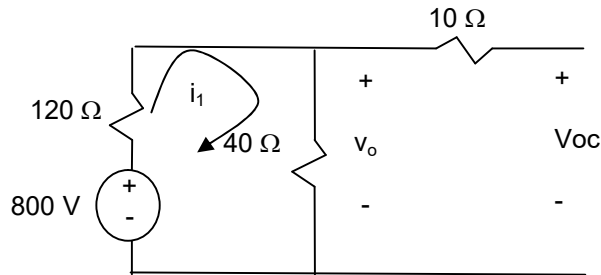To Find V_{th} or V_{oc} disable Voltage source (short)



$$KVL \rightarrow -800 + 120 i_1 + 40 i_1 = 0 \rightarrow 160 i_1 = 800 \rightarrow i_1 = 5 A \rightarrow V_{oc} = 40 * 5 = 200 V$$

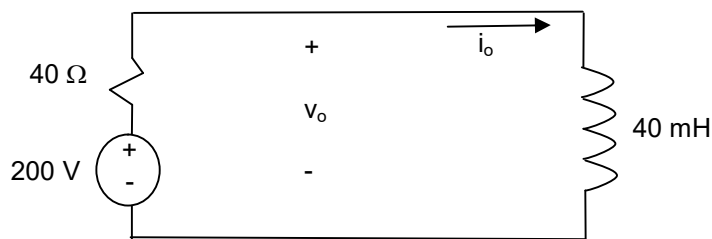
Place the Thevenin Equivalent back into the circuit:



$$\text{Apply the step response relationships } i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-(R/L)t} \text{ for } t \geq 0$$

$$\rightarrow i_o(t) = \frac{200}{40} + \left(20 - \frac{200}{40} \right) e^{-(40/.004)t} = 5 + 15e^{-1000t} A \text{ for } t \geq 0$$

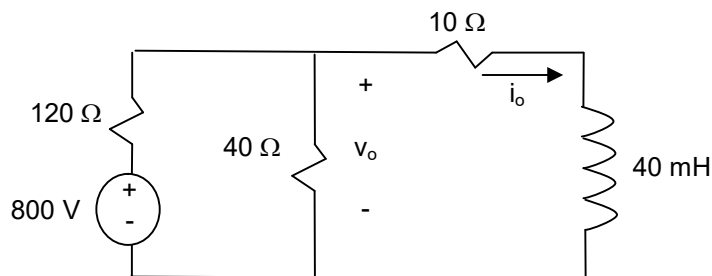
b) Find the numerical expression for $v_o(t)$ where $t \geq 0^+$.



$$v_o(t) = 10i_o + L \frac{di}{dt} = 10(5 + 15e^{-1000t}) + 0.04(-1000)(15e^{-1000t}) = 50 - 450e^{-1000t} \text{ for } t \geq 0$$


4U. The switch in the following circuit has been in position a for a long time. At $t=0$, the switch moves instantaneously to position b.

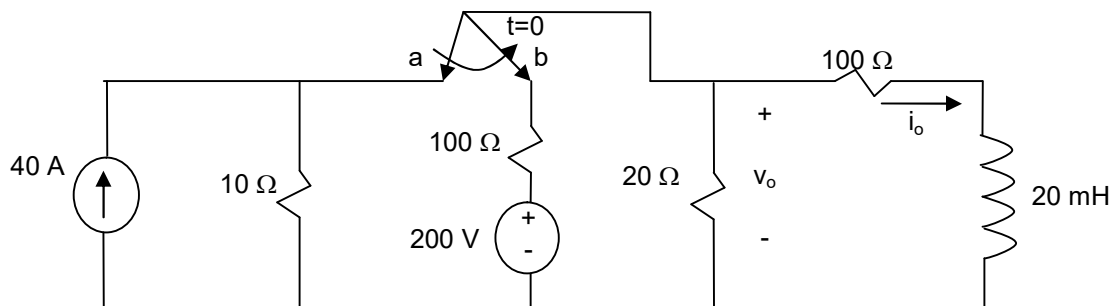- Find the numerical expression for $i_o(t)$ where $t \geq 0$.
- Find the numerical expression for $v_o(t)$ where $t \geq 0^+$.




Solution:

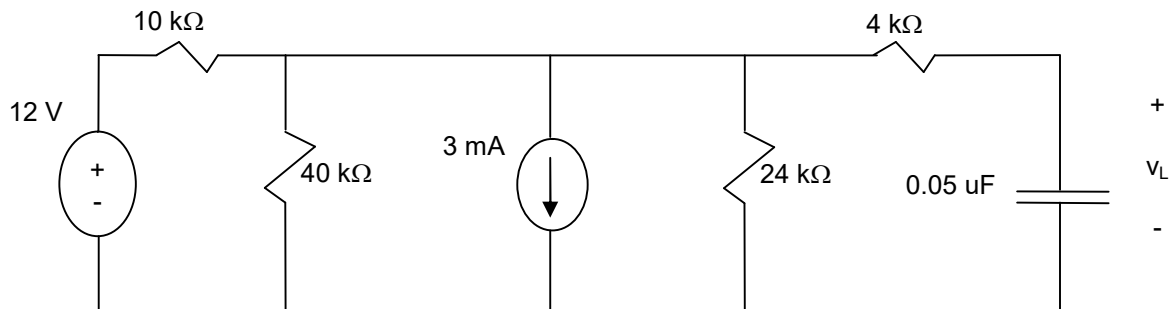5S. The following circuit has been in operation for a long time. At $t=0$, the voltage source reverses polarity and the current source drops from 3 mA to 2 mA. Find $v_L(t)$ for $t \geq 0$.




Solution:

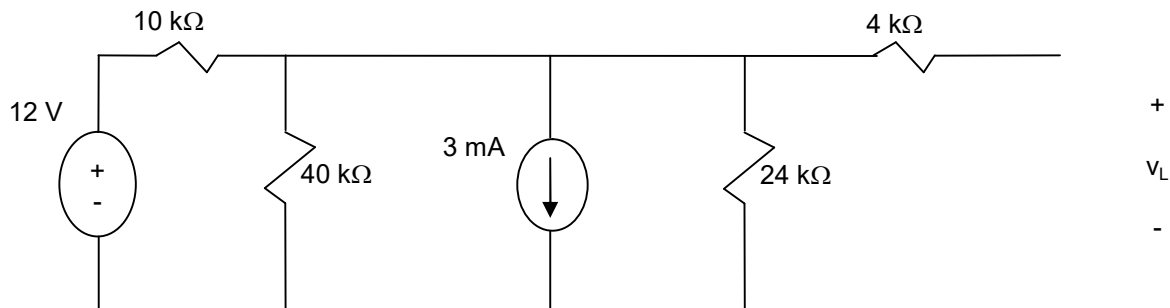
After circuit has been in current state for a long-time ($t=0^-$), Capacitor will appear as an open



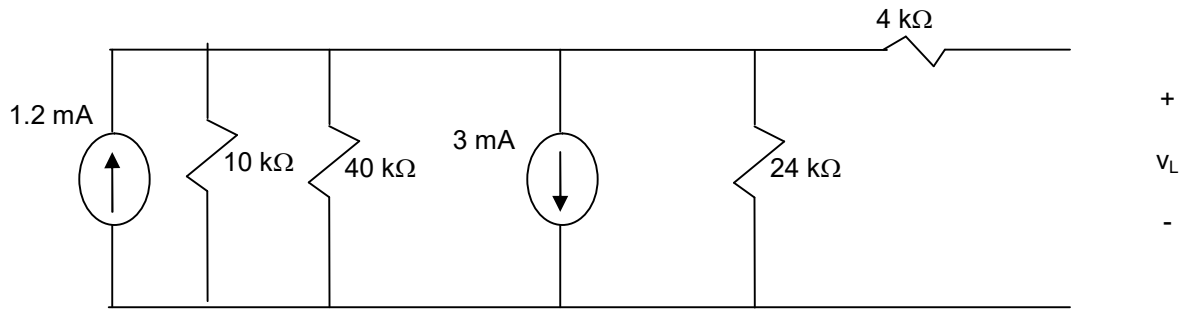
Use source transformation to simplify the circuit:
 $12\text{V} \text{ \& series } 10\text{ k}\Omega \rightarrow 1.2\text{ mA and parallel } 10\text{ k}\Omega$


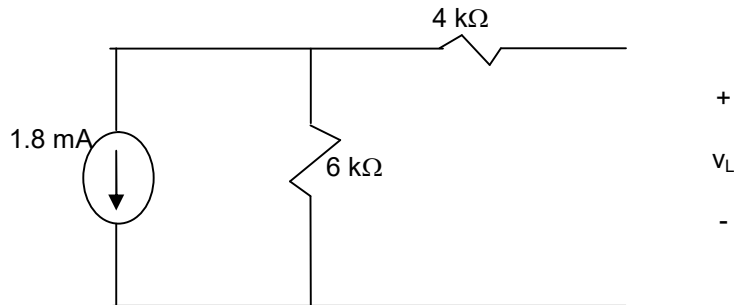
$$R = (10 \parallel 40 \parallel 24) = 6 \text{ k}\Omega$$




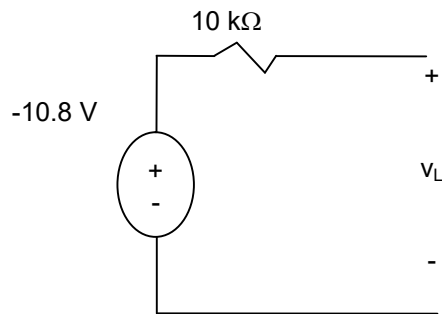1.8 mA & parallel 6 kΩ → 10.8 V and series 6 kΩ




$$v_{L(0^-)} = 1.8 \text{ mA} \cdot 6 \text{ k}\Omega = -10.8 \text{ V}$$

at $t=0$ ($t > 0$): circuit changes to

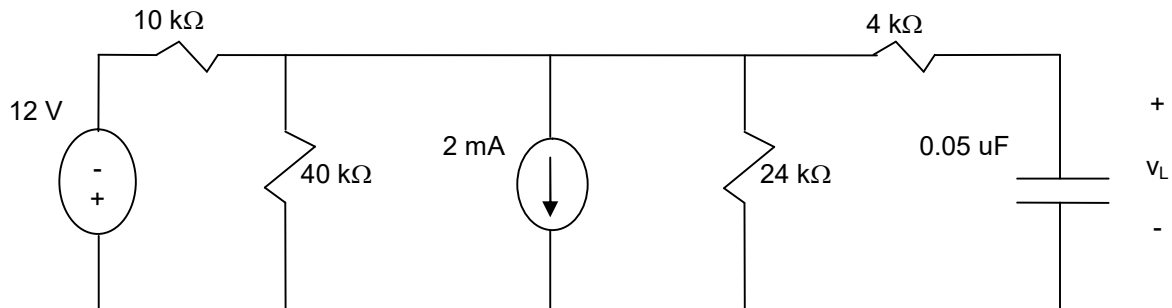


Use similar source transformation technique as used earlier will simplify the circuit into Norton equivalent.

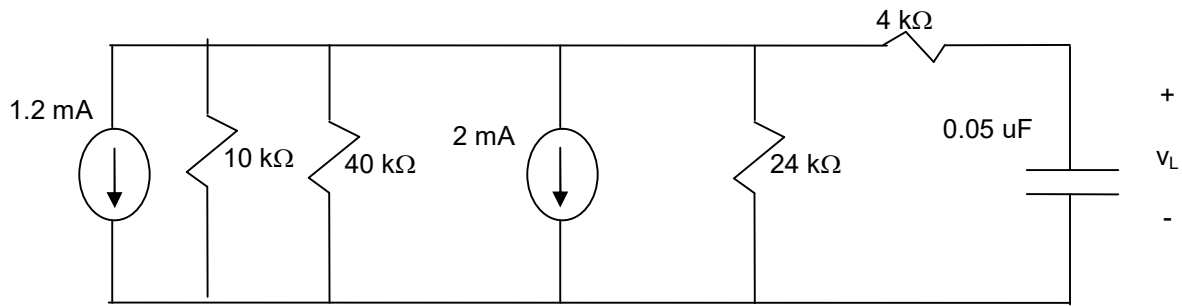
12v & series 10 kΩ → 1.2 mA and parallel 10 kΩ



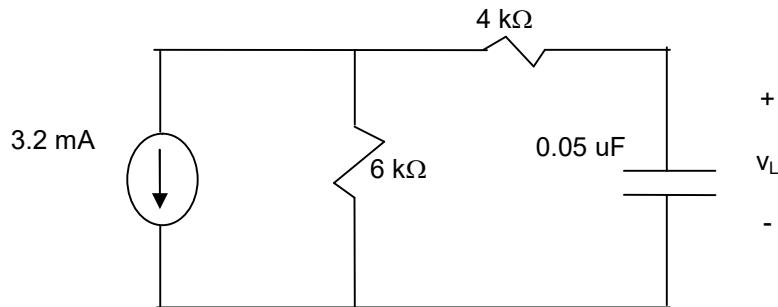
$$R = (10 \parallel 40 \parallel 24) = 6 \text{ k}\Omega$$



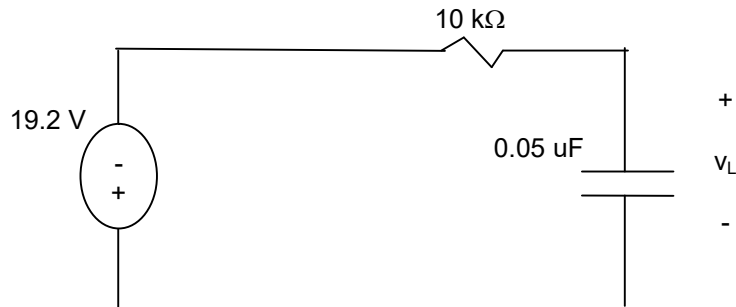3.2 mA & parallel 6 kΩ → 19.2 V and series 6 kΩ
Another source transformation reduces the circuit to:



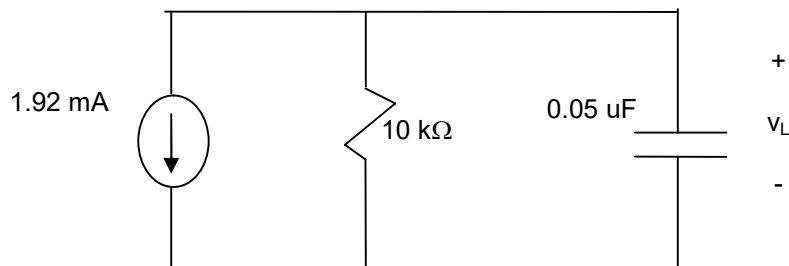Another transformation get us back to the standard form:
19.2v & series 10 kΩ → 1.92 mA and parallel 10 kΩ




Apply the step response for RC circuit $v(t) = I_s R + (V_0 - I_s R)e^{-t/RC}$ for $t \geq 0$

$$v_L(t) = -(0.00192) * (10,000) - (-10.8 - (-0.00192 * 10,000))e^{-t/0.0005} \text{ for } t \geq 0$$

$$v_L(t) = -19.2 + (+10.8 - 19.2)e^{-2000t} \text{ for } t \geq 0$$


$$v_L(t) = -19.2 - 8.4e^{-2000t} \text{ for } t \geq 0$$

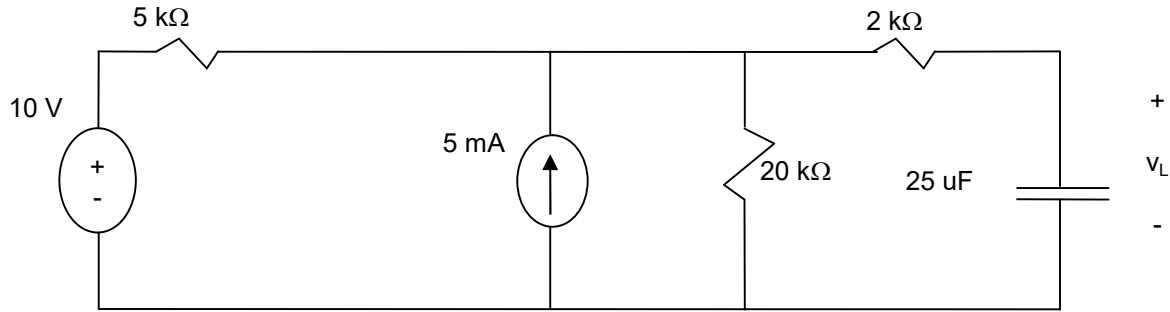5U. The following circuit has been in operation for a long time. At $t=0$, the voltage source reverses polarity and the current source drops from 5 mA to 3 mA. Find $v_L(t)$ for $t \geq 0$.



Solution:

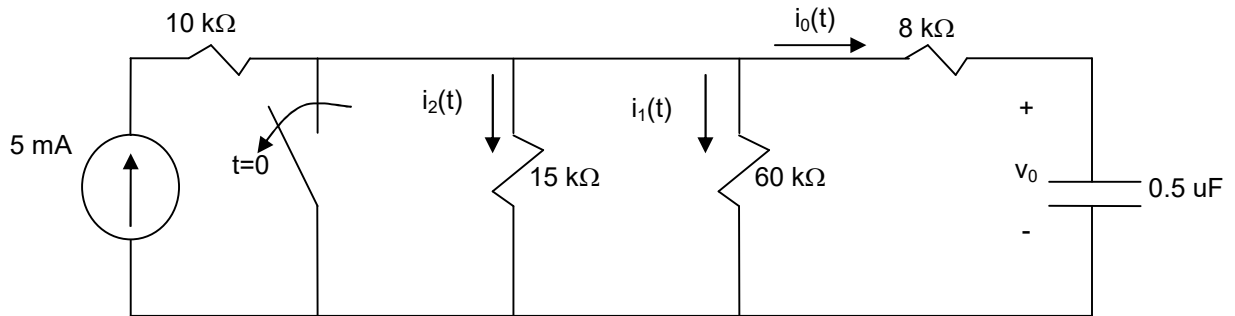6S. The switch in the following circuit has been closed a long time before opening at $t = 0$.




For $t \geq 0^+$, find:

- a) $v_0(t)$. b) $i_0(t)$. c) $i_1(t)$. d) $i_2(t)$. e) $i_1(0^+)$.

Solution:

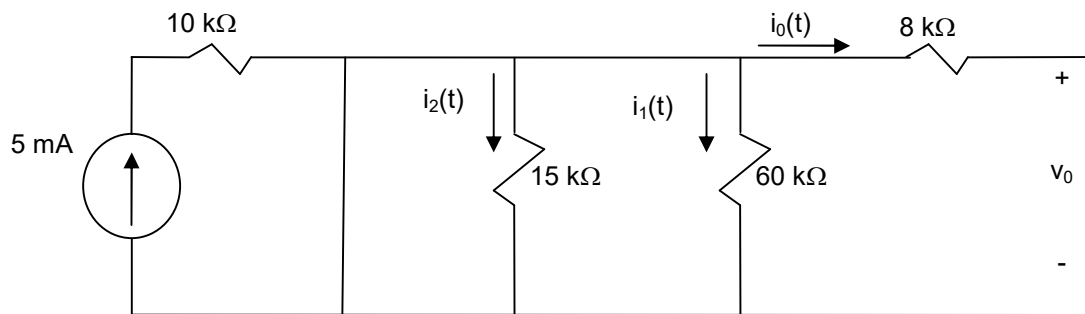a) $v_0(t)$

After a long time at $t=0^-$, capacitor appears as open...




Short across the source then no power is delivered to the rest of the circuit \rightarrow

$$v_0(0^-) = 0 \text{ V}$$


$$i_0(0^-) = i_1(0^-) = i_2(0^-) = 0 \text{ A}$$

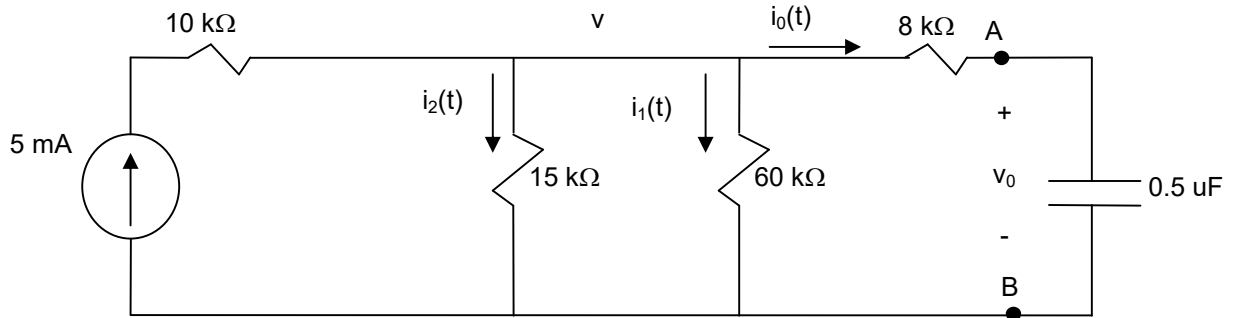After $t=0$ ($t>0$), circuit is redrawn as:




At $t=0^+$, Capacitor appears as a short $\rightarrow V_o(0^+)=0$ V.
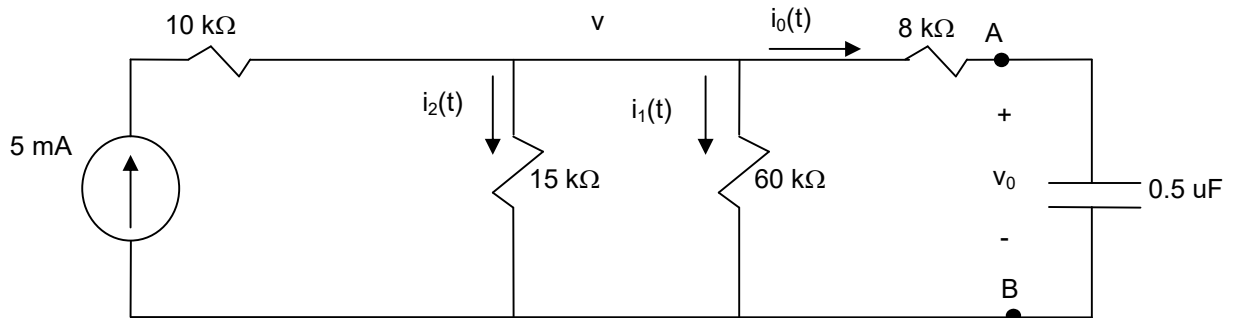
$$\text{KCL} \rightarrow -5 + v/15 + v/60 + v/8 = 0 \rightarrow 25v = 5 \cdot 120 \rightarrow v(0^+) = 24 \text{ V} \rightarrow i_0(0^+) = 3 \text{ mA}$$




Find the Norton Equivalent at terminal AB \rightarrow

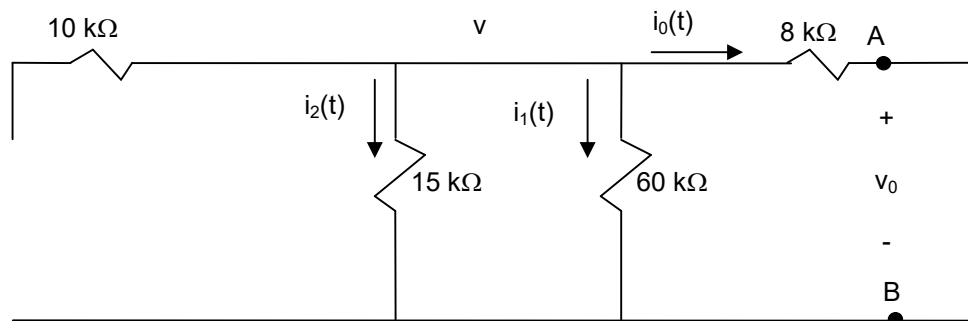Disable current source (open) to find R_{th} :




$$R_{th} = (15 \parallel 60) + 8 = 20 \text{ k}\Omega$$

Find I_{sc} :

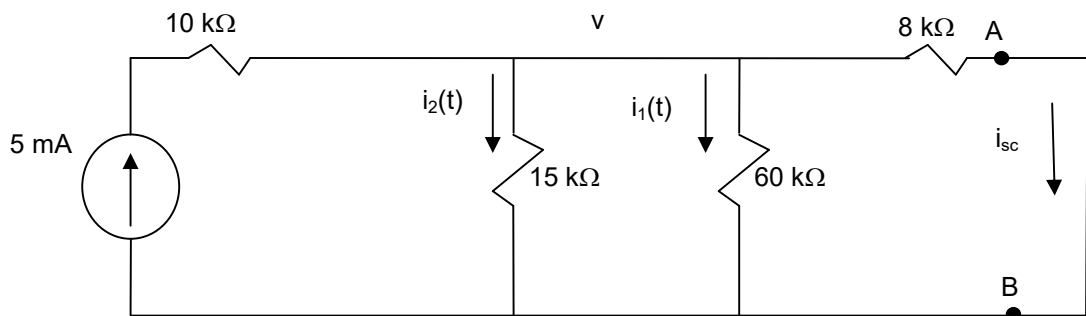
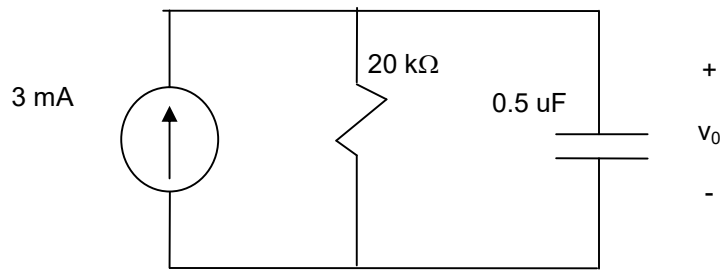
$$\text{KCL} \rightarrow -5 + v/15 + v/60 + v/8 = 0 \rightarrow 25v = 5 \cdot 120 \rightarrow v(0^+) = 24 \text{ V} \rightarrow i_{sc} = 3 \text{ mA}$$



Apply the step response for RC circuit $\rightarrow v(t) = I_s R + (V_0 - I_s R)e^{-t/RC}$ for $t \geq 0$


$$v_0(t) = 0.003 * 20,000 + (0 - 0.003 * 20,000)e^{-t/(20,000 * 0.5 * 10^{-6})} \text{ for } t \geq 0$$

$$v_0(t) = 60 - 60e^{-100t} \text{ V for } t \geq 0$$

b) $i_0(t)$

$$i_0(t) = C \frac{dv}{dt} = 0.5 * 10^{-6} * (-60) * (-100)e^{-100t} = 3e^{-100t} \text{ mA for } t \geq 0$$

c) $i_1(t)$

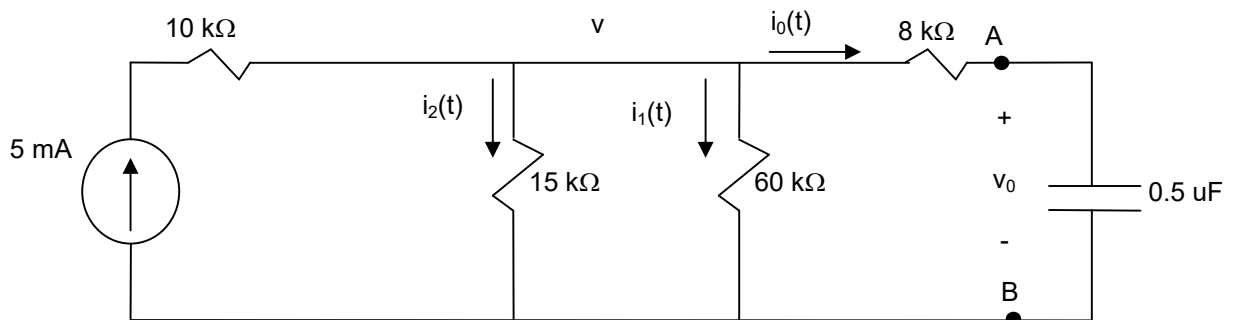

$$v(t) = 8,000 * i_0(t) + v_0(t) = 8 * 3e^{-100t} + 60 - 60e^{-100t} = 60 - 36e^{-100t} \text{ for } t \geq 0$$

$$i_1(t) = \frac{v(t)}{60,000} = 1 + 0.6e^{-100t} \text{ mA for } t \geq 0$$

d) $i_2(t)$


$$i_2(t) = \frac{v(t)}{15,000} = 4 + 2.4e^{-100t} \text{ mA for } t \geq 0$$

e) $i_1(0^+)$

$v(0^+) = 24 \text{ V}$ from earlier part.

$$i_1(0^+) = v(0^+)/60,000 = 0.4 \text{ mA}$$

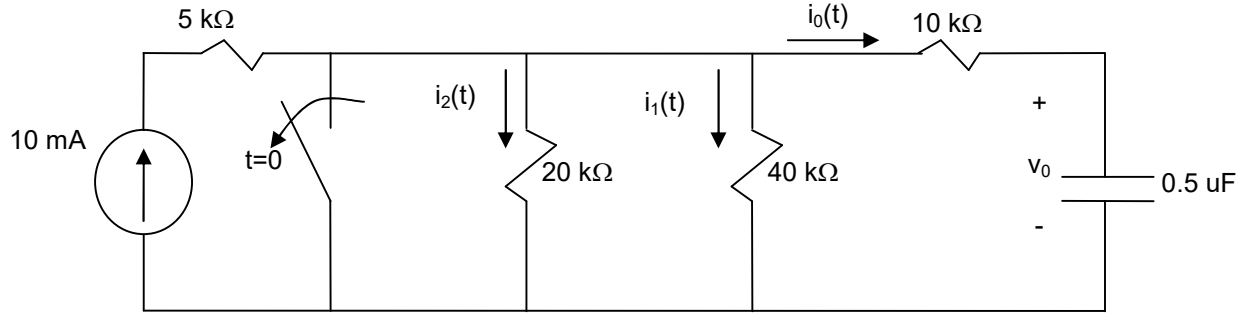6U. The switch in the following circuit has been closed a long time before opening at $t = 0$.




For $t \geq 0^+$, find:

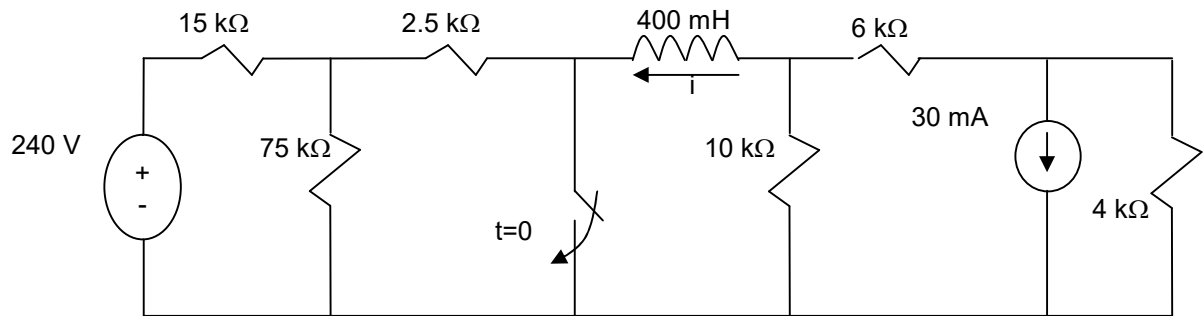- a) $v_0(t)$. b) $i_0(t)$. c) $i_1(t)$. d) $i_2(t)$. e) $i_1(0^+)$.

Solution:

7S. At $t=0$ the switch is closed in the following circuit after the switch being open for a long time.




Calculate:

- a) the initial value of i
 b) the final value of i
 c) the time constant for $t \geq 0$
 d) the numerical expression for $i(t)$ when $t \geq 0$.

Solution:

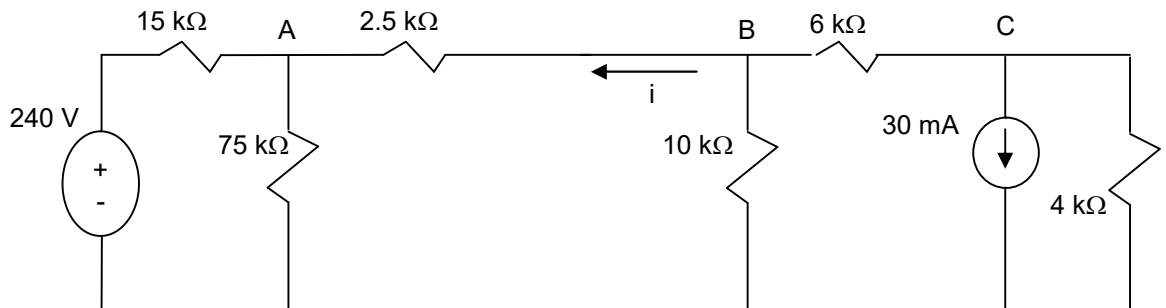- a) the initial value of i

At $t=0^-$, the inductor appears as a short since the circuit has been stabilized for a long time. The circuit can be redrawn as:



$$\text{KCL Node A} \rightarrow (V_A - 240)/15 + V_A/75 + (V_A - V_B)/2.5 = 0 \rightarrow 36V_A - 30V_B = 1200$$

$$\text{KCL Node B} \rightarrow (V_B - V_A)/2.5 + V_B/10 + (V_B - V_C)/6 = 0 \rightarrow -12V_A + 20V_B - 5V_C = 0$$


$$\text{KCL Node C} \rightarrow (V_C - V_B)/6 + 30 + V_C/4 = 0 \rightarrow -2V_B + 5V_C = -360$$

$$\text{Solve} \rightarrow V_A = 37.5\text{V}; V_B = 5\text{V}; V_C = -70\text{V}$$


$$i(0^-) = (V_B - V_A)/2.5 = (5 - 37.5)/2.5 = -13 \text{ mA} \text{ Initial value of } i$$

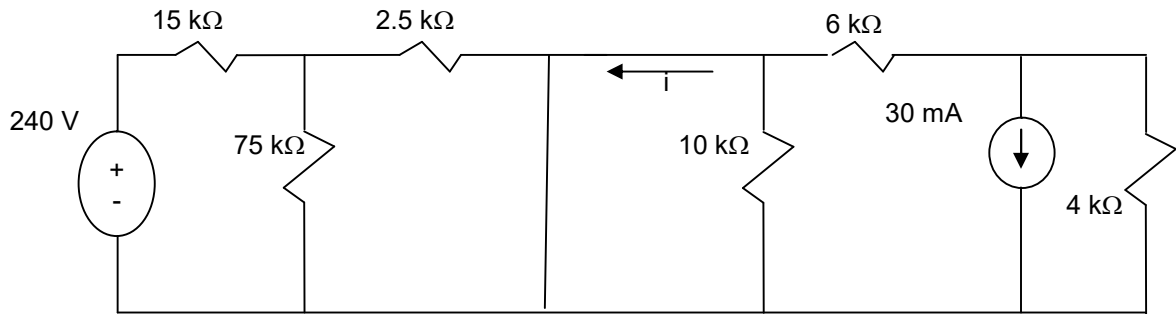b) Final value of i

At $t = \infty$, the inductor appears as a short and the circuit can be redrawn as:



Or can be redrawn as:

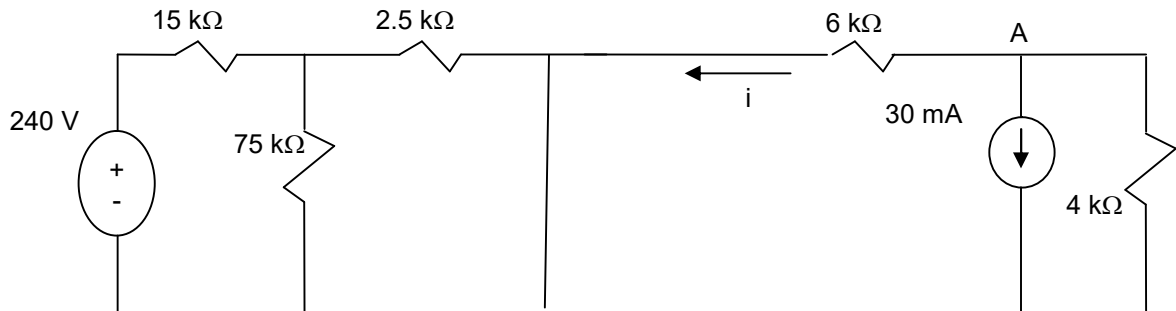


$$\text{KCL} \rightarrow V_A / 6 + 30 + V_A / 4 = 0 \rightarrow V_A = -72$$

$$i(\infty) = -72 / 6 = -12 \text{ mA}$$

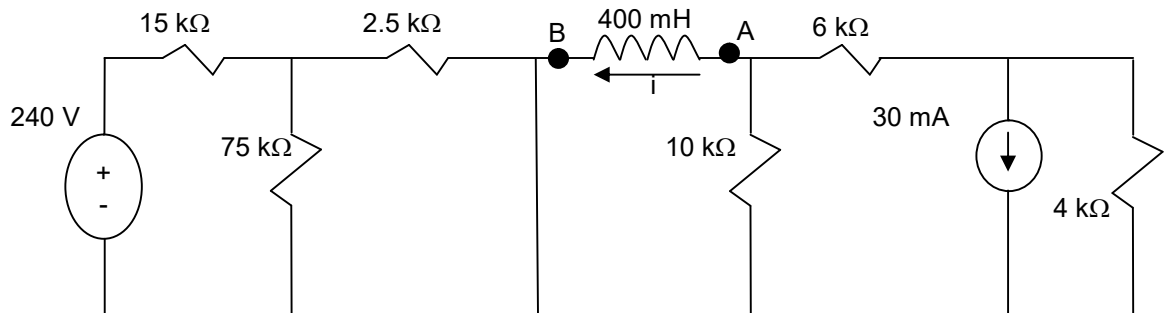
c) Time constant for $t \geq 0$

After $t=0$, the circuit may be redrawn as:




Find the Thevenin equivalent...

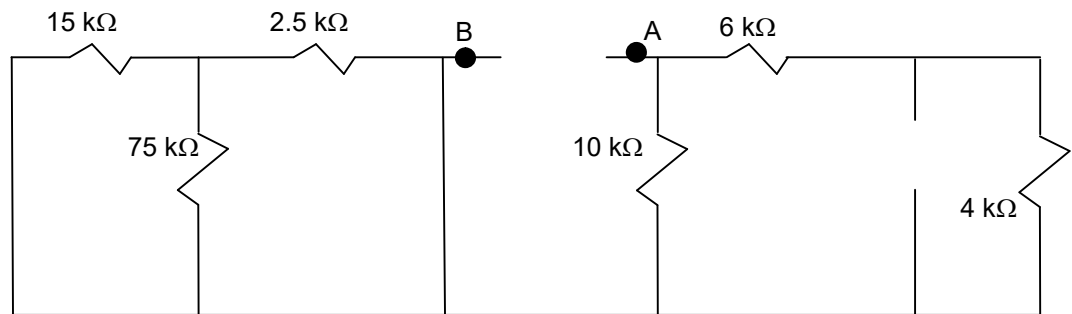Calculate R_{th} by disable the sources (short for voltage source and open for current source):


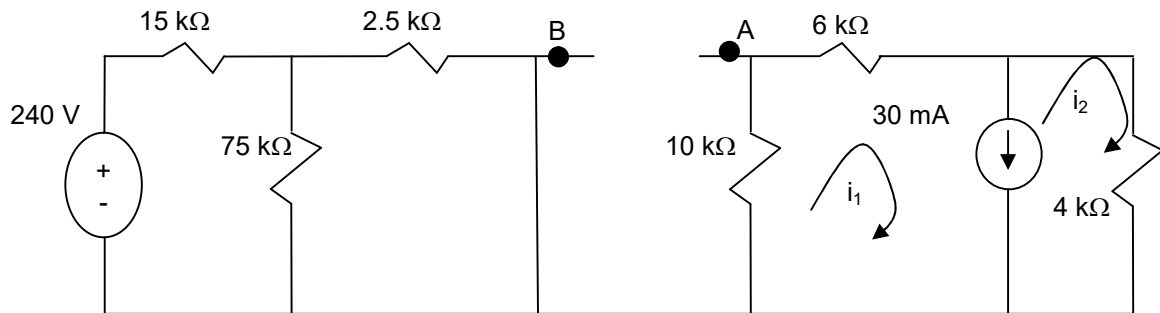
$$R_{th} = (10 \parallel (6+4)) = 5 \text{ k}\Omega$$



Choose B as the reference ($v=0$) and write the super mesh current equation:


$$10i_1 + 6i_1 + 4i_2 = 0$$

$$i_1 - i_2 = 30 \text{ mA}$$

Solve $\rightarrow i_1 = 6 \text{ mA}$

$$V_{th} = V_{oc} = V_{BA} = - (10,000)(0.006) = -60 \text{ V}$$

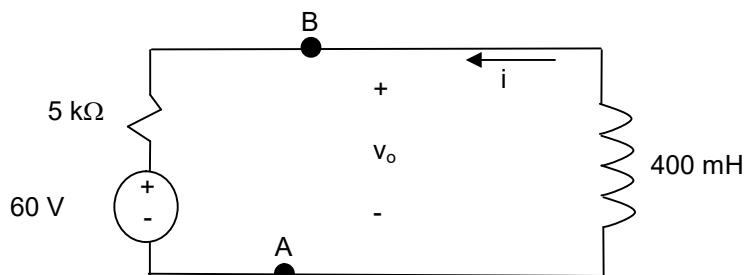Place the Thévenin Equivalent back into the circuit:




$$\text{Time Constant} = L/R = 0.4/5000/0.4 = 80 \text{ uSec}$$

d) The numerical expression for $i(t)$ when $t \geq 0$.

$$\text{Apply Step response for RL Circuit} \rightarrow i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-(R/L)t} \text{ for } t \geq 0$$

$$i(t) = -\frac{60}{5000} + \left(-0.013 - \frac{-60}{5000} \right) e^{-12,500t} = -.012 - .001e^{-12,500t} \text{ A for } t \geq 0$$

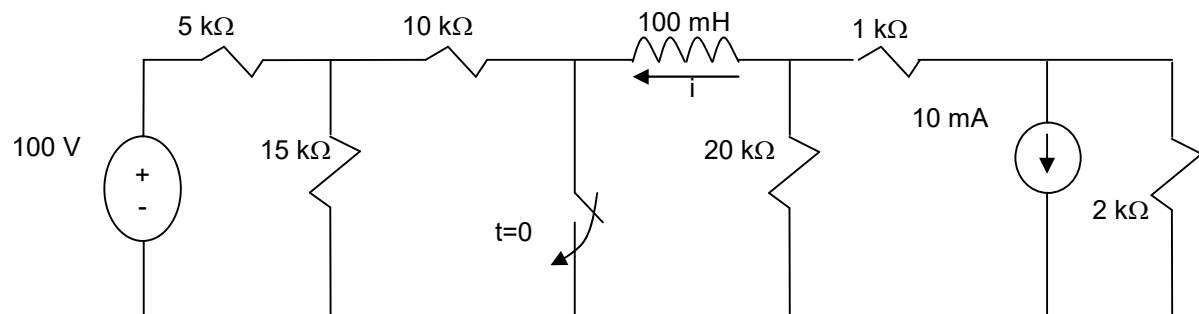7U. At $t=0$ the switch is closed in the following circuit after the switch being open for a long time.




Calculate:

- the initial value of i
- the final value of i
- the time constant for $t \geq 0$

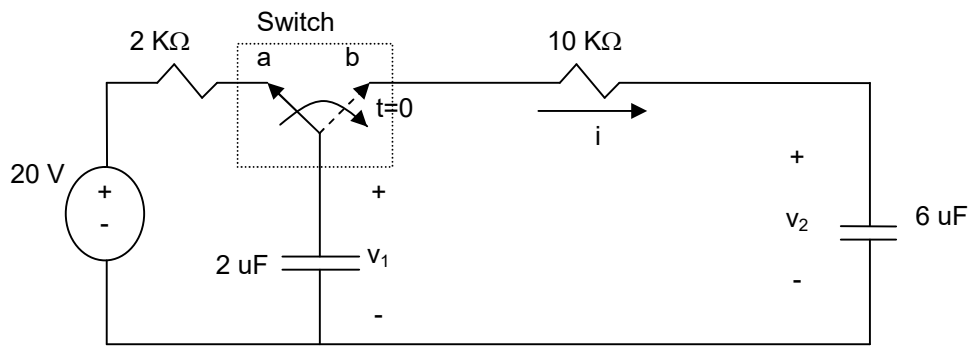d) the numerical expression for $i(t)$ when $t \geq 0$.

Solution:

8S. In the following circuit, switch has been in the “a” position for a long time. At $t=0$, the switch is moved to position “b”:




For the above circuit:

- Find the values of $i(0^+)$, $v_1(0^+)$ and $v_2(0^+)$.
- Calculate $i(t)$ for $t > 0$


Solution:

- $i(0^+) = 0$
 $v_1(0^+) = v_2(0^+) = 20 \text{ V}$

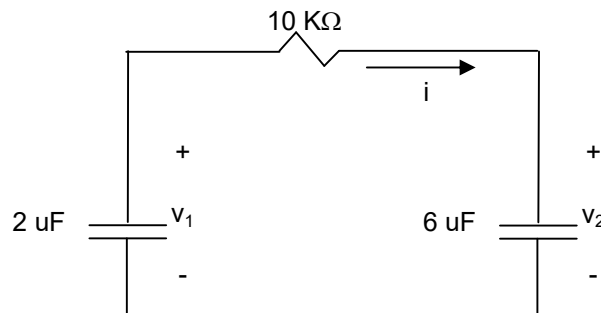- Redraw Circuit with the new switch position



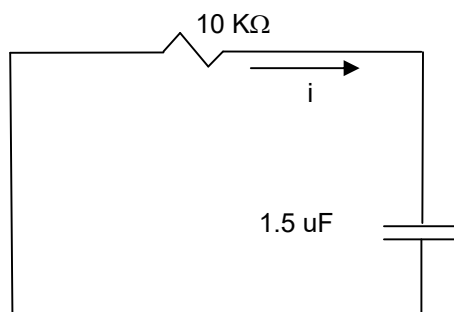
$$C_{eq} = 1/(1/2 + 1/6) = 1.5 \text{ } \mu\text{F}$$



Natural Response $\rightarrow v(t) = v(0)e^{-t/RC} = 20e^{-66.67t}$ for $t \geq 0$

$$i(t) = C \frac{dv}{dt} = (1.5 \times 10^{-6})(1333.4)e^{-66.67t} \text{ for } t \geq 0$$

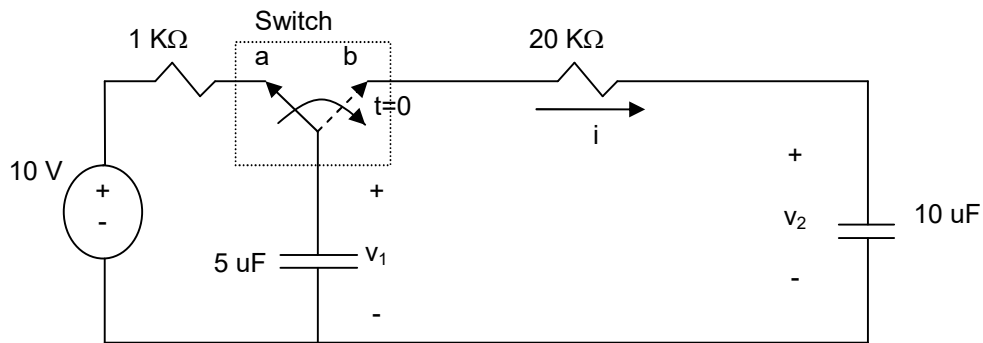8U. In the following circuit, switch has been in the “a” position for a long time. At $t=0$, the switch is moved to position “b”:



For the above circuit:

- Find the values of $i(0^+)$, $v_1(0^+)$ and $V_2(0^+)$.
- Calculate $i(t)$ for $t > 0$

Solution: