

## Fundamentals of Electrical Circuits - Chapter 9

---

- 1S. Consider the Sinusoidal Voltage  $\rightarrow v(t) = 40 \cos(100\pi t + 60^\circ) \text{ V}$
- a) What is the Maximum Amplitude of the Voltage?
  - b) What is the frequency in Hertz?
  - c) What is the frequency in Radians per second?
  - d) What is the phase angle in radians?
  - e) What is the phase angle in degrees?
  - f) What is the period in milliseconds?
  - g) What is the first time after  $t=0$  that  $v=-40 \text{ V}$ ?
  - h) The sinusoidal function is shifted  $10/3 \text{ ms}$  to the right along the time axis. What is the expression for  $v(t)$ ?
  - i) What is the minimum number of milliseconds that the function must be shifted to the right if the expression for  $v(t)$  is  $40 \sin(100\pi t)$ ?
  - j) What is the minimum number of milliseconds that the function must be shifted to the left if the expression for  $v(t)$  is  $40 \cos(100\pi t) \text{ V}$ .

**Solution:**

- a)  $V_{\max} = 40 \text{ V}$
- b)  $\omega = 2\pi f = 100\pi \rightarrow f = (100\pi)/2\pi = 50 \text{ Hz}$
- c)  $\omega = 100\pi \text{ rad./Sec.}$
- d)  $\Phi = (60^\circ)(\pi \text{ rad}/180^\circ) = \pi/3$
- e)  $\Phi = (60^\circ)$
- f)  $T = 1/f = 1/50 = 20 \text{ ms}$
- g)  $t = ?$  where  $v(t) = -40 = 40\cos(100\pi t + 60^\circ)$   
 $\cos(100\pi t + 60^\circ) = -1 = \cos((2k+1)\pi)$  where  $k = 0, 1, 2, 3, \dots$   
 $100\pi t + \pi/3 = (2k+1)\pi \rightarrow t = (2k + 1 - 1/3)/100 = (6k + 2)/300$   
first time after  $t=0$ ,  $v(t)=40$  at  $t = 2/300$  ( $K=0$ )
- h)  $\Delta t = 10/3 \text{ ms}$  "shift to the right on time axis"  
 $\Delta\Phi = \Delta t * \omega = (1/300 \text{ s})(100\pi \text{ rad/s}) = \pi/3$   
 $v_{\text{shifted}}(t) = 40\cos(100\pi t + \pi/3 - \pi/3) = 40\cos(100\pi t)$
- i) We need  $\Delta\Phi = -\pi/2 - \pi/3 = -5\pi/6$  (to convert sine to cosine and then shift to zero)  
Now convert to time from radian  
 $\Delta t = \Delta\Phi / \omega = (-5\pi/6) / (100\pi) = -5/600 = -8.33 \text{ ms}$  (negative indicates shift to the right)
- j) We need go forward by  $2\pi$  to find the left shift in other word add  $2\pi$  to the  $\Delta\Phi$  in section i.  
 $\Delta\Phi = 2\pi - 5\pi/6 = 7\pi/6$  (to convert cosine to sine and then shift to zero)  
Now convert to time from radian  
 $\Delta t = \Delta\Phi / \omega = (7\pi/6) / (100\pi) = 7/600 = 11.67 \text{ ms}$  (positive indicates shift to the left)


- 
- 1U. Consider the Sinusoidal Voltage  $\rightarrow v(t) = 15 \cos(250\pi t + 75^\circ) \text{ V}$
- a) What is the Maximum Amplitude of the Voltage?
  - b) What is the frequency in Hertz?
  - c) What is the frequency in Radians per second?
  - d) What is the phase angle in radians?
  - e) What is the phase angle in degrees?
  - f) What is the period in milliseconds?
  - g) What is the first time after  $t=0$  that  $v=-10 \text{ V}$ ?

- h) The sinusoidal function is shifted 10/3 ms to the right along the time axis. What is the expression for  $v(t)$ ?
- i) What is the minimum number of milliseconds that the function must be shifted to the right if the expression for  $v(t)$  is  $15 \sin(250\pi t)$
- j) What is the minimum number of milliseconds that the function must be shifted to the left if the expression for  $v(t)$  is  $15 \cos(250\pi t)$  V.

**Solution:**

2S. The Voltage applied to the circuit shown below at  $t=0$  is  $20 \cos(800t + 25^\circ)$ . The circuit resistance is  $80 \Omega$ , and the initial current in the 75 mh inductor is zero.

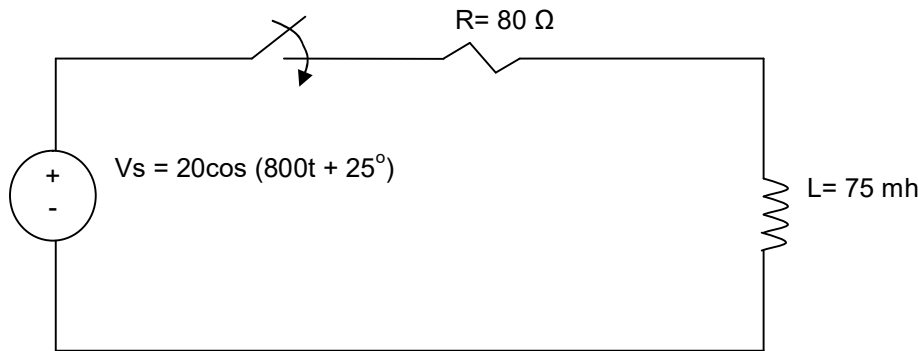- a) Find  $i(t)$  for  $t \geq 0$ .
- b) Write the expression for the transient and steady state component of  $i(t)$ .
- c) Find the numerical value of  $I$  after the switch has been closed for 1.875 ms.
- d) What are the maximum amplitude, frequency (rad./s), and phase angle of the steady state current?
- e) By how many degrees are the voltage and steady state current out of phase?



**Solution:**

- a) Since Here we are asked to find the total response  $i(t)$ , we can use the following equation where the first term is the transient component and second term is the steady state component.

$$i(t) = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-(R/L)t} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta) \quad \text{where } \theta = \tan^{-1}(\omega L / R)$$

$$\omega = 800, \quad \phi = 25^\circ, \quad V_m = 20 \quad V$$

$$\theta = \tan^{-1}(800 * 0.075 / 80) = 36.87^\circ$$

$$i(t) = \frac{-20}{\sqrt{80^2 + 800^2 (.075)^2}} \cos(25^\circ - 36.87^\circ) e^{-(80/0.075)t} + \frac{20}{\sqrt{80^2 + 800^2 (.075)^2}} \cos(800t + 25^\circ - 36.87^\circ)$$

$$i(t) = -0.2 \cos(-11.87^\circ) e^{-1066.67t} + 0.2 \cos(800t - 11.87^\circ)$$

b)

$$\text{Transient part of } i(t) = i(t) = -0.2 \cos(-11.87^\circ) e^{-1066.67t}$$

$$\text{Steady State part of } i(t) = +0.2 \cos(800t - 11.87^\circ)$$

c) Numerical value of  $I(t=1.875 \text{ ms})$

$$i(1.875 \text{ ms}) = -0.2 \cos(-11.87^\circ) e^{-(1066.67 * 1.875 / 1000)} + 0.2 \cos(800 * 1.875 / 1000 - 11.87^\circ * \pi / 180)$$


$$i(1.875 \text{ ms}) = 173.46 \text{ ma}$$

- d) For steady state part:  
 Maximum Amplitude =  $I_{\text{max}} = 0.2$   
 Angular Frequency (Rad/s) =  $\omega = 800 \text{ rad/sec.}$   
 Phase Shift =  $\Phi = -11.87^\circ$

e) Phase difference =  $25 - (-11.87) = 36.87^\circ$

2U. The Voltage applied to the circuit shown below at  $t=0$  is  $10\cos(120t + 60^\circ)$ . The circuit resistance is  $100 \Omega$ , and the initial current in the  $10 \text{ mh}$  inductor is zero.

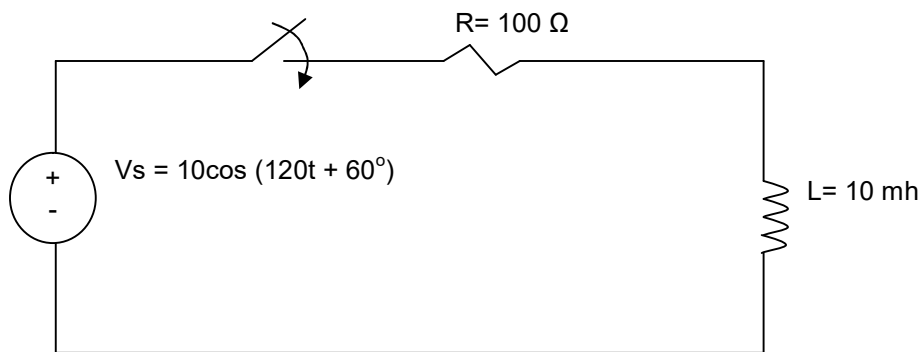
- a) Find  $i(t)$  for  $t \geq 0$ .  
 b) Write the expression for the transient and steady state component of  $i(t)$ .  
 c) Find the numerical value of  $I$  after the switch has been closed for  $2 \text{ ms}$ .  
 d) What are the maximum amplitude, frequency (rad./s), and phase angle of the steady state current?  
 e) By how many degrees are the voltage and steady state current out of phase?



**Solution:**

3S. Write the time domain equation and phasor Polar, Rectangular and Angular forms for the following Signals (use  $\omega=3000 \text{ rad/sec.}$  if not provided)

a)

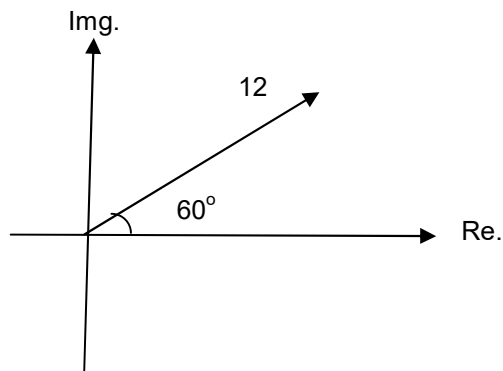

- b)  $X = 20 e^{j\pi/3}$   
 c)  $x(t) = 25 \cos(300\pi t + \pi/3)$


**Solution:**

Part	Time Domain	Angular	Polar	Rectangular
------	-------------	---------	-------	-------------

<b>a</b>	$12\cos(3000t + \pi/3)$	$12 \angle \pi/3$	$12e^{j\pi/3}$	$6 + j10.4$
<b>b</b>	$20\cos(3000t + \pi/3)$	$20 \angle \pi/3$	$20e^{j\pi/3}$	$6 + j17.32$
<b>c</b>	$25 \cos(300\pi t + \pi/3)$	$25 \angle \pi/3$	$25e^{j\pi/3}$	$12.5 + j21.65$

3U. Write the time domain equation and phasor Polar, Rectangular and Angular forms for the following Signals (use  $\omega=3000$  rad/sec. if not provided)

a)

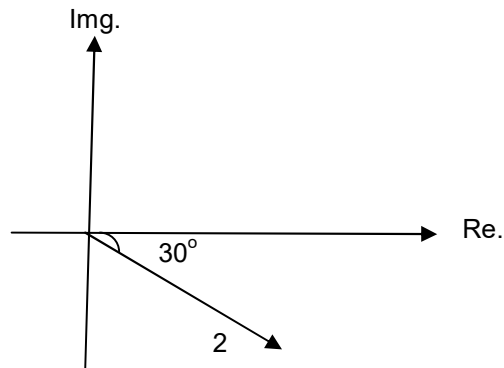

b)  $X = 25 e^{j\pi/4}$

c)  $X = 4 e^{-j\pi/3}$

d)  $x(t) = 25 \cos(300\pi t + \pi/3)$

e)  $x(t) = 10 \sin(500\pi t + \pi/2)$

f)  $X = 3 \angle 2\pi/3$

g)  $X = 25 + j32$


h)  $x(t) = 20 \cos(30\pi t + 6\pi/3)$

**Solution:**

4S. A 1000 Hz Sinusoidal voltage with a maximum amplitude of 200 V at  $t=0$  is applied across the terminals of an inductor. The maximum amplitude of the steady-state current in the inductor is 25 A.

- What is the frequency of the inductor current?
- What is the phase angle of the voltage?
- What is the phase angle of the current?
- What is the inductive reactance of the inductor?
- What is the inductance of the inductor in millihenrys?
- What is the impedance of the inductor?

**Solution:**

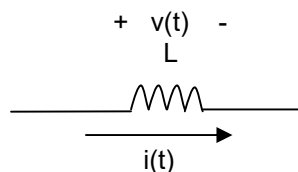

- Frequency =  $f = 1000$  Hz (same as voltage)
- Since the maximum amplitude of voltage occurs at  $t=0$  then phase of voltage is 0  
 $\Phi_v = 0$
- We know the Inductor shift current by  $-\pi/2$  rad compared to voltage  $\rightarrow$   
Current Phase Shift =  $\Phi_i = 0 - \pi/2 = -\pi/2$


- d) Inductive reactance =  $\omega L = ?$   
 $Z = V/I \rightarrow \omega L = V_{\max}/I_{\max} = 200/25 = 8 \Omega$  (reactance)
- e)  $\omega = 2\pi f = 2000\pi$   
 $\omega L = (2000\pi) L = 8 \rightarrow L = 1.27 \text{ mH}$
- f) Impedance of inductor =  $Z = j\omega L = j8 \Omega$

- 4U. A 2500 Hz Sinusoidal voltage with a maximum amplitude of 80 V at  $t=0$  is applied across the terminals of an inductor. The maximum amplitude of the steady-state current in the inductor is 10 A.
- What is the frequency of the inductor current?
  - What is the phase angle of the voltage?
  - What is the phase angle of the current?
  - What is the inductive reactance of the inductor?
  - What is the inductance of the inductor in millihenrys?
  - What is the impedance of the inductor?

**Solution:**

- 5S. A 50 kHz sinusoidal voltage has zero phase angle and a maximum amplitude of 10 mV. When this voltage is applied across the terminals of a capacitor, the resulting steady-state current has a maximum amplitude of 628.32  $\mu\text{A}$ .
- What is the frequency of the current in radians per second?
  - What is the phase angle of the current?
  - What is the capacitive reactance of the capacitor?
  - What is the capacitance of the capacitor in microfarads?
  - What is the impedance of the capacitor?

**Solution:**

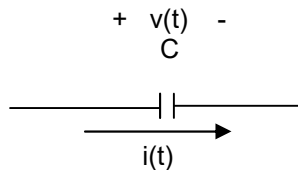

- Angular Frequency (rad/s) =  $\omega = 2\pi f = 2\pi(50,000) = 100,000\pi$  rad/sec
- Phase Angle =  $\Phi_i = \pi/2$  Since Current is  $+\pi/2$  shift from voltage (current leads the voltage by  $\pi/2$ )
- Capacitive reactance =  $1/\omega C = V_{\max}/I_{\max}$   
 $1/\omega C = (10 \times 1000)/628.32 = 15.92 \Omega$
- $-1/\omega C = -15.92 \rightarrow C = 1/(15.92 \times 100,000\pi) = 0.2 \mu\text{F}$
- Impedance of the capacitor =  $Z = j(-1/\omega C) = -j15.92 \Omega$

- 5U. A 15 kHz sinusoidal voltage has  $45^\circ$  phase angle and a maximum amplitude of 50 mV. When this voltage is applied across the terminals of a capacitor, the resulting steady-state current has a maximum amplitude of 250  $\mu\text{A}$ .
- What is the frequency of the current in radians per second?
  - What is the phase angle of the current?
  - What is the capacitive reactance of the capacitor?

- d) What is the capacitance of the capacitor in microfarads?  
e) What is the impedance of the capacitor?

**Solution:**

6S. Convert Steady State current  $i(t) = 10 \cos(150t - \pi/3)$  to Phasor Domain and write out the equivalent current in Angular, Polar and Rectangular forms. Also draw the Phasor representation of this signal.

**Solution**


$$i(t) = 10 \cos(150t - \pi/3) = 10 \cos(150t - \pi/3) \rightarrow \omega = 150 \text{ rad/sec; Phase} = -\pi/3; V_{\max} = 10\text{v}$$

$$\text{Angular Form} \rightarrow 10 \angle -\pi/3$$

$$\text{Polar Form} \rightarrow 10 e^{-j\pi/3}$$

$$\text{Rectangular Form} \rightarrow 10\cos(-\pi/3) + j10\sin(-\pi/3) = 5 - j8.6$$

Phasor Diagram  $\rightarrow$

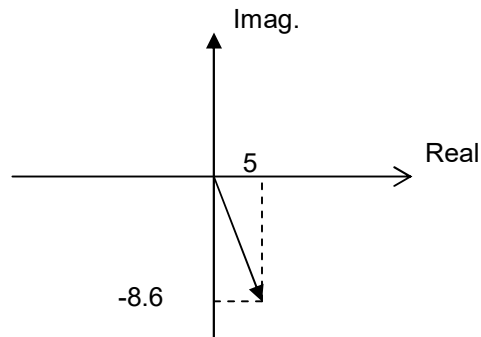

6U. Convert Steady State current  $i(t) = 30 \cos(200t + \pi/6)$  to Phasor Domain and write out the equivalent current in Angular, Polar and Rectangular forms. Also draw the Phasor representation of this signal.

**Solution**

6Sb. Convert Steady State voltage  $v(t) = 25 \sin(2000t + \pi/8)$  to Phasor domain and write out the equivalent voltage in Angular, Polar and Rectangular forms.

**Solution:**

$$V(t) = 25 \sin(2,000t + \pi/8) \text{ Need to convert to cosine by } (-\pi/2 \text{ shift})$$

$$V(t) = 25 \cos(2,000t + \pi/8 - \pi/2) = 25 \cos(2,000t - 3\pi/8) \rightarrow \omega = 2,000 \text{ rad/sec; Phase} = -3\pi/8; V_{\max} = 25\text{v}$$


$$\text{Angular Form} \rightarrow 25 \angle -3\pi/8$$

$$\text{Polar Form} \rightarrow 25 e^{-j3\pi/8}$$

$$\text{Rectangular Form} \rightarrow 25\cos(-3\pi/8) + j25\sin(-3\pi/8) = 9.6 - j23.1$$


7S. Draw the phasor-domain equivalent circuit of the circuit shown below. Also identify the currents with the largest and the smallest magnitude among the three parallel branch currents ( $I_1$ ,  $I_2$ ,  $I_3$ )

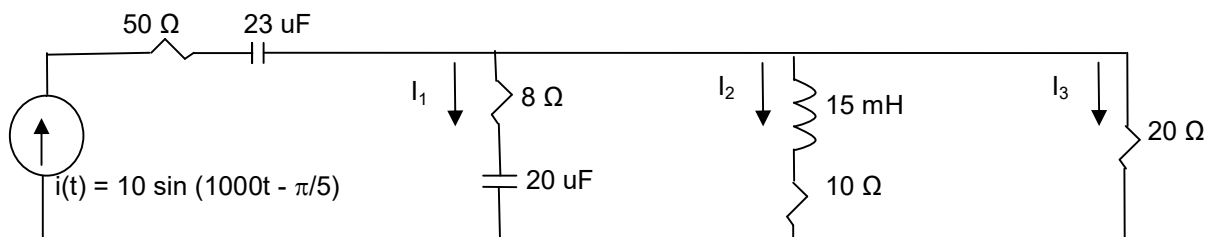*Hint: Finding the exact value of  $I_1$ ,  $I_2$  and  $I_3$  is not required.*



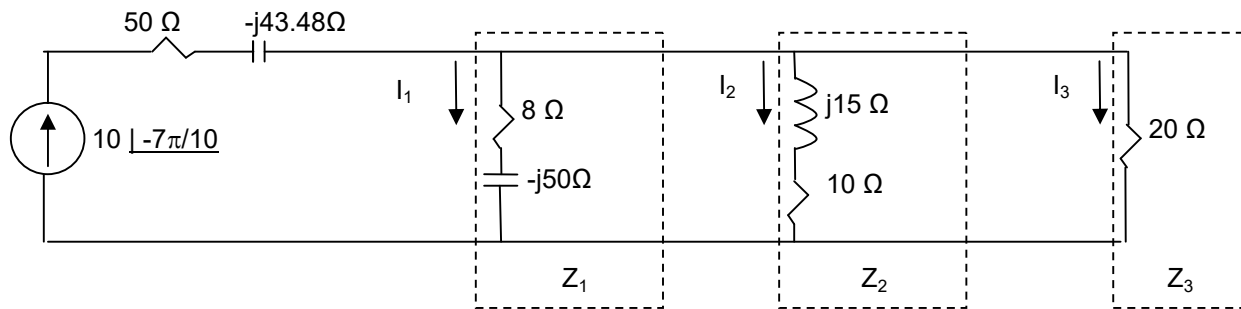**Solution**

Step 1. Covert to Phasor Domain (  $C \rightarrow 1/j\omega C$ ;  $L \rightarrow j\omega L$ ;  $R \rightarrow R$  )  
 $\omega = 1000$




This is a current divider when  $I_n$  is inversely proportional to  $Z_n$

$$|Z_1| = \sqrt{8^2 + 50^2} = 50.7\Omega \quad \text{Largest Impedance therefore Smallest current } |I_1|$$

$$|Z_3| = 20\Omega \quad \text{Middle value Impedance therefore middle value current } |I_3|$$

$$|Z_2| = \sqrt{10^2 + 15^2} = 18.03\Omega \quad \text{Smallest Impedance therefore Largest current } |I_2|$$

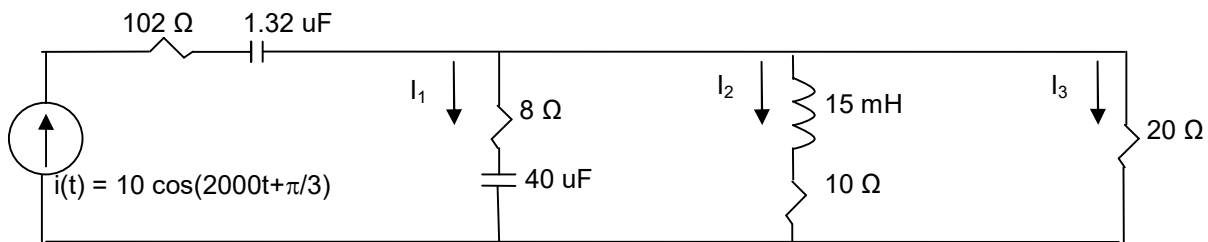7U. Draw the Phasor domain equivalent of the circuit shown below. Also identify the currents with the largest and the smallest magnitude among the three parallel branch currents ( $I_1$ ,  $I_2$ ,  $I_3$ )




**Solution:**

8S. A  $10\ \Omega$  resistor and a  $5\ \mu\text{F}$  Capacitor are connected in parallel. This parallel combination is also in parallel with the series combination of an  $8\ \Omega$  resistor and an  $300\ \mu\text{H}$  inductor. These three parallel branches are driven by a sinusoidal current source whose current is  $922\cos(20,000t + 30^\circ)\ \text{A}$ .

- Draw the Frequency-domain equivalent circuit.
- Reference the voltage across the current source as a rise in the direction of the source current, and find the phasor voltage.
- Find the steady-state expression for  $v(t)$ .

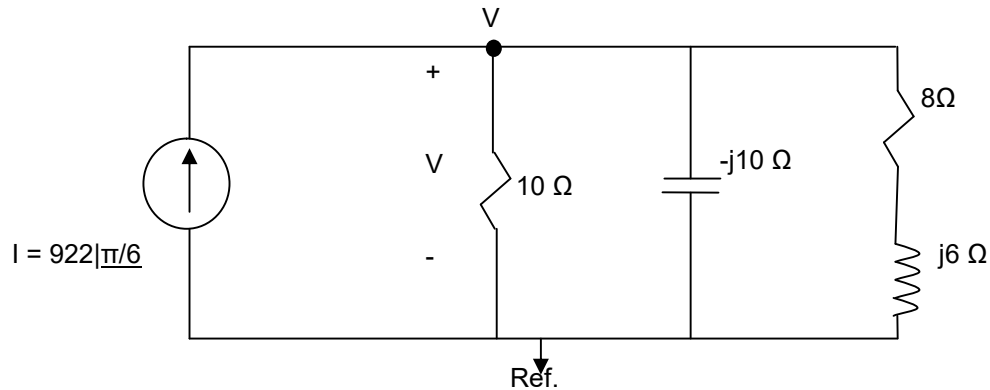**Solution:**

- Note ( $R \rightarrow R$ ,  $L \rightarrow j\omega L$ ,  $C \rightarrow 1/j\omega C = -j/\omega C$  where  $\omega = 20,000$ )



- To find  $V$ , use Node-Voltage method and write the KCL equation for node  $V$

First write the  $I$  in Rectangular form  $\rightarrow I = 922\cos(\pi/6) + j922\sin(\pi/6) = 798.48 + j461$

Now the KCL for  $V$

$$-(798.48 + j461) + V/10 + V/(-j10) + V/(8 + j6) = 0$$

$$V = (798.48 + j461) / (1/10 + j/10 + 1/(8 + j6)) = 4769.6 + j1501.2 \text{ (rectangular- Phasor form)}$$

$$\text{Amplitude} = V_{\text{max}} = \sqrt{4769.6^2 + 1501.2^2} = 5000.2 \text{ V}$$

$$\text{Phase} = \Phi = \tan^{-1}\left(\frac{1501}{4769.6}\right) = 0.3 \text{ Rad. or } 17.5^\circ$$

$$V = 5000 \angle 17.5^\circ$$

- Steady State  $v(t) = 5000\cos(20,000t + 17.5^\circ)$

8U. A  $20\ \Omega$  resistor and a  $50\ \mu\text{F}$  Capacitor are connected in parallel. This parallel combination is also in parallel with the series combination of an  $50\ \Omega$  resistor and an  $200\ \mu\text{H}$  inductor. These three parallel branches are driven by a sinusoidal current source whose current is  $120\cos(10,000t + 45^\circ)\ \text{A}$ .

- Draw the Frequency-domain equivalent circuit.
- Reference the voltage across the current source as a rise in the direction of the source current, and find the phasor voltage.
- Find the steady-state expression for  $v(t)$ .


**Solution:**



- 9S. A  $40\ \Omega$  resistor, a  $5\text{ mH}$  inductor and a  $1.25\ \mu\text{F}$  capacitor are connected in series. The series-connected elements are energized by a sinusoidal voltage source whose voltage is  $600 \cos(8000t + 20^\circ)\text{ V}$ .
- Draw the frequency-domain equivalent circuit.
  - Reference the current in the direction of the voltage rise across the source, and find the phasor current.
  - Find the steady state expression for  $i(t)$ .

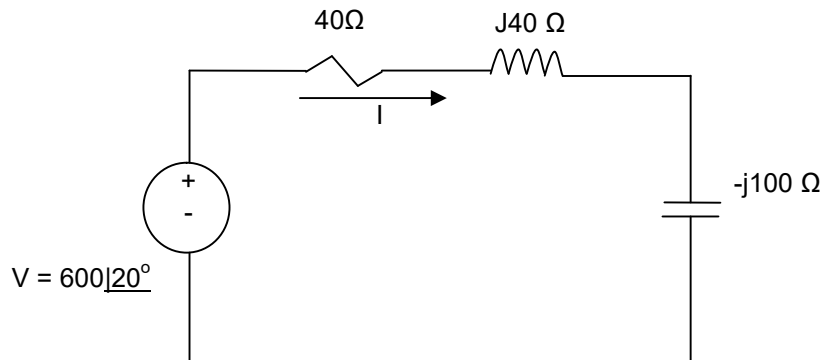**Solution:**

- Note:  $R \rightarrow R$ ,  $L \rightarrow j\omega L$ ,  $C \rightarrow 1/j\omega C = -j/\omega C$  where  $\omega = 8,000$



- $I = V/Z$   
If we write  $Z$  also in angular form then we can divide magnitudes and subtract phase to get the angular form of  $I$

$$Z = (40 + j40 - j100) = (40 - j60) = \sqrt{40^2 + 60^2} \angle \tan^{-1}\left(-\frac{60}{40}\right) = 72.11 \angle -56.31^\circ$$

$$I = (600\angle 20^\circ) / (72.11 \angle -56.31^\circ) = (600/72.11) \angle (20 - (-56.31))^\circ$$


$$I = 8.32 \angle 76.31^\circ\text{ A}$$

- Steady State  $i(t) = 8.32 \cos(8,000t + 76.31^\circ)\text{ A}$

- 9U. A  $40\ \Omega$  resistor, a  $5\text{ mH}$  inductor and a  $1.25\ \mu\text{F}$  capacitor are connected in series. The series-connected elements are energized by a sinusoidal voltage source whose voltage is  $600 \cos(8000t + 20^\circ)\text{ V}$ .
- Draw the frequency-domain equivalent circuit.
  - Reference the current in the direction of the voltage rise across the source, and find the phasor current.
  - Find the steady state expression for  $i(t)$ .

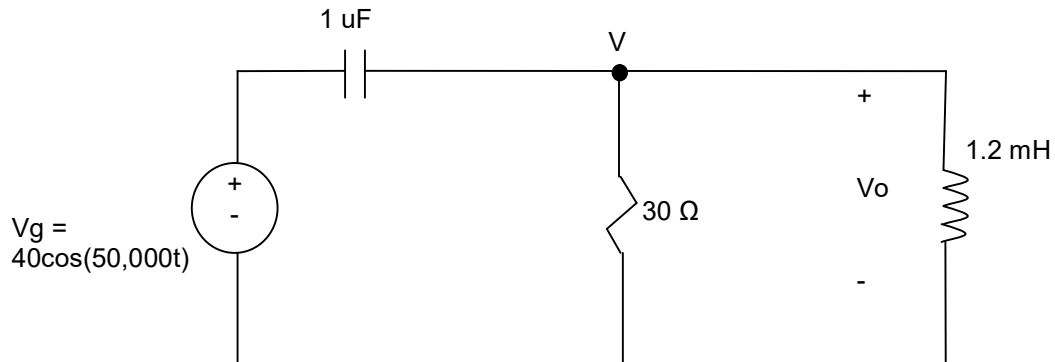**Solution:**


- 10S. The Circuit in the following figure is operating in the sinusoidal steady state. Find the steady-state expression for  $v_o(t)$  if  $v_g(t) = 40 \cos(50,000t)$  V.



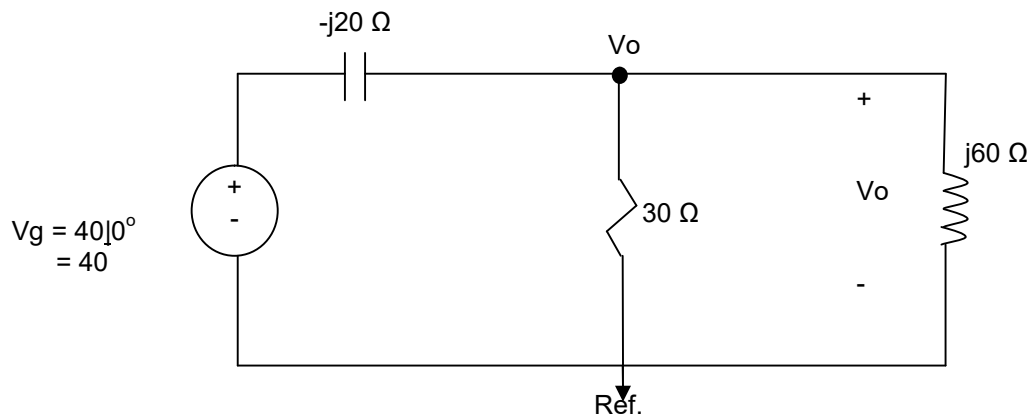**Solution:**

Step 1) Convert the circuit to Frequency domain using phasor transformation

Note ( $R \rightarrow R$ ,  $L \rightarrow j\omega L$ ,  $C \rightarrow 1/j\omega C = -j/\omega C$  where  $\omega = 50,000$ )



Step 2) Decide on Analysis method, Node Voltage is the simplest approach with 1 KCL equation


So write the KCL for Node  $V_o$

$$(V_o - 40) / -j20 + V_o / 30 + V_o / j60 = 0$$

$$V_o = (-40/j20) / (1/-j20 + 1/30 + 1/j60) = 30 + j30 = 42.43 \angle 45^\circ$$


$$\text{Steady State expression} \rightarrow v(t) = 42.43 \cos(50,000t + 45^\circ)$$

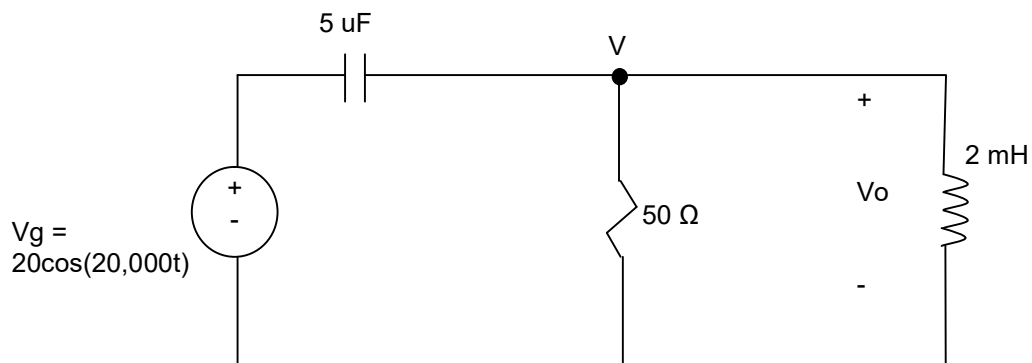- 10U. The Circuit in the following figure is operating in the sinusoidal steady state. Find the steady-state expression for  $v_o(t)$  if  $v_g(t) = 20 \cos(20,000t)$  V.



**Solution:**

- 11S. Find the Thevenin equivalent circuit with respect to the terminals a, b for the circuit shown in the following figure.

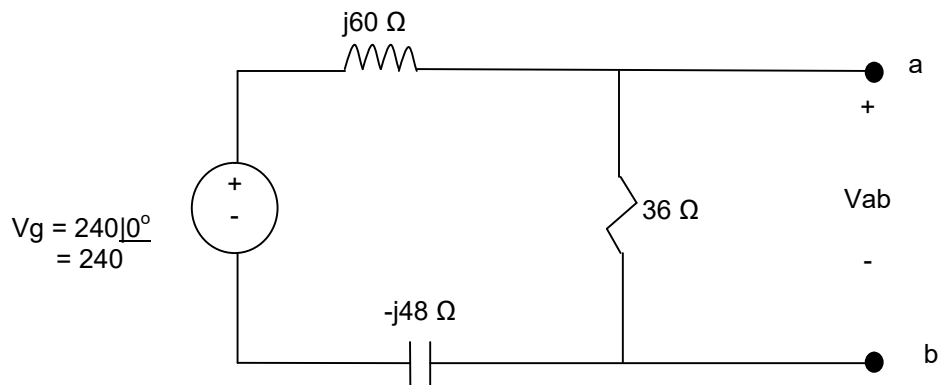**Solution:**

Step 1) Find the  $V_{oc} = V_{th}$

You could look at this circuit as voltage divider where

$$V_{th} = V_{oc} = V_{ab} = (240 / (j60 + 36 - j48)) * 36 = 8640 / (36 + j12)$$


If we rewrite the bottom as a angular form phase then we can divide amplitudes and subtract phases

$$36 + j12 = \sqrt{36^2 + 12^2} \angle \tan^{-1}\left(\frac{12}{36}\right) = 37.95 \angle 18.43^\circ$$

$$V_{th} = (8640 \angle 0^\circ) / (37.95 \angle 18.43^\circ) = (8640/37.95) \angle (0-18.43)^\circ$$


$$V_{th} = 227.668 \angle -18.43^\circ$$

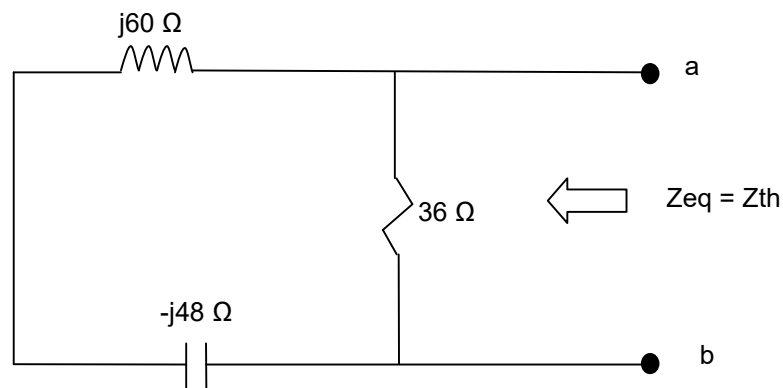Step 2) Find the  $R_{th} = R_{eq}$  when all independent sources are deactivated




$$Z_{th} = 1 / (1 / (j60 - j48) + 1 / 36) = 3.6 + j10.8$$

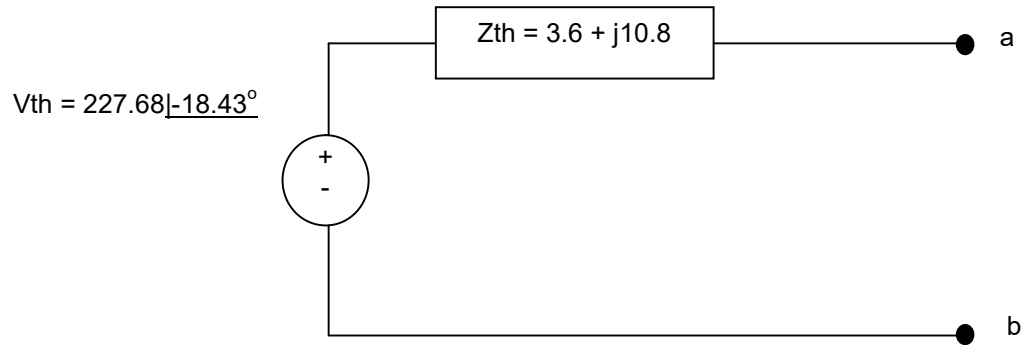Step 3) Draw the Thevenin Equivalent Circuit



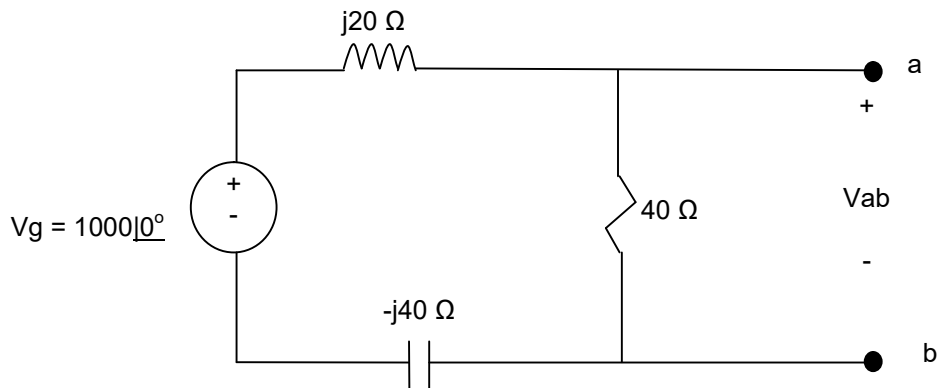11U. Find the Thevenin equivalent circuit with respect to the terminals a, b for the circuit shown in the following figure.




**Solution:**

12S. Use the mesh-current method to find the steady-state expression for the voltage  $v_o(t)$  for the circuit shown below when:

$$v_{g1} = 20 \cos(2000t - 36.87^\circ) \text{ V}$$
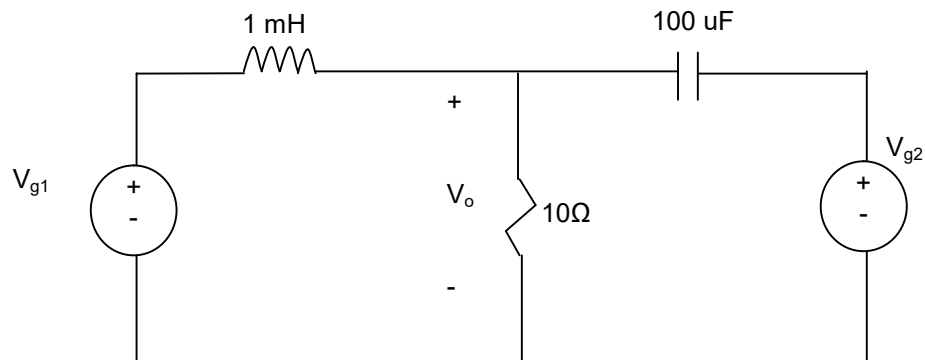
$$v_{g2} = 50 \sin(2000t - 16.26^\circ) \text{ V}$$




**Solution:**

Step 1) Convert  $v_{g2}$  to Cosine standard form by subtraction  $90^\circ$  from the phase.:

$$v_{g2} = 50 \sin(2000t - 16.26^\circ) = 50 \cos(2000t - 106.26^\circ)$$

Step 2) Convert the circuit to Frequency domain using phasor transformation

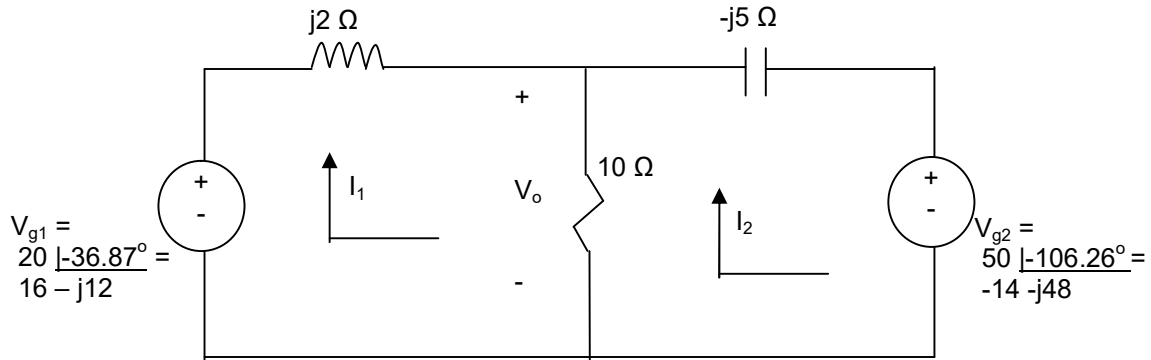Note ( $R \rightarrow R$ ,  $L \rightarrow j\omega L$ ,  $C \rightarrow 1/j\omega C = -j/\omega C$  where  $\omega = 2000$ )



Step 3) Write the KVL equations for the two meshes:

$$\text{Mesh 1} \rightarrow -(16 - j12) + j2I_1 + 10(I_1 - I_2) = 0$$

$$\text{Mesh 2} \rightarrow (-14 - j48) - j5I_2 + 10(I_2 - I_1) = 0$$

From Mesh 1 equation find  $I_2$  in term of  $I_1$ , plug the expression in Mesh 2 equation for  $I_2$

$$I_1 = -6 + j10$$

$$I_2 = -9.6 + j10$$

Step 4) Find the  $V_o$


$$V_o = (I_1 - I_2) \cdot 10 = (3.6 \cdot 10) = 36 \angle 0^\circ$$

$$v(t) = 36 \cos(2000t)$$

12U. Use the mesh-current method to find the steady-state expression for the voltage  $v_o(t)$  for the circuit shown below when:

$$v_{g1} = 10 \cos(1000t - 30^\circ) \text{ V}$$
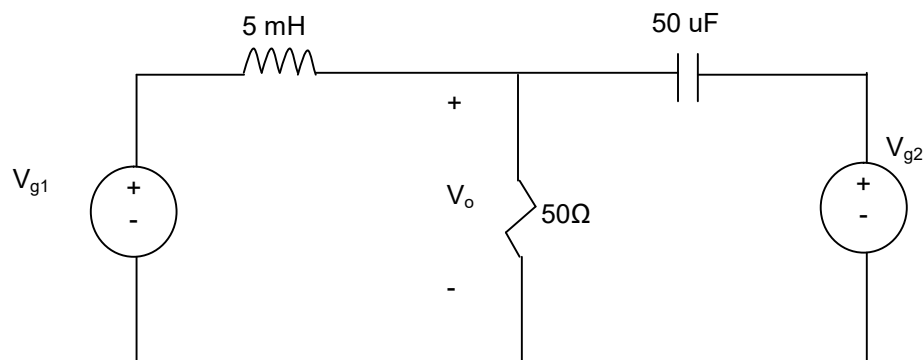
$$v_{g2} = 20 \sin(1000t - 45^\circ) \text{ V}$$



**Solution:**


13S. The parameters in the circuit shown below are  $R_1 = 0.1 \Omega$ ,  $\omega L_1 = 0.8 \Omega$ ,  $R_2 = 24 \Omega$ ,  $\omega L_2 = 32 \Omega$  and  $V_L = 240 + j0$ .

a) Calculate the phasor voltage  $V_s$ .

b) Connect a capacitor in parallel with the inductor  $L_2$ , hold  $V_L$  constant, and adjust the capacitor until the magnitude of  $I$  is a minimum. What is the capacitive reactance? What is the Value of  $V_s$ ?

c) Find the value of the capacitive reactance that keeps the magnitude of  $I$  as small as possible while

$$|V_s| = |V_L| = 240 \text{ V.}$$

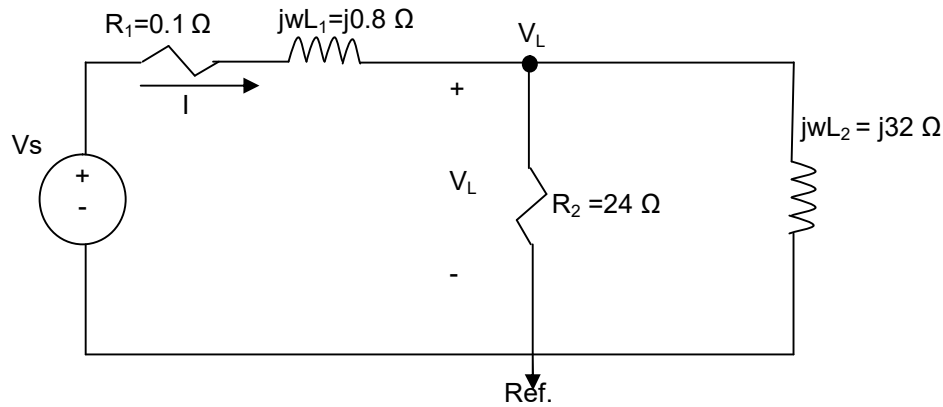

**Solution:**


a)  $V_s = ?$

$$\text{Write KCL at node } V_L \rightarrow (V_L - V_s)/(R_1 + j\omega L_1) + V_L/R_2 + V_L/j\omega L_2 = 0$$

$$(240 - V_s)/(0.1 + j0.8) + 240/24 + 240/j32 = 0$$

$$V_s = (0.1 + j0.8)(240/(0.1 + j0.8) + 10 - j7.5) = 247.35 \angle 1.85^\circ$$

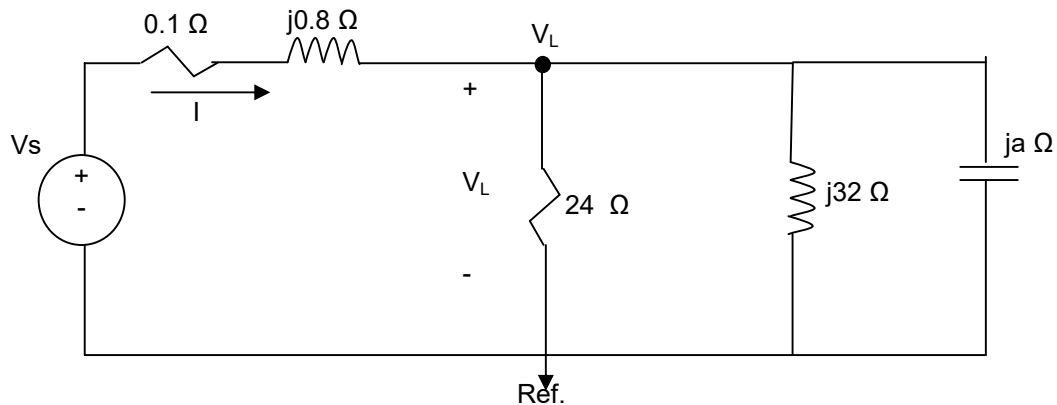b) Find capacitance reactance =  $a = -1/\omega c$  when  $V_L = 240 \text{ V}$  and magnitude of  $I$  is minimum.



$$I = 240/24 + 240/j32 + 240/ja = 10 - j(7.5 + 240/a)$$


$$\text{magnitude of } I = |I| = \sqrt{10^2 + (7.5 + 240/a)^2}$$

$$\text{Min of } |I| \text{ only when Cap. Cancels out the Inductor so } \rightarrow (7.5 + 240/a)^2 = 0 \rightarrow a = -32$$

Which means  $I = 10 \text{ A}$

$$V_s = (0.1 + j0.8) \cdot 10 + 240 = 241 + j8 = 241.13 \angle 1.9^\circ$$

c) Find capacitance reactance =  $a = -1/\omega c$  when  $|V_L| = |V_s|$  and magnitude of  $I$  is minimum

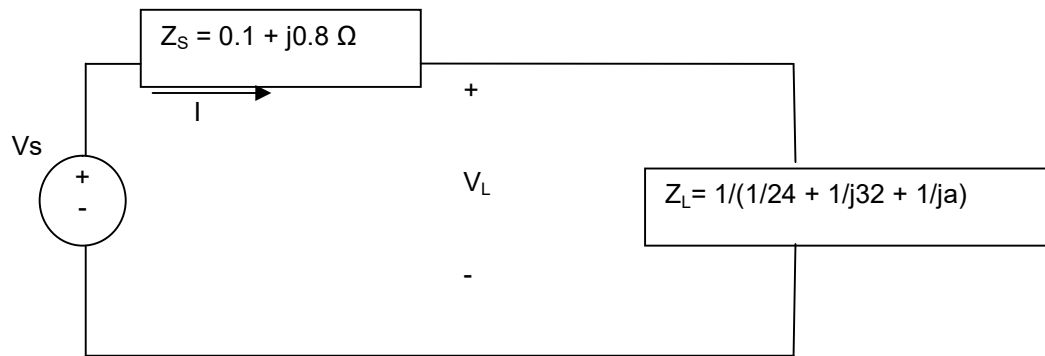


$$|V_L| = |V_s| \left( \frac{Z_L}{Z_L + Z_s} \right)$$

to Meet the condition  $\rightarrow \left( \frac{Z_L}{Z_L + Z_s} \right) = 1 \rightarrow$  since  $Z_s$  is not 0 then  $Z_L$  must be infinite

$$\text{or the denominator } |Z_L| \text{ of is } 0 \rightarrow |j4 + 3 - j96a| = \sqrt{3^2 + (4 - 96a)^2} = 0 \rightarrow$$

$$(4 - 96a)^2 = -9 \text{ Not Possible}$$

13U. Given the following Circuit:

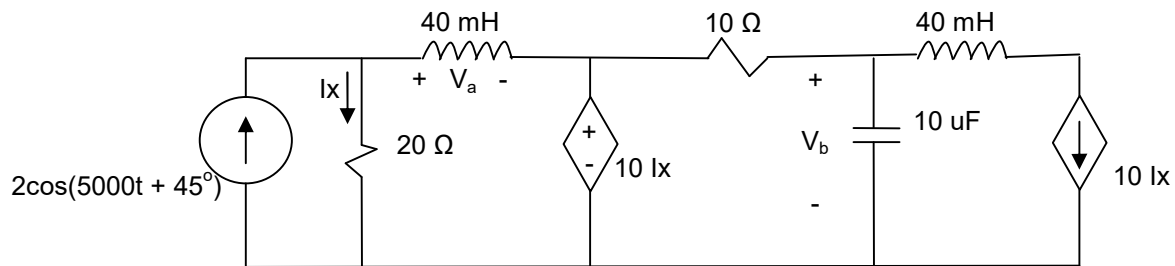

Find the relationship between  $V_a(t)$  and  $V_b(t)$  when the circuit is in steady state.

**Solution:**